

# Electric Current and Resistance

- Current
- Parts of a circuit
- Resistivity
- Ohm's Law
- Ohmic and Nonohmic materials
- Energy and Power


# Electric Current

- Electric current is the movement of electric charge
- Very important in our lives – we use it to deliver energy and information



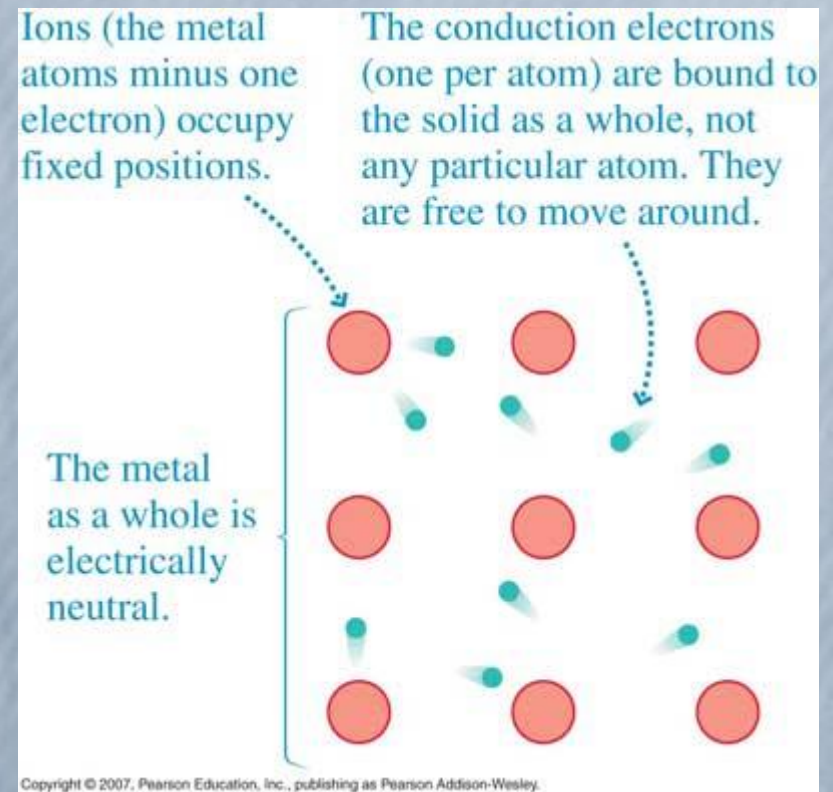
# Current in Conductors

- Current in conductors is produced by electrons moving through a lattice of fixed ions
- Current is a drift of the sea of electrons through the lattice
- Lattice is not charged




# Creating a current in a wire

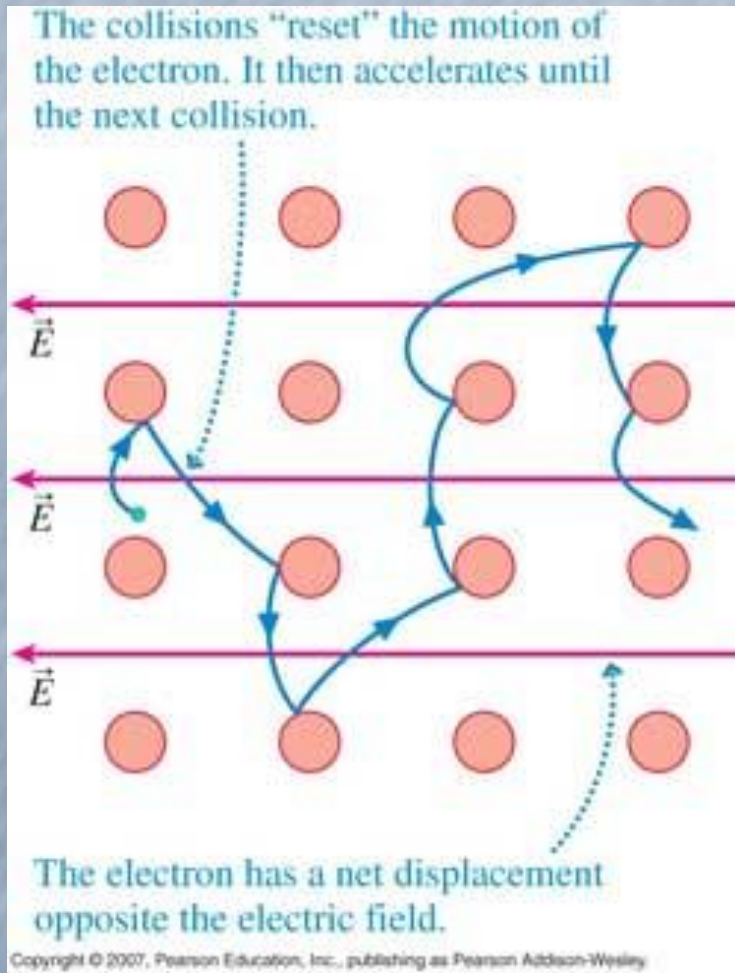

- Currents are created by an electric field pushing the electrons along a wire
- The electric field is produced by a potential difference along the length of the wire like a capacitor or a battery
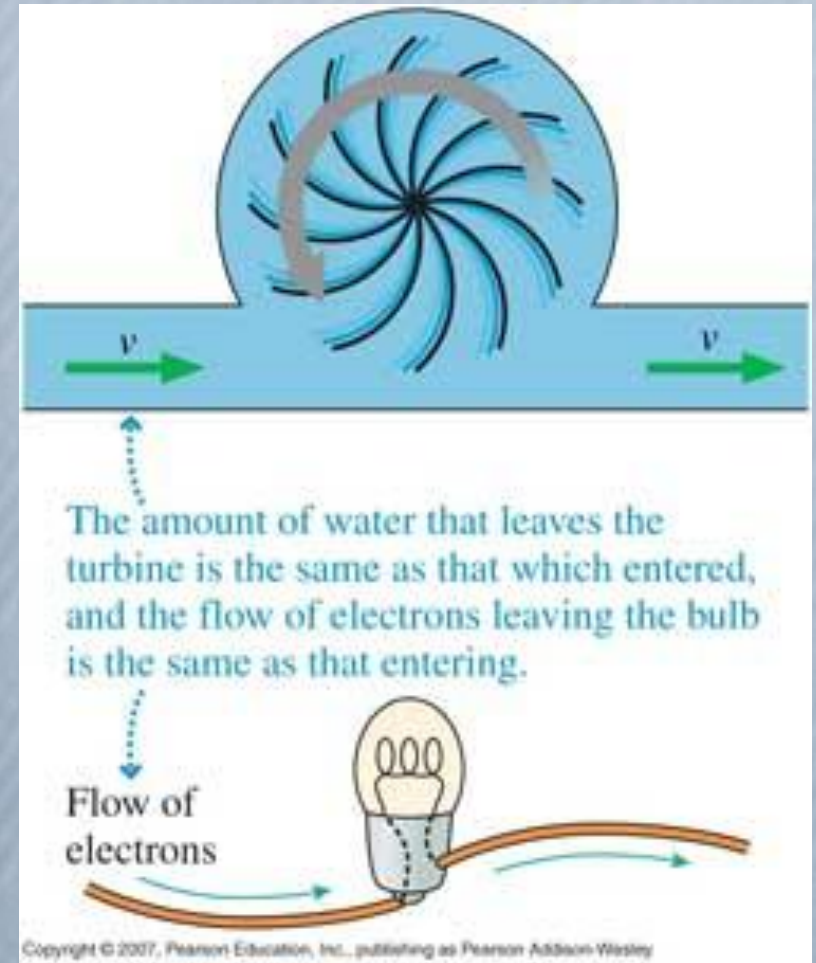
# Conservation of current

- Follows from the conservation of charge
- The current is the same at all points along a wire
- Similar to a water turbine, same amount of water in as water out




# Definition of Current

Current,  $I$ , is defined as the rate of change of **positive** charge:

$$I = \frac{\Delta Q}{\Delta t}$$

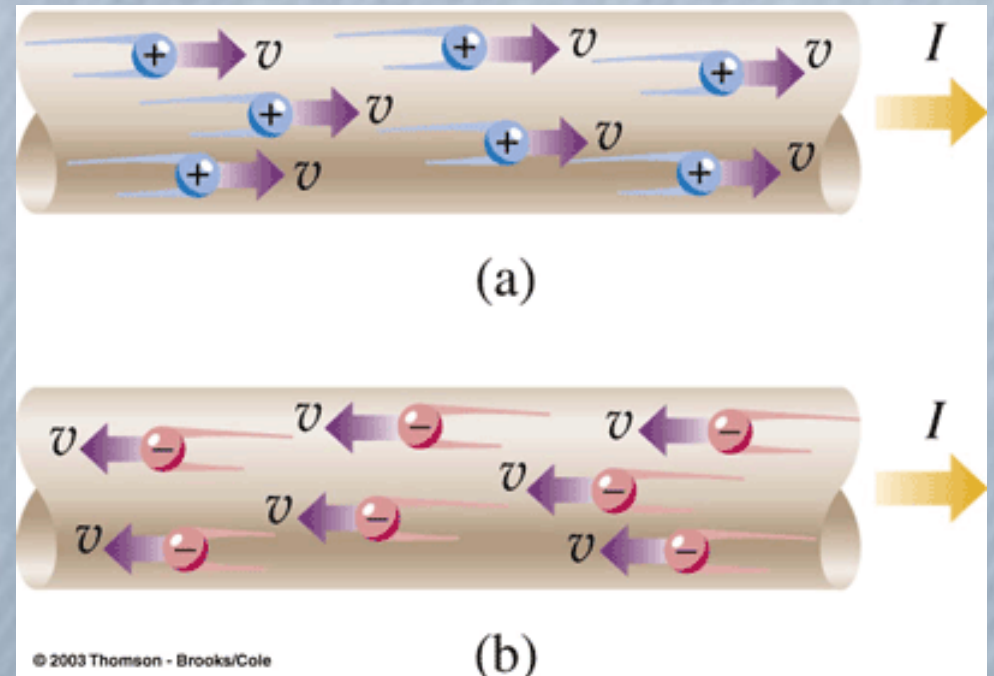Units: Coulombs/second or  
Amperes or Amps



# Definition of Current


Current,  $I$ , is defined as the rate of change of **positive** charge:

$$I = \frac{\Delta Q}{\Delta t}$$

Units: Coulombs/second or  
Amperes or Amps


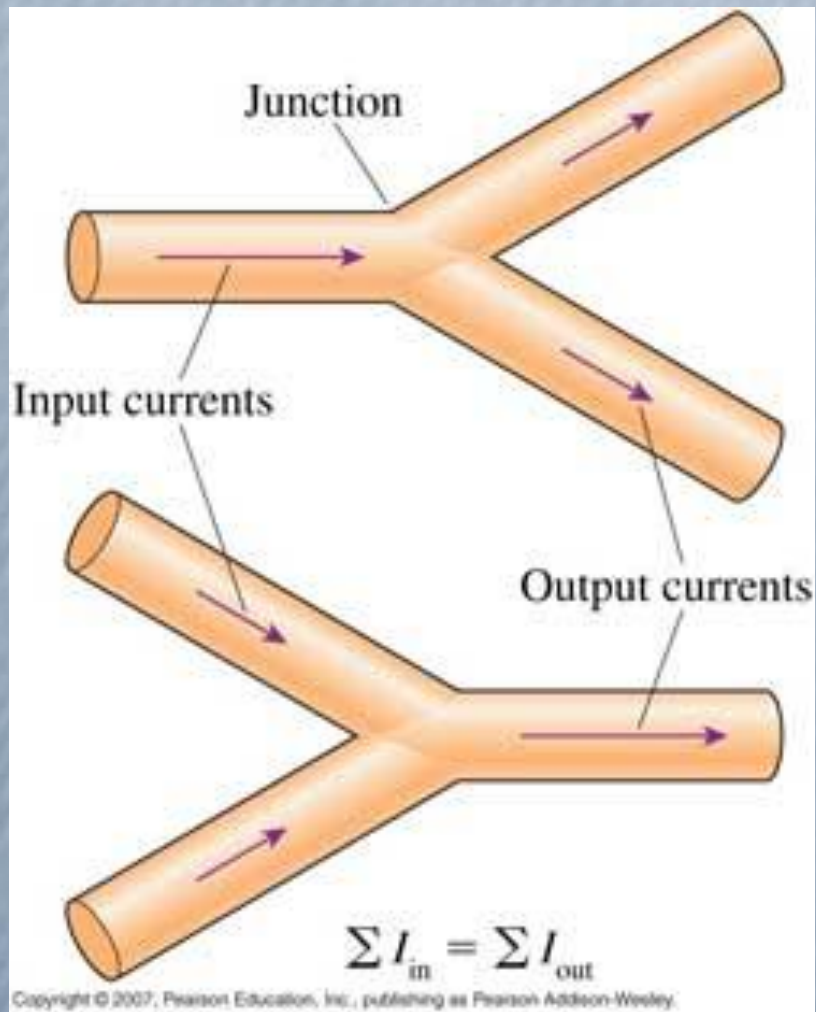
# Conservation of current: Kirchhoff's Law



The sum of currents into a junction must equal the currents flowing out of it

$$\sum I_{in} = \sum I_{out}$$


Sometimes expressed as:

$$\sum_j I_j = 0$$




# Example of Kirchhoff's Law

What are the currents in B and C ?

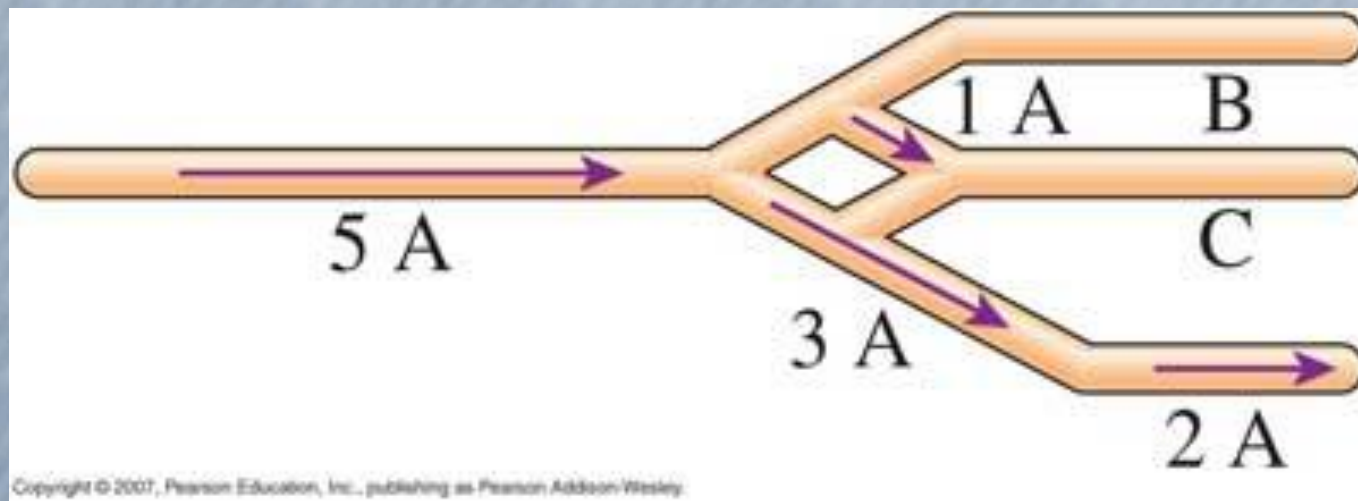


# Batteries

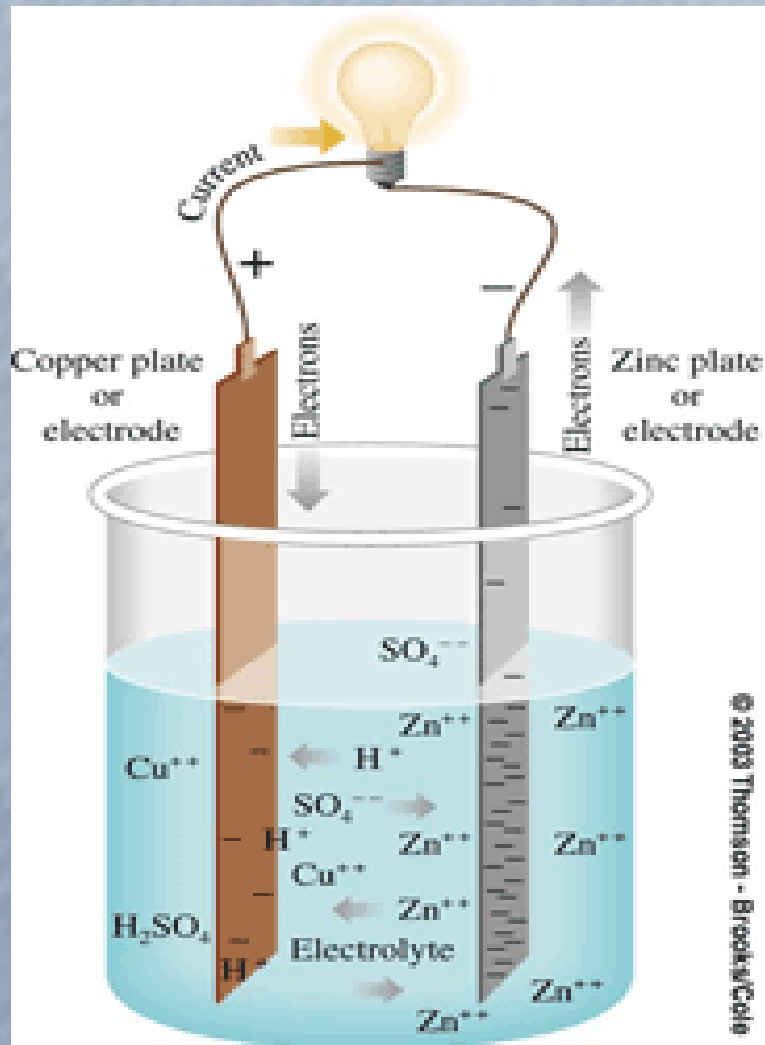

- Batteries produce a potential difference from chemical reactions in electrolytes
- Chemical energy from breaking bonds, force the separation of ions and electrons

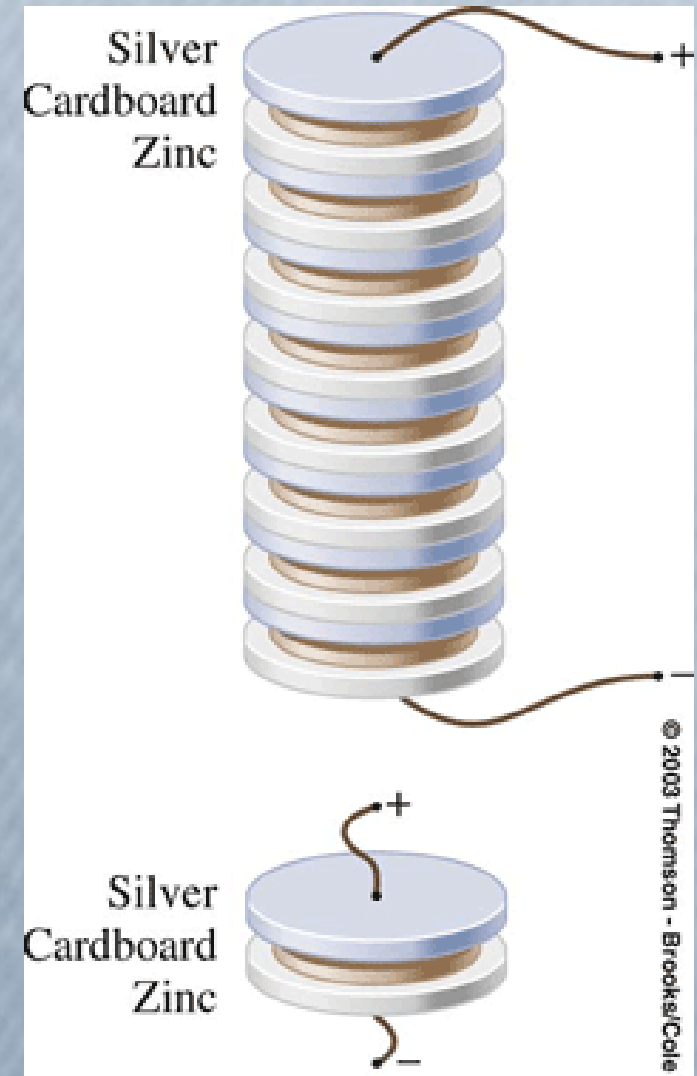
# E.M.F

- The chemical reaction creates a voltage between the electrodes, called the **emf** (electromotive force)
- The value of the emf depends on the chemicals in the battery – 1.2V NiCad, 1.5V alkaline
- The emf is also called **terminal voltage**
- Capacitors cannot “move” or recharge the electrons between electrodes, they have ZERO emf



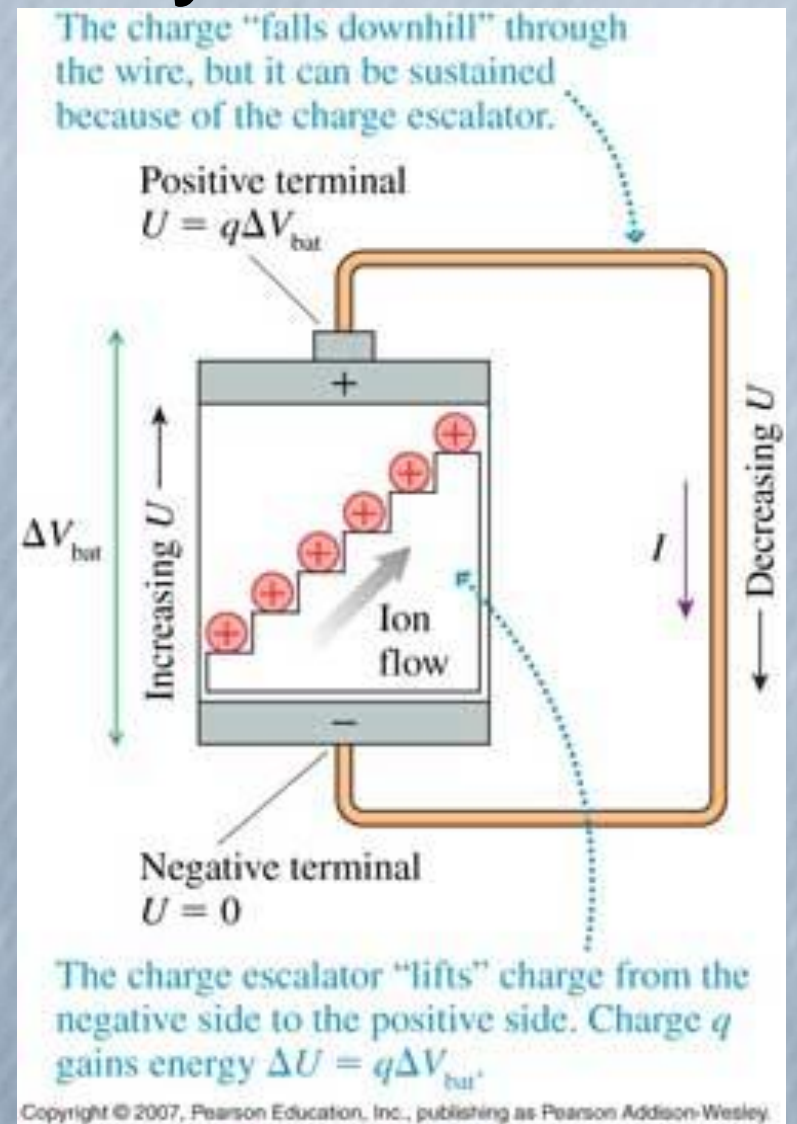
# Inside a battery

- Can be thought of as a machine increasing the potential of positive ions
- Competing a circuit will drain the energy of the battery



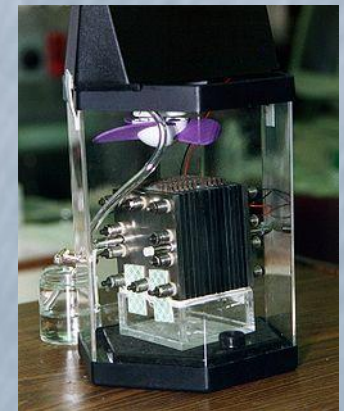
# Other types of current generators

- Electricity generators (Nuclear, Coal, Oil)
- Fuel Cells – mixing  $H_2$  and  $O_2$  with Polymer membrane electrolytes
- electric eel (*Electrophorus electricus*)




# A simple circuit

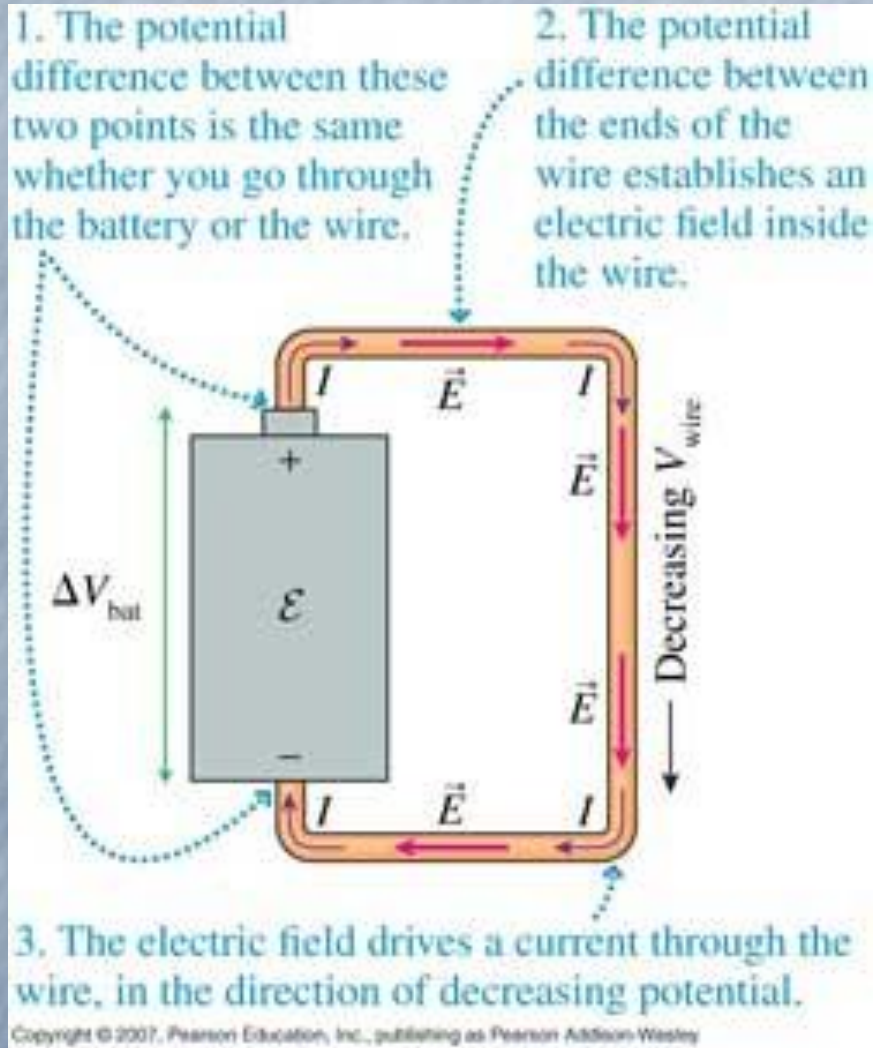

- The potential difference along the wire is the same as the emf
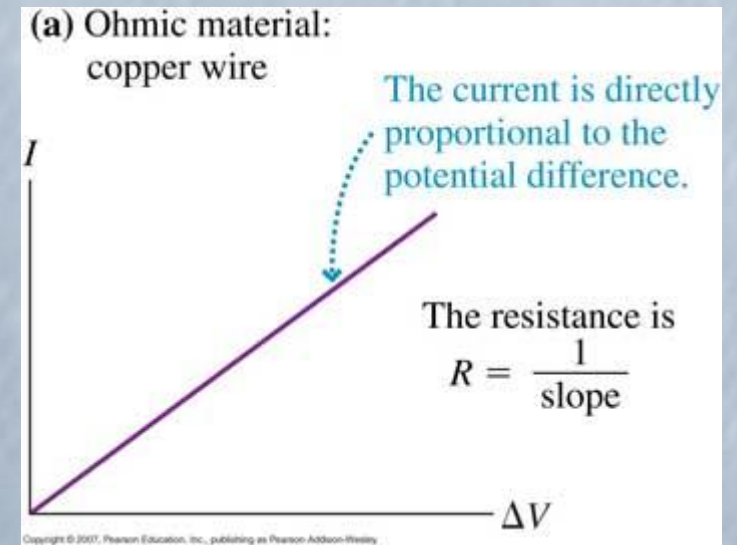
# Ohm's Law

- In many conductors – such as copper wire, the voltage  $V$ , required to drive a current  $I$  is linear
- Materials which are linear are said to obey Ohm's Law
- Leads to a useful concept called **resistance**




$$V = IR$$

$$V \propto I$$
$$R = \frac{V}{I}$$
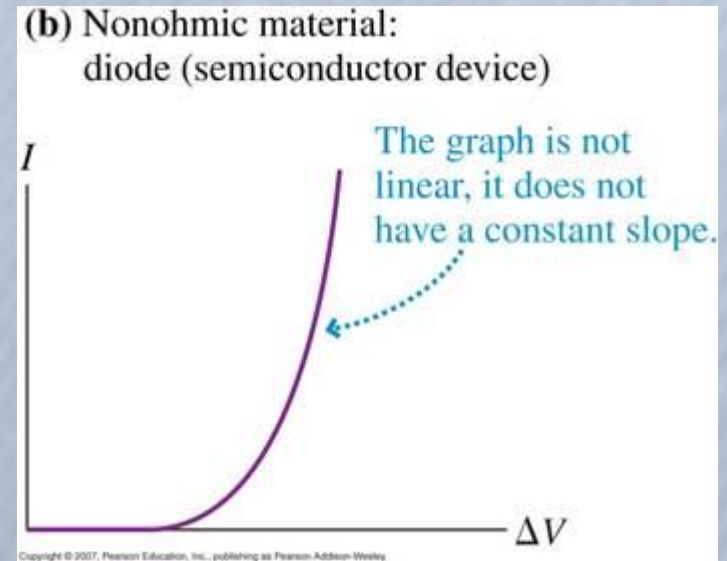
# Resistance

- Resistance is a useful concept, and is applied to materials which are nonohmic ( $I$  vs.  $V$  is not linear)
- Units of volts/amp or ohms ( $\Omega$ )
- Nonohmic materials include batteries, capacitors, air, semi-conductors in an electric field and superconductors




$$R = \frac{V}{I}$$



# Resistivity

Experiments with wires made with metals such as copper, show that the resistance,  $R$ , of a wire depends on the cross sectional area,  $A$ , and its length,  $L$


$$R = \rho \frac{L}{A}$$

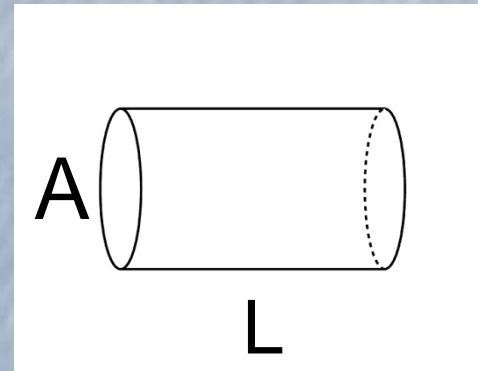

- This defines  $\rho$ , the **resistivity**, with units  $\Omega\text{m}$ .
- It is a property of the material – copper is  $1.7 \times 10^{-8}$ , muscle is 13, fat is 25  $\Omega\text{m}$
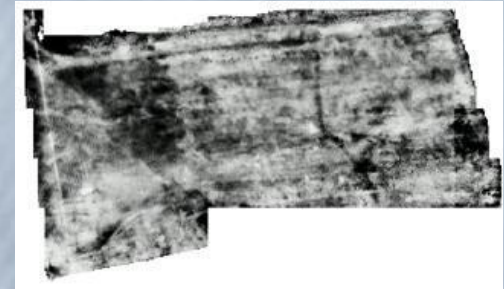
# Uses of Resistivity

- Measure the spreading of a gap with a thin wire
- Measure the fat to muscle ratio in the human body
- Testing drinking water
- Mapping resistivity in soil to look for archeological features



# Review of yesterday

Please answer the problem number 21 (a) and (b) on page 745 while we are waiting to start.

“What is the resistance of

(a) A 1.0m long...


(b) A 10cm long...”

Note the **resistivities** of Copper and Iron can be found in the inside end cover of Knight.
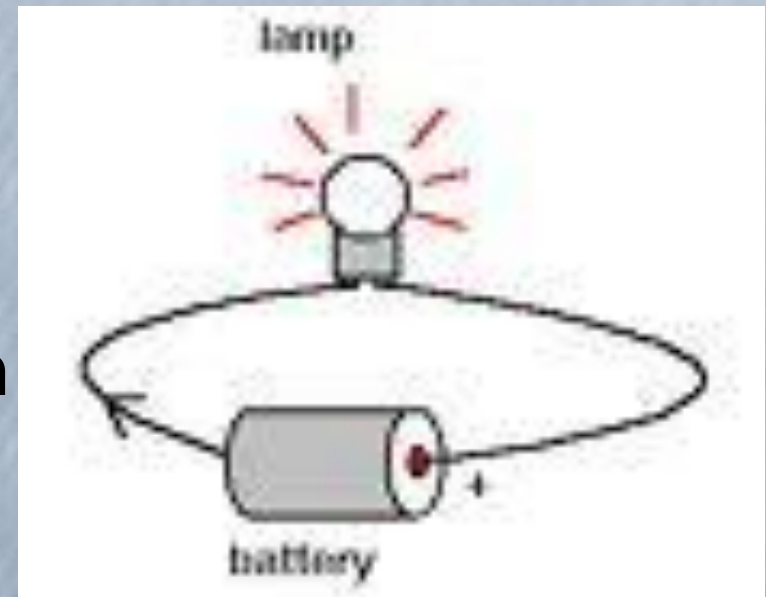
# Ideal Circuits

In circuits we will use, it is normal to make the following assumptions:

- Ideal wires – thick copper wires, with zero resistance
- Ideal batteries – that never run down, or have an emf dependent on the load
- Ideal bulbs – resistance does not change with time



# Ideal Circuits

In circuits we will use, it is normal to make the following assumptions:

- Ideal resistors – always follow Ohm's Law perfectly

Voltage drop across the resistor is  $\Delta V$ .  
The Electric field along the resistor  
will be

$$E = \frac{\Delta V}{L}$$



# Energy from a moving charge in a field

Energy transferred by a moving charge is

$$\Delta U = q\Delta V$$

- $\Delta U$  is the change in energy (Joules)
- $q$  is the charge (Coulombs)
- $\Delta V$  is the change in potential (Volts)

# Energy from a moving charge in a field

Energy transferred by a change in charge through a potential  $V$

$$\Delta U = \Delta q V$$

- $\Delta U$  is the change in energy (Joules)
- $\Delta q$  is the change in charge (Coulombs)
- $V$  is the potential the charge has been moved (Volts)

# Definition of Power from charge moving through a field

Power,  $P$ , is defined as the rate of change of energy

$$P = \frac{\Delta U}{\Delta t}$$

- $P$  is power (Joules per second, or Watts)
- $\Delta U$  is the change in energy (Joules)
- $\Delta t$  is how long the change in energy lasts (seconds)



# Definition of Power from charge moving through a field

$$P = \frac{\Delta U}{\Delta t} = \frac{\Delta q}{\Delta t} V_{emf} = I V_{emf}$$

- $P$  is the power, Joules per second or Watts
- $I$  is the current, Coulombs per second or Amps
- $V_{emf}$  is the change in potential (Volts)

# Power and Resistance


- Using  $P=VI$  and  $V=IR$  we get 2 important equations
- Power dissipation increases quadratically with either current or voltage at constant resistance

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$
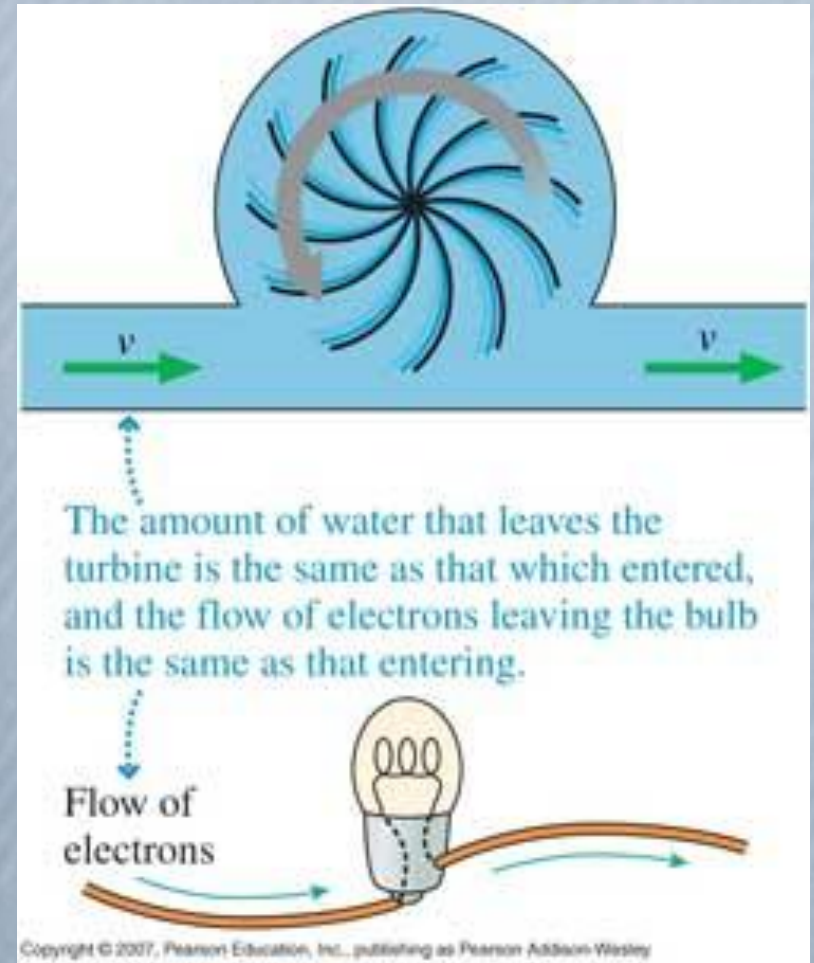
# Power in circuits

- Where does the power come from ?
- Current is conserved!



# Summary

- Current
- Parts of a circuit
- Resistivity
- Ohm's Law
- Ohmic and Nonohmic materials
- Energy and Power

# Homework

Knight Chapter 22, page 747

53, 54, 55, 56, 58, 59, 60 ,62

# Review question on Currents

While we are waiting please try question 7 on page 745

“A capacitor is charged to  $6.0 \times 10^{-4}$  C, then discharged....”