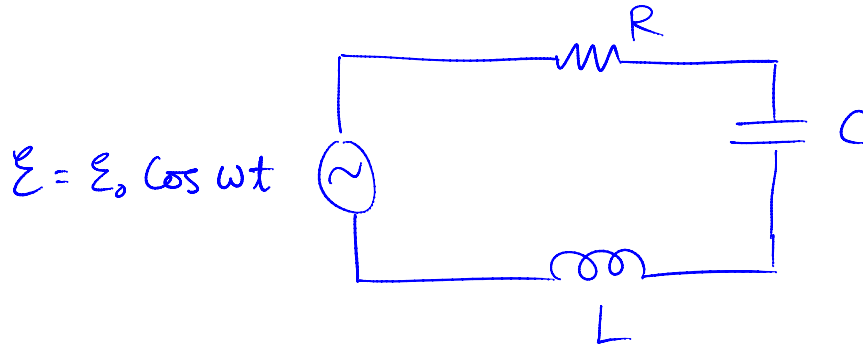


Solution to Problems 5 & 6

Phys 270

Problem 5:

A series RLC circuit would look like



The Resonance Frequency of the circuit is given as

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

We are given that

$$\omega_0 > \omega$$

The current i is given as

$$i = I \cos(\omega t - \varphi)$$

where φ , which can be positive or negative,
is

$$\varphi = \tan^{-1} \frac{X_L - X_C}{R} = \frac{V_L - V_C}{V_R}$$

Now $X_L = \omega L$ and $X_C = \frac{1}{\omega C}$

$$\Rightarrow \varphi = \tan^{-1} \frac{\omega L - \frac{1}{\omega C}}{R}$$

$$= \tan^{-1} \frac{\omega L}{R} \left[1 - \frac{1}{(\omega L)(\omega C)} \right]$$

Clearly, since

$$\varphi < 0, X_L < X_C$$

$$\Rightarrow IX_L < IX_C$$

$$\Rightarrow V_L < V_C$$


$$= \tan^{-1} \frac{\omega L}{R} \left[1 - \frac{1}{\omega^2 LC} \right]$$

$$= \tan^{-1} \frac{\omega L}{R} \left[1 - \frac{(\omega_0 \sqrt{LC})^2}{\omega^2} \right]$$

$$= \tan^{-1} \frac{\omega L}{R} \left[1 - \frac{\omega_0^2}{\omega^2} \right]$$

If $\omega_0 > \omega$, $1 - \frac{\omega_0^2}{\omega^2} < 0 \Rightarrow \varphi < 0$

Hence the current leads the EMF

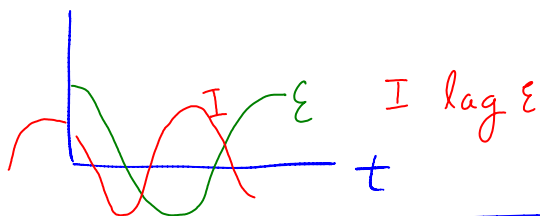

Problem 6:

The charge on the capacitor


$$\text{is } Q = C \cdot V$$

and the Electric-field inside is


$$E = \frac{V}{L} \Rightarrow V = E \cdot L$$

$$\Rightarrow Q = C \cdot E \cdot L$$

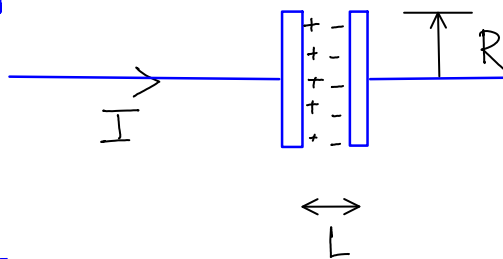Hence, the current $I = \frac{dQ}{dt} = C \cdot L \cdot \frac{dE}{dt}$ Ⓢ



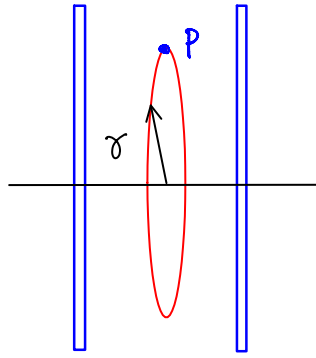Now, let's consider a circular loop of radius r , passing thro' point P.



Now, we have

$$\int_{\text{loop}} \vec{B} \cdot d\vec{s} = \mu_0 \epsilon_0 \frac{d\Phi_E^{\text{loop}}}{dt}$$

Where Φ_E^{loop} is the flux of the electric field through the loop in picture.

$$\begin{aligned} \Rightarrow B \cdot 2\pi r &= \mu_0 \epsilon_0 \cdot \frac{d}{dt} E \cdot \pi r^2 \\ &= \mu_0 \epsilon_0 \pi r^2 \frac{dE}{dt} \end{aligned}$$

But from ①, $\frac{dE}{dt} = \frac{I}{CL}$

Hence

$$B \cdot 2\pi r = \mu_0 \epsilon_0 \pi r^2 \cdot \frac{I}{C \cdot L}$$

$$B = \frac{\mu_0 \epsilon_0 I \cdot r}{CL \cdot 2}$$

Now, for a parallel plate Capacitor,

$$C = \frac{\epsilon_0 A}{L} = \frac{\epsilon_0 \pi R^2}{L}$$

$$\Rightarrow B = \frac{\mu_0 \cancel{\epsilon_0} I}{\frac{\cancel{\epsilon_0} \pi R^2}{L} \cdot L} \cdot \frac{r}{2}$$

$$B = \frac{\mu_0 I}{2\pi} \frac{r}{R^2}$$

25