
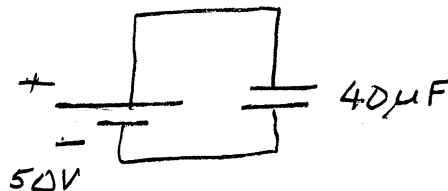


HOMEWORK - SOLNS # 7


16-37 FIRST CALCULATE CHARGE ON $25\mu\text{F}$ and $40\mu\text{F}$

$$Q = CV$$

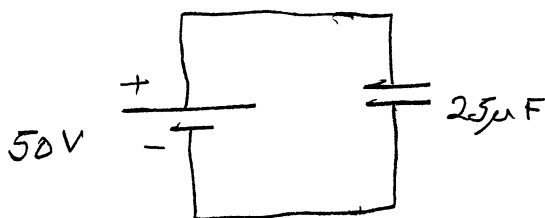

$$Q_{25} = (50 \times 25 \times 10^{-6}) \text{ C} \\ = 1.25 \times 10^{-3} \text{ C}$$

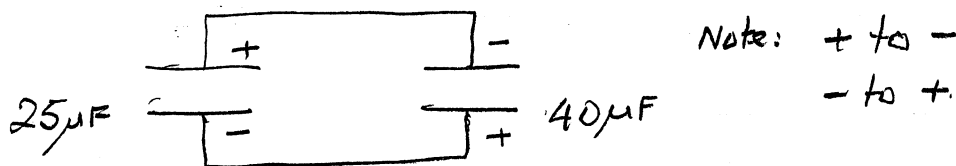
$$Q_{40} = (50 \times 40 \times 10^{-6}) \text{ C} \\ = 2.00 \times 10^{-3} \text{ C}$$



Charge is conserved so Total charge now is

$$Q_{40} - Q_{25} = (2 \times 10^{-3} - 1.25 \times 10^{-3}) \text{ C} \\ = 7.5 \times 10^{-4} \text{ C} = 750 \mu\text{C}$$

and the capacitors

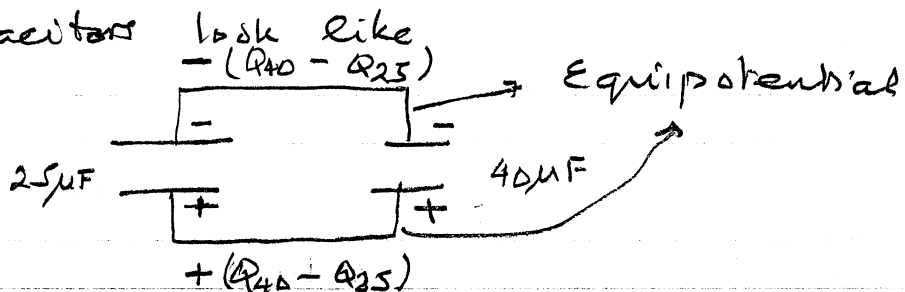

Because conductor is Equipotential $V_{25} = V_{40}$

$$\frac{Q_{25}}{25 \times 10^{-6}} = \frac{Q_{40}}{40 \times 10^{-6}} = V_{25} = V_{40}$$


$$\frac{7.5 \times 10^{-4} - Q_{40}}{25 \times 10^{-6}} = \frac{Q_{40}}{40 \times 10^{-6}}$$

$$Q_{40} = 462 \mu\text{C}$$

$$Q_{25} = 750 - 462 \mu\text{C} = 288 \mu\text{C}$$

$$V_{40} = \frac{Q_{40}}{40} = 11.5 \text{ V}$$


40

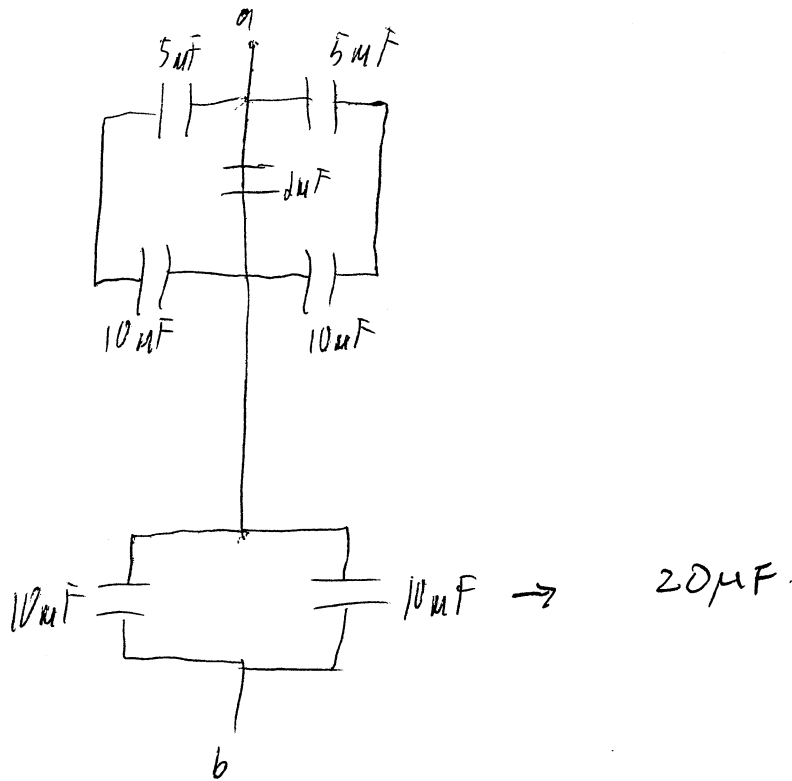

For TWO CAPACITORS.

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} \text{ series}$$

$$C_p = C_1 + C_2 \text{ parallel}$$

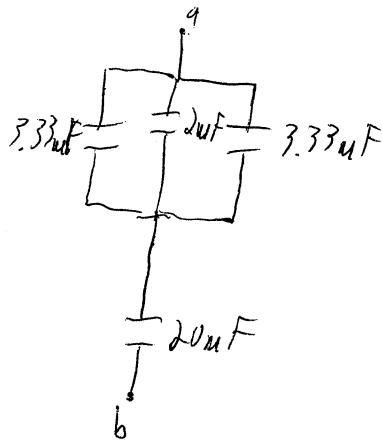


and 5µF and 10µF in series

$$\frac{1}{C_s} = \frac{1}{5} + \frac{1}{10} = \frac{3}{10}$$

$$C_s = 10/3 = 3.33\mu F.$$

Next 3.33µF, 2µF and 3.33µF in parallel


hence

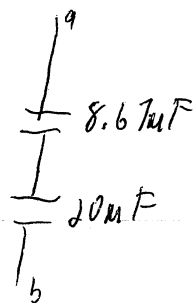


8.67µF and 20µF in series

$$\frac{1}{C_{ab}} = \frac{1}{8.67} + \frac{1}{20}$$

$$C_{ab} = 6.05\mu F$$

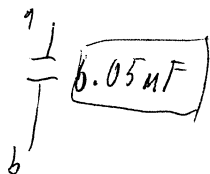

44

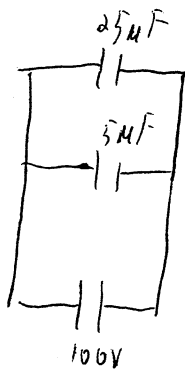


$$U_E = \frac{Q^2}{2C} = \frac{1}{2} CV^2$$

(a.) $U_E = \frac{1}{2} (100V)^2 (25\mu F + 5\mu F)$

~~Energy~~

$$U_E = 0.15 \text{ J}$$

(b)

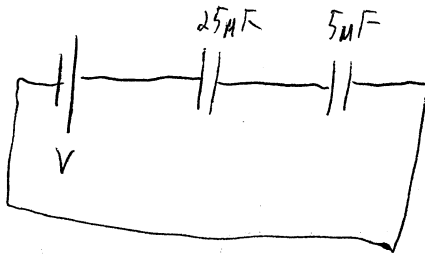

In Series

$$\frac{1}{C} = \frac{1}{5} + \frac{1}{25}$$

$$= \frac{6}{25} \quad C = \frac{25}{6} \mu F$$

$$0.15 \text{ J} = \frac{1}{2} V^2 ((25\mu F)^{-1} + (5\mu F)^{-1})^{-1}$$

$$V = 268 \text{ V}$$

C reduces from 30 μF to 4.16 μF hence V must increase by $\frac{30}{4.16}$

49

(a)

$$C = \frac{\kappa \epsilon_0 A}{d}$$

$$A = 175 \text{ cm}^2 \left(\frac{\text{m}}{100 \text{ cm}} \right)^2 = 0.0175 \text{ m}^2$$

$$= \frac{2.1 (8.85 \times 10^{-12} \frac{\text{C}^2}{\text{Nm}}) (0.0175 \text{ m}^2)}{(0.04 \times 10^{-3} \text{ m})}$$

$$= \underline{8.13 \times 10^{-9} \text{ F}}$$

(b)

$$E_{\text{max}} = 60 \times 10^6 \text{ V/m}$$

$$V_{\text{max}} = E_{\text{max}} d$$

$$= (60 \times 10^6 \text{ V/m}) (0.04 \times 10^{-3} \text{ m})$$

$$\underline{V_{\text{max}} = 2400 \text{ V}}$$

For Teflon

From Table 16.1

on p 557 we know that

$$\kappa = 2.1.$$

and

$$E_{\text{max}} = 60 \times 10^6 \text{ V/m}$$

50


$$C = 9.5 \times 10^{-8} \text{ F}$$

$$A = Lw \quad w = 7 \times 10^{-2} \text{ m}$$

$$d = \cancel{.004 \times 10^{-3} \text{ m}} + .025 \times 10^{-3} \text{ m} = 2.5 \times 10^{-5} \text{ m}$$

$$x = 3.70$$
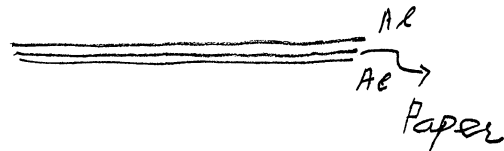
$$C = \frac{\kappa \epsilon_0 A}{d} = \frac{\kappa \epsilon_0 Lw}{d}$$



$$L = \frac{dC}{\kappa \epsilon_0 w} = \frac{(2.5 \times 10^{-5} \text{ m})(9.5 \times 10^{-8} \text{ F})}{3.70 (8.85 \times 10^{-12} \frac{\text{C}^2}{\text{Vm}}) (7 \times 10^{-2} \text{ m})}$$

$$L = 1.09 \text{ m}$$

54

$$C_p = C_1 + C_2 \rightarrow \textcircled{1}$$

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2}, \quad C_s = \frac{C_1 C_2}{C_1 + C_2} \rightarrow \textcircled{2}$$

Multiply $\textcircled{1}$ and $\textcircled{2}$

$$C_s C_p = C_1 C_2, \quad C_1 = \frac{C_s C_p}{C_2}$$

$$\text{Substitute in } \textcircled{1} \quad C_p = \frac{C_s C_p}{C_2} + C_2$$

$$\text{or} \quad C_p C_2 = C_s C_p + C_2^2$$

$$C_2^2 - C_p C_2 + C_s C_p = 0$$

$$\text{Solve quadratic } C_2 = \frac{C_p \pm \sqrt{C_p^2 - 4C_s C_p}}{2}$$

$$C_1 = C_p - C_2 = \frac{2C_p - C_p \mp \sqrt{C_p^2 - 4C_s C_p}}{2}$$

$$= \frac{C_p \mp \sqrt{C_p^2 - 4C_s C_p}}{2}$$

PHYS 122

Homework #7 solutions

Ch. 17: 1, 5, 8, 15, 19, 21, ...

⑤ The period of the electron in its orbit is $T = \frac{2\pi r}{v}$.


The current represented by the orbiting electron is

$$I = \frac{\Delta Q}{\Delta t} = \frac{|e|}{T} = \frac{v|e|}{2\pi r}$$

$$= \frac{(2.19 \times 10^6 \text{ m/s})(1.60 \times 10^{-19} \text{ C})}{2\pi(5.29 \times 10^{-11} \text{ m})}$$

$$= 1.05 \times 10^{-3} \text{ C/s}$$

$$I = 1.05 \text{ mA}$$

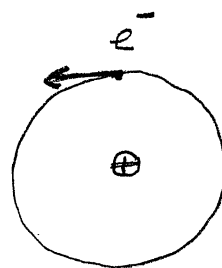

① The charge that moves past the cross section:


$$\Delta Q = I(\Delta t)$$

of electrons:

$$n = \frac{\Delta Q}{|e|} = \frac{I(\Delta t)}{|e|}$$

$$= \frac{(80.0 \times 10^{-3} \text{ C/s})[(10.0 \text{ min})(60.0 \text{ sec/min})]}{1.60 \times 10^{-19} \text{ C}}$$
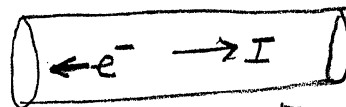
$$n = 3.00 \times 10^{20} \text{ electrons}$$



Electrons drift to left, direction of I is to right*

* Remember that electrons move in the opposite direction of the conventional current.

⑧ Assuming that, on average, each aluminum atom contributes one electron, the density of charge carriers is the same as the number of atoms per cubic meter.

$$n = \frac{\text{density}}{\text{mass per atom}} \quad M = \text{mass/mol. / mol}$$

$$N_A = \text{Avogadro's No}$$

$$= \frac{\rho}{M/N_A}$$

$$= \frac{N_A \rho}{M}$$

$$= \frac{(6.02 \times 10^{23} / \text{mol}) [2.7 \text{ g/cm}^3] (10^6 \text{ cm}^3 / \text{m}^3)}{26.98 \text{ g/mol}}$$

$$\Rightarrow n = 6.0 \times 10^{28} / \text{m}^3$$

Then, the drift speed of the electrons in the wire :

$$v_d = \frac{I}{n |e| A}$$

$$= \frac{5.0 \text{ C/s}}{(6.0 \times 10^{28} / \text{m}^3) (1.60 \times 10^{-19} \text{ C}) (4.0 \times 10^{-6} \text{ m}^2)}$$

$$v_d = 1.3 \times 10^{-4} \text{ m/s}$$

15

$$\textcircled{a} \quad R = \frac{\Delta V}{I} = \frac{12V}{0.40A} = \boxed{30 \Omega}$$

$$\textcircled{b} \quad \text{From } R = \frac{\rho L}{A},$$

$$\rho = \frac{R \cdot A}{L}$$

$$= \frac{(30 \Omega) [\pi (0.40 \times 10^{-2} \text{ m})^2]}{3.2 \text{ m}}$$

$$\Rightarrow \boxed{\rho = 4.7 \times 10^{-4} \Omega \cdot \text{m}}$$

19) The volume of material in the wire is constant :

$$V = AL_0 = (\pi r_0^2) L_0 = \text{constant.}$$

So, as the wire is stretched to decrease its radius, the length increases such that

$$(\pi r_f^2) L_f = (\pi r_0^2) L_0.$$

This gives

$$L_f = \left(\frac{r_0}{r_f}\right)^2 L_0 = \left(\frac{r_0}{0.25 r_0}\right)^2 L_0 = (4.0)^2 L_0 = 16 L_0.$$

The new resistance is —

$$R_f = \rho \frac{L_f}{A_f} = \rho \frac{L_f}{\pi r_f^2} = \rho \frac{16L_0}{\pi (r_0/4)^2}$$

$$= 16(4)^2 \rho \frac{L_0}{\pi r_0^2} = 256 R_0$$

$$= 256 (1.00 \Omega)$$

$$\Rightarrow \boxed{R_f = 256 \Omega}$$

② From Definition of Resistance

$$\Delta V = I_i R_i = I_f R_f$$

∴ The current in Antarctica is increased because on cooling the resistance reduces

$$I_f = I_i \left(\frac{R_i}{R_f} \right)$$

$$= I_i \left[\frac{R_0 [1 + \alpha (T_i - T_0)]}{R_0 [1 + \alpha (T_f - T_0)]} \right]$$

$$= (1.00 \text{ A}) \left(\frac{1 + [3.90 \times 10^{-3} (\text{C}^{-1})] (58.0^\circ\text{C} - 20.0^\circ\text{C})}{1 + [3.90 \times 10^{-3} (\text{C}^{-1})] (-88.0^\circ\text{C} - 20.0^\circ\text{C})} \right)$$

$$\Rightarrow \boxed{I_f = 1.98 \text{ A}}$$