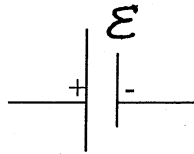


DEVICES - AC CIRCUITS

Battery Source of Coulomb \vec{E} -field

Output is *emf*: ϵ




Capacitor: Container for \vec{E} -field $C = \frac{Q}{V}$


Potential Energy $U_E = \frac{Q^2}{2C}$

$\eta_E =$ Energy stored per $m^3 = \frac{1}{2} \epsilon_0 E^2$
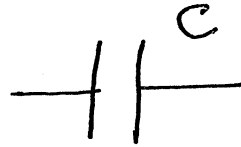
$$\epsilon_0 = 9 \times 10^{-12} \text{ F/m}$$



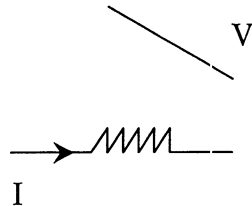Resistor: Represents that it costs energy to transport charge through a conductor



$$R = \frac{V}{I} \quad \left[\vec{J} = \sigma \vec{E} \right]$$

$$\text{Power loss } P = I^2 R = \frac{V^2}{R}$$

Inductor: A time varying current causes a Non-Coulomb \vec{E} -field, induced *emf*, $L = \frac{-\epsilon}{(\Delta i / \Delta t)}$

Container for \vec{B} -field, Potential Energy $U_B = \frac{1}{2} Li^2$



$\eta_B =$ Energy stored per $m^3 = \frac{B^2}{2\mu_0}$

A.C. Generator: Wire loops of area A rotated at ω rad/s in a \vec{B} -field. Generates non-coulomb

\vec{E} -field in the loops, produces an *emf*: $\epsilon = \omega NBA \sin(\omega t)$

Where $N = \#$ of turns in the loop. Hence *ac-generator*

$$\Phi_B = NBA \cos(\theta)$$

where θ is angle between \hat{n} and \vec{B}

Rottn by ω rad/s makes





$$\theta = \omega t, \quad \Phi_B = NBA \cos \omega t$$


$$\text{So } \frac{\Delta \Phi_B}{\Delta t} = -NBA\omega \sin \omega t, \quad \epsilon = -\frac{\Delta \Phi_B}{\Delta t} = \omega NBA \sin \omega t$$

CIRCUITS

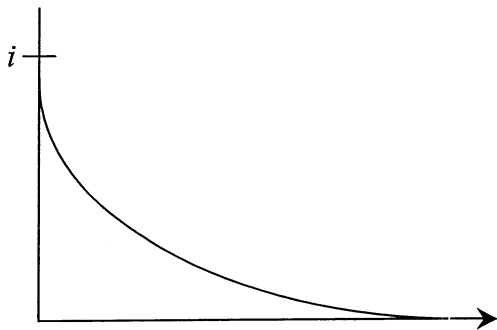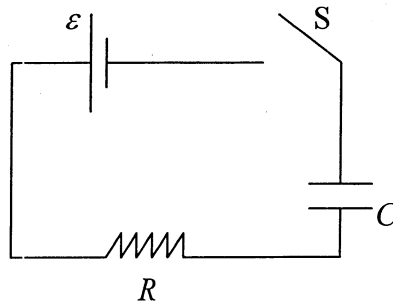I. RC with battery, close switch at $t=0$, current flows immediately, potential across C appears later $\varepsilon = \frac{q}{C} + iR$



$$i = \frac{\varepsilon}{R} e^{-t/RC}$$

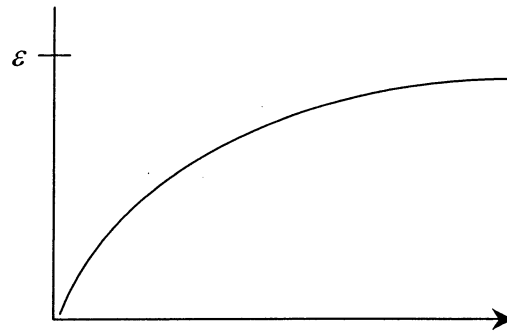


$$v_c = \varepsilon \left[1 - e^{-t/RC} \right]$$

$$\tau = RC$$

N.B. Current first, voltage later.


II. RL With Battery

Close switch at $t=0$, v_L immediately jumps to $|\varepsilon|$

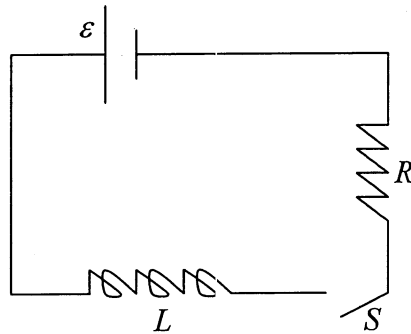


Current builds slowly.
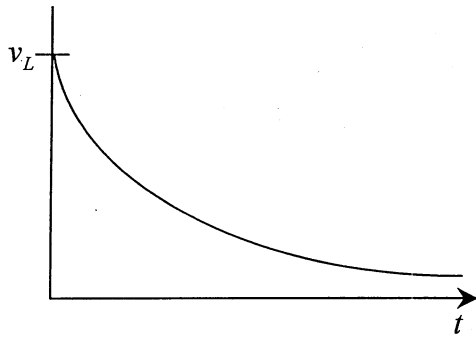
$$\varepsilon = L \frac{\Delta i}{\Delta t} + iR$$



$$v_L = \varepsilon e^{-Rt/L}$$

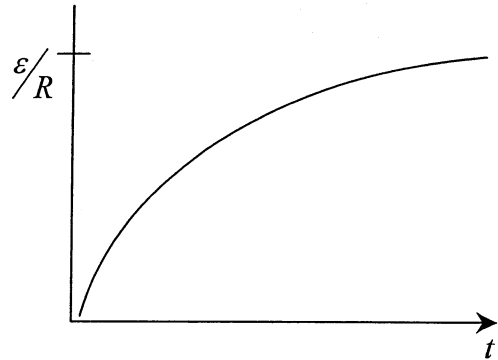

$$i = \frac{\varepsilon}{R} \left[1 - e^{-Rt/L} \right]$$


$$\tau = \frac{L}{R}$$

Note: Voltage First, Current Later.

III. LC-Circuit: Undamped Oscillator

First charge C to Q_0 . Close switch at $t=0$. Energy stored in

capacitor $U_E = \frac{Q_0^2}{2C}$

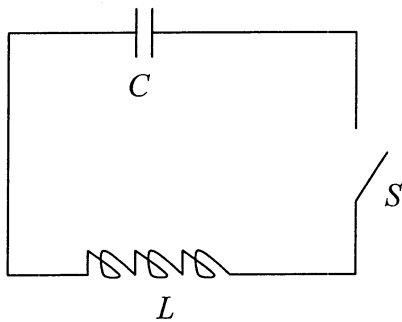


Charge begins to flow. Total Energy = (Energy in \vec{E} -field) + (Energy in \vec{B} -field)
 = (Energy in C) + (Energy in L)

$$\frac{Q_0^2}{2C} = \frac{q^2}{2C} + \frac{1}{2} L \left(\frac{\Delta q}{\Delta t} \right)^2$$

Recognize, similarity to spring-mass oscillator
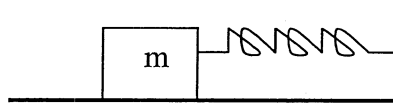
$$\frac{1}{2}kA^2 = \frac{1}{2}kx^2 + \frac{1}{2}m\left(\frac{\Delta x}{\Delta t}\right)^2$$



$$x \rightarrow q$$

$$x = A \cos \omega t$$

$$m \rightarrow L$$



$$\omega_0 = \sqrt{\frac{k}{m}}$$

$$k \rightarrow \frac{1}{C}$$



$$q = Q_0 \cos \omega_0 t$$

Now

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

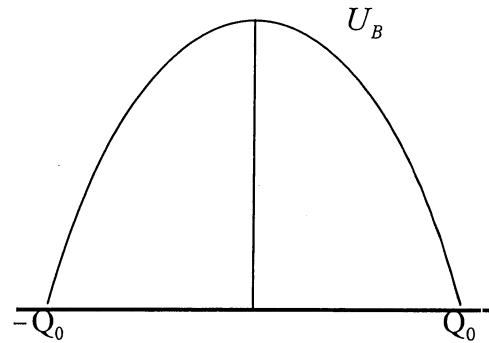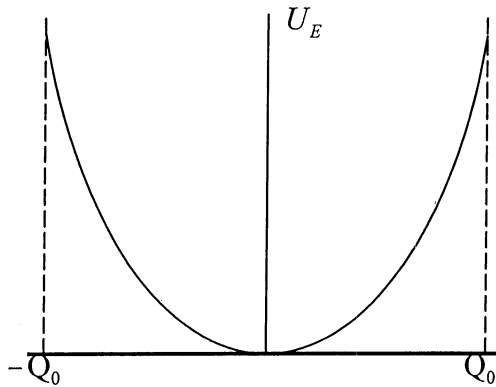

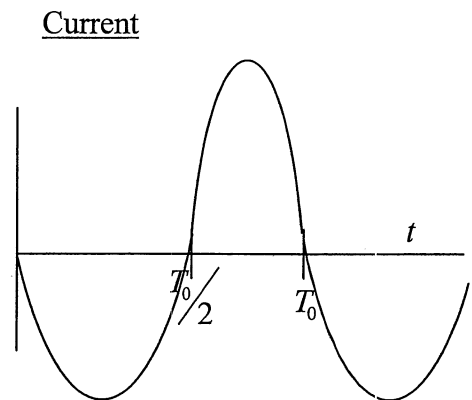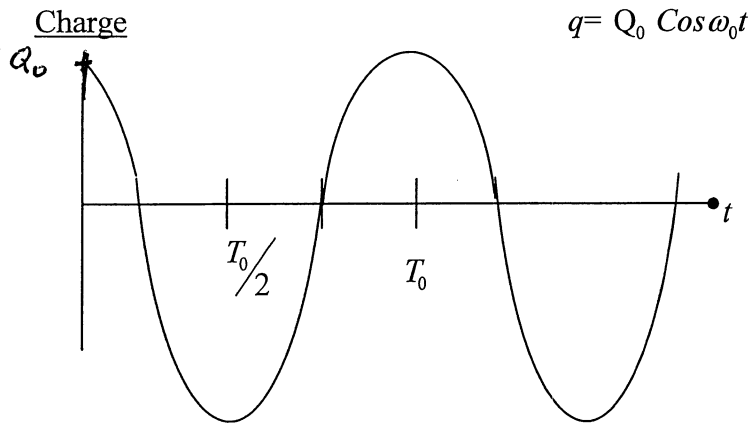\vec{E} -field collapses giving rise to \vec{B} -field and vice versa.




$$i = -Q_0 \omega_0 \sin \omega_0 t$$

$$\text{Period } T = \frac{2\pi}{\omega_0}$$

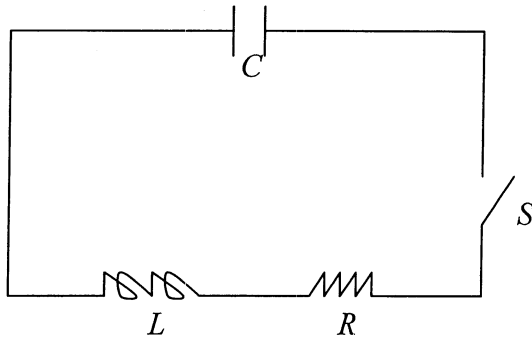IV. LCR-CIRCUIT: DAMPED OSCILLATOR.

At $t=0$, charge C to Q_0 close switch. Now driving i through R costs $i^2 R$ per second.



So $\left(\frac{q^2}{2C} + \frac{1}{2}Li^2\right)$ IS NOT CONSTANT

$$\frac{\Delta\left(\frac{q^2}{2C} + \frac{1}{2}Li^2\right)}{\Delta t} = -i^2 R$$


-ive sign on right because energy is being lost (R is getting warmer).

Now $q = Q_0 e^{-Rt/2L} \cos \omega t$

$$\omega = \omega_0 \left[1 - \frac{1}{(2\omega_0\tau)^2}\right]^{1/2}$$

$$\tau = \frac{L}{R}$$

$$\omega_0\tau = \text{Quality factor} = Q_e$$

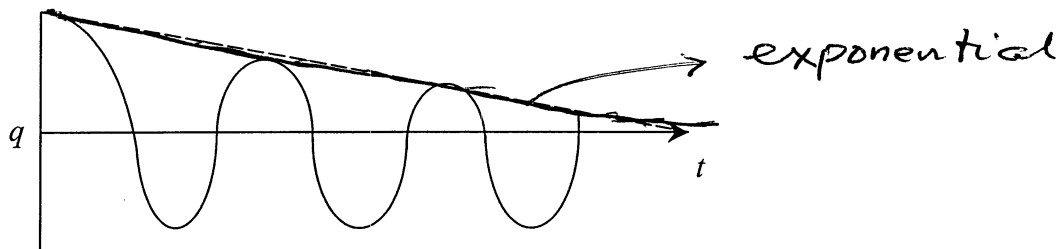


Note 1: smaller R , larger the duration for which the oscillations persist.

Note 2: R plays role of friction; as always energy lost goes to raise temperature. Electrical Equivalent of Heat.

CIRCUITS: AC

I. Resistor and Generator

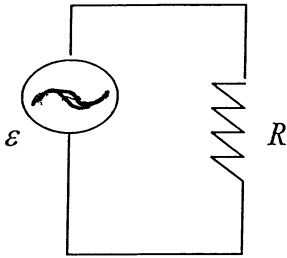

$$V_R = IR$$

so

$$\text{If } \varepsilon = \varepsilon_0 \sin \omega t$$


$$i = \frac{\varepsilon_0}{R} \sin \omega t$$

Current and voltage are in phase.

Power


$$P(t) = iv$$
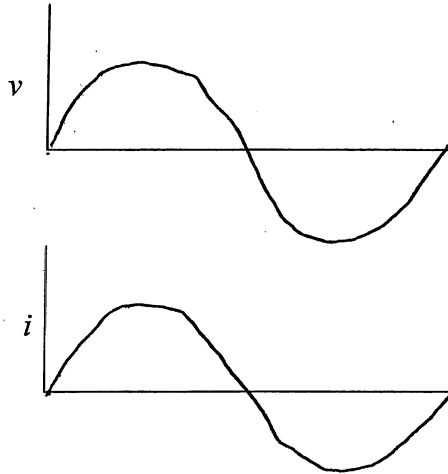
$$= \frac{\varepsilon_0}{R} \sin^2 \omega t$$



averaged over a cycle. $\langle P \rangle = \frac{\varepsilon_0^2}{2R} = \frac{i_0 \varepsilon_0}{2} = \frac{i_0^2 R}{2}$ and the power loss is as if R was connected to a battery who $\varepsilon = \frac{\varepsilon_0}{\sqrt{2}}$. In this sense one talks of $\frac{\varepsilon_0}{\sqrt{2}}$ and $\frac{i_0}{\sqrt{2}}$ as root-mean-square or r.m.s. voltage and current.

II. Generator and Capacitor

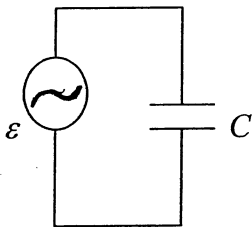

now $q=Cv$


so charge and voltage in phase.

$$v = \varepsilon_0 \sin \omega t$$

$$q = \varepsilon_0 \sin \omega t$$

$$i = \frac{\Delta q}{\Delta t} = + \varepsilon_0 C \omega \cos \omega t$$

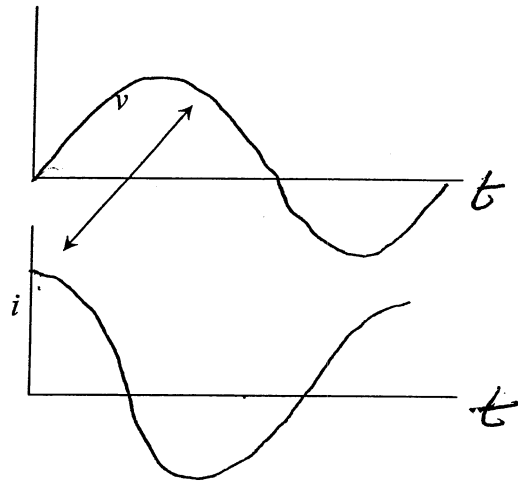i and v are not in phase i leads v by $\pi/2$



$\frac{1}{\omega C}$ has dimensions of R and we define capacitive reactance

$$X_c = \frac{1}{\omega C}$$


$$i = \frac{\varepsilon_0}{X_c} \cos \omega t$$

Now $P(t) = \frac{\varepsilon_0^2}{X_c} \sin \omega t \cos \omega t$

Average $\langle P \rangle = 0$

No power loss on average.

III.

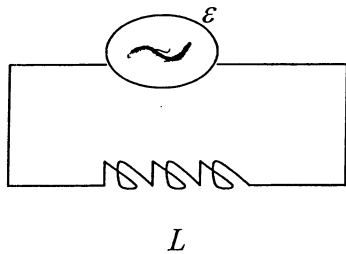


Now voltage in phase with slope of i vs t curve.

If $i = i_0 \sin \omega t$

$$\varepsilon - \frac{L \Delta i}{\Delta t} = 0$$


$$v_L = \frac{L \Delta i}{\Delta t}$$

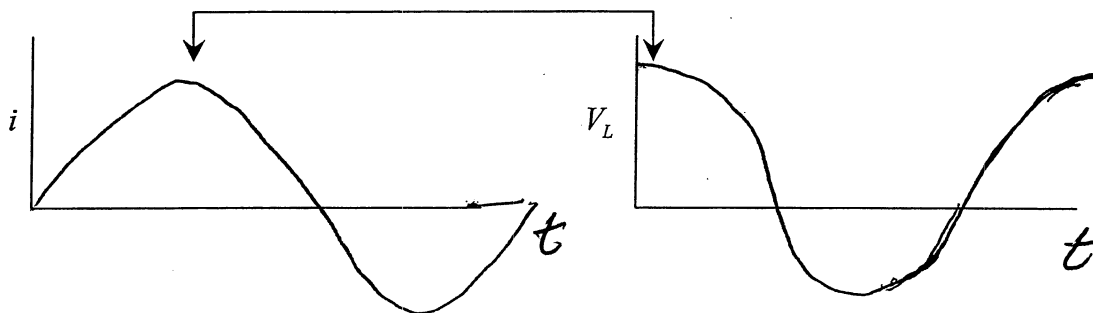$v_L = i_0 \omega L \cos \omega t$ and now voltage leads current by $\frac{\pi}{2}$



Again $X_L = \omega L$
and $\langle P \rangle = 0$


IV. Generator with all three.

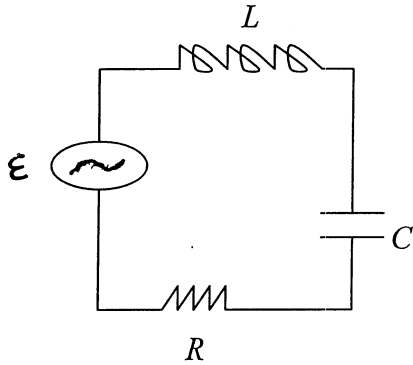




To work out behavior of L-C-R circuit we have to keep track of the relative phases in R , C , and L .

We introduce the concept of a Phasor. We have a series loop so current has to be same at all points. We begin with the current and build the voltage vector.

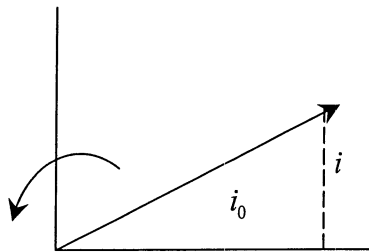Take $i = i_0 \sin \omega t$ and represent it by current Phasor: vector of magnitude i_0 rotating at angular velocity ω , i.e.




Concentrate on $t=0$

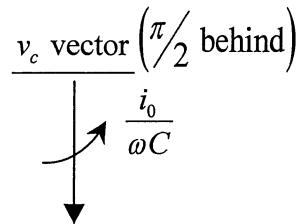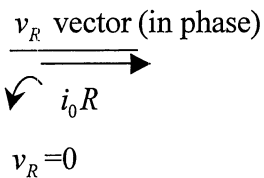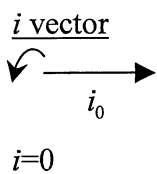


$v_c \text{ max}^m - \text{ive}$

v_L vector $\left(\frac{\pi}{2}$ ahead

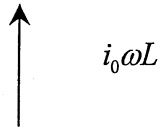

v_L max + ive

Total voltage vector

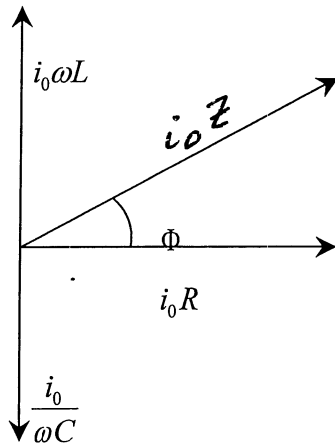

$$\varepsilon_0 = v_0 = i_0 \left[R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2 \right]^{1/2}$$

$$\tan \Phi = \frac{\omega L - \frac{1}{\omega C}}{R}$$

$$i = i_0 \sin \omega t$$

$$v = \varepsilon_0 \sin(\omega t + \Phi)$$

Power in Circuit

$$P = iv = i_0 \varepsilon_0 \sin \omega t \sin(\omega t + \Phi)$$

$$= i_0 \varepsilon_0 \left[\sin^2 \omega t \cos \Phi + \sin \omega t \cos \omega t \sin \Phi \right]$$

$$\langle P \rangle = \frac{i_0 \varepsilon_0}{2} \cos \Phi$$

This is the concept of Power factor $\cos \Phi$

Next, Define Impedance

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}$$

$$\text{then } i_0 = \frac{\varepsilon_0}{Z} \text{ \& } \cos \Phi = \frac{R}{Z}$$

$$\text{so } \langle P \rangle = \frac{\varepsilon_0^2}{2Z} \cos \Phi = \frac{\varepsilon_0^2}{2R} \cos^2 \Phi$$


RESONANCE If generator frequency can be varied $i_0 = \frac{\varepsilon_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$

Gives $i_0 \rightarrow 0$ when $\omega \rightarrow 0$ b/c $\frac{1}{\omega C} \rightarrow \infty$ [capacitor cuts off i_0]


$i_0 \rightarrow 0$ when $\omega \rightarrow \infty$ b/c $\omega L \rightarrow \infty$ [Inductor cuts off i_0]

i_0 is max^m when $\omega L = \frac{1}{\omega C}$

This is the phenomenon of Resonance

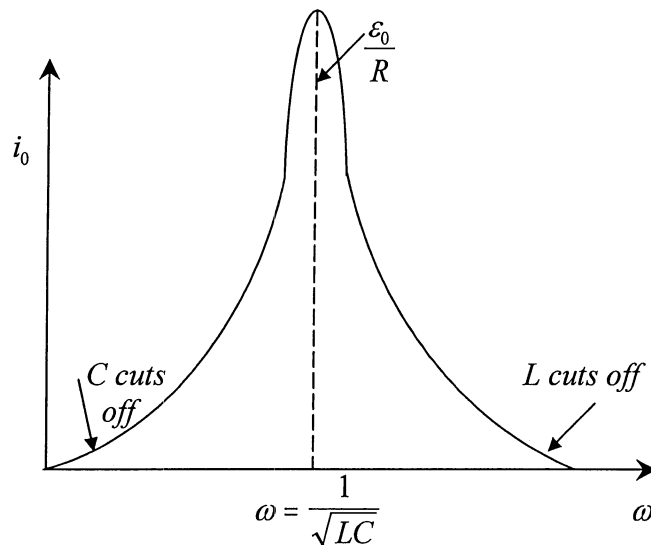

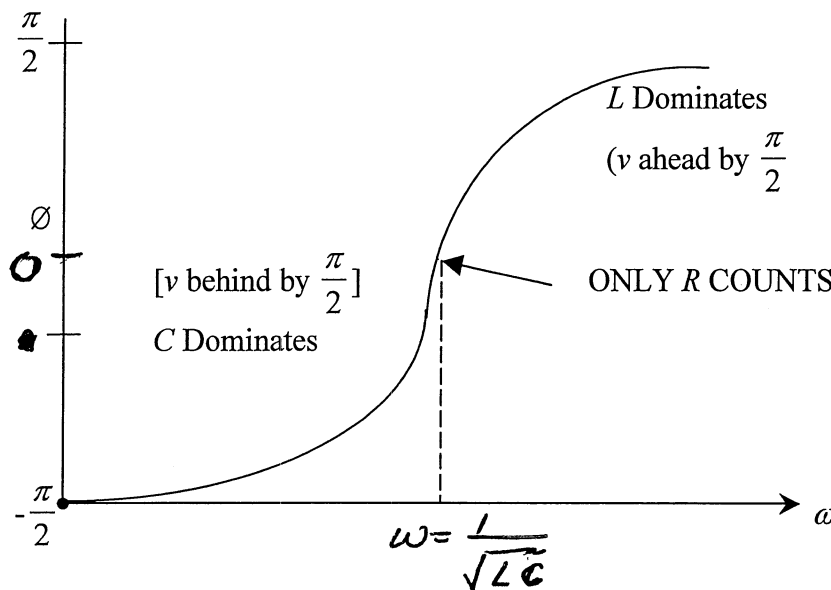The phase difference ϕ is also a function of frequency



[v and i
in phase
R gets
max^m
power
hence
"RESONANCE"]

11 / 11

$$\omega = \frac{1}{\sqrt{LC}}$$

Note: Resonance occurs when Generator frequency ω is equal to natural frequency of LC

Circuit $\omega_0 = \frac{1}{\sqrt{LC}}$
