

Devices: L-R CIRCUIT

We already know that a

Resistor: represents that it costs energy to transport charge through a conductor. Establish a current i , a voltage drop v appears across R such that


$$R = \frac{v}{i}$$

Faraday's discoveries allow us to define a new device:

Inductor: (L) i causes \vec{B}

$$\frac{\Delta i}{\Delta t} \text{ causes } \frac{\Delta \vec{B}}{\Delta t} \text{ causes } \frac{\Delta \Phi_B}{\Delta t} \text{ causes } (-\epsilon)$$

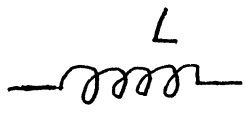L is defined by $L = \frac{-\epsilon}{(\Delta i / \Delta t)}$




And we showed in class that the self Inductance of a solenoid is $L = \mu_0 n^2 V$, where

n = # of turns per meter
 V = volume of solenoid

Now we want to study what happens when we connect our 3-devices, Battery, R and L in the circuit shown.

At $t=0$, put the switch as shown (1 \rightarrow 2). The battery immediately wants to set up a current.

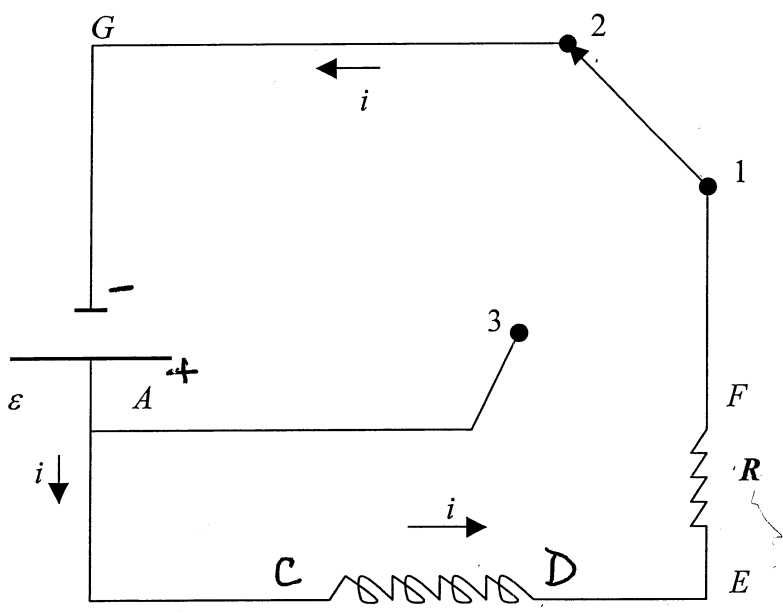
However, L immediately objects by setting up a "back" emf , which will oppose ϵ , $\epsilon_B = -L \left(\frac{\Delta i}{\Delta t} \right)_0$



* The "minus" sign in the equation ensures that an Inductor always opposes any change in current through it.


Thus it will take time for the current to grow.

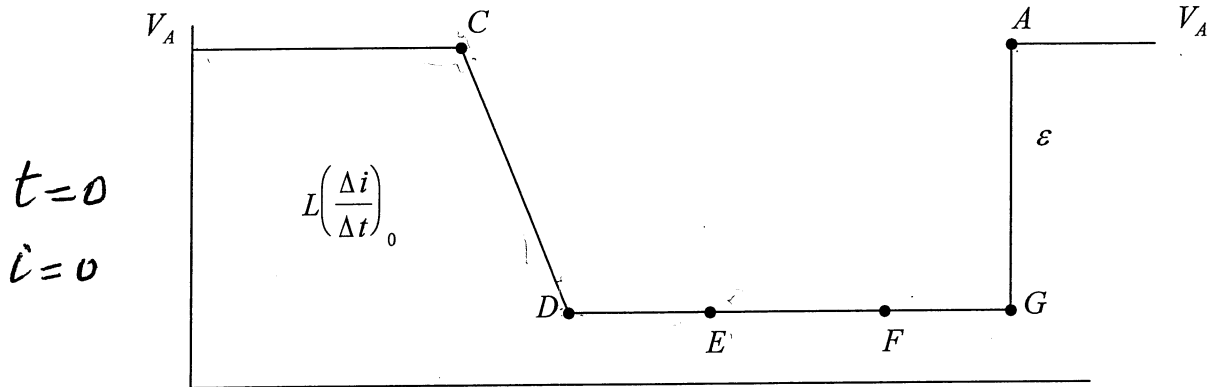Step 1 at $t=0$, $i=0$, No potential drop across R . As a function of position on the circuit the potential values are



$$\varepsilon - L \left(\frac{\Delta i}{\Delta t} \right)_0 = 0$$

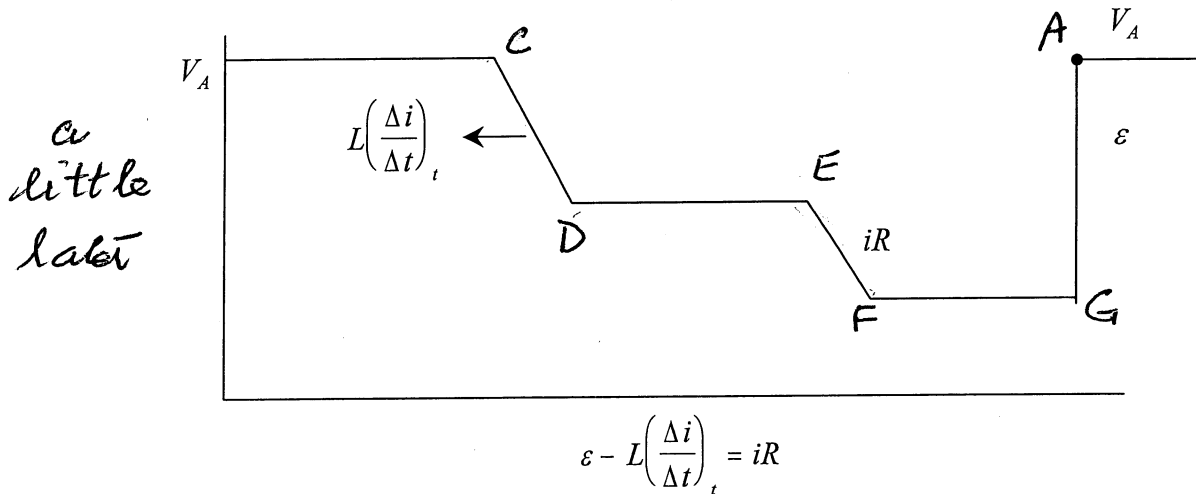
Step 2 A little time later i has grown some so now $v_R = iR$ and the potentials become



$$\varepsilon - L \left(\frac{\Delta i}{\Delta t} \right)_t = iR$$

Clearly, $\left(\frac{\Delta i}{\Delta t} \right)_t < \left(\frac{\Delta i}{\Delta t} \right)_0$ Rate of growth has slowed down.

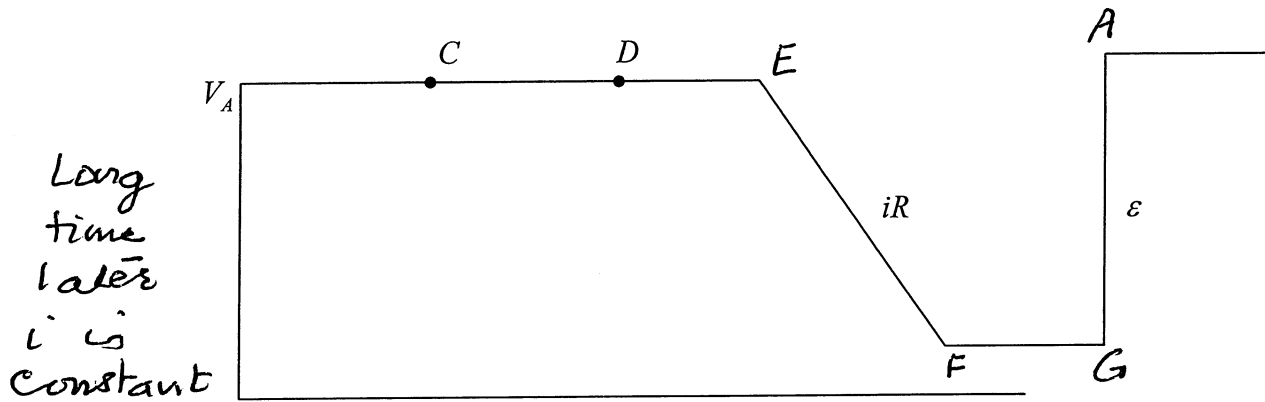Step 3 A long time later i has grown to its full value, i stops changing with time, $\frac{\Delta i}{\Delta t} \rightarrow 0$ so no more back emf from L . Potential variation looks like.



$$i(t \rightarrow \infty) = \frac{\epsilon}{R}$$

Note:



$$V_L = \epsilon_B \text{ is } \epsilon \text{ at } t=0, i=0$$

$$V_L = \epsilon_B \text{ is } 0 \text{ at } t \rightarrow \infty, i = \frac{\epsilon}{R}$$

The time variations are controlled by the characteristic time

$$\tau = \frac{L}{R} \text{ (verify that this has dimensions of time)}$$

and look like

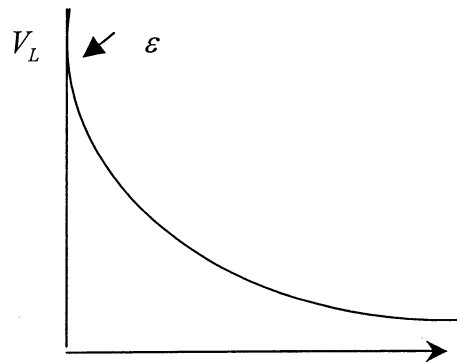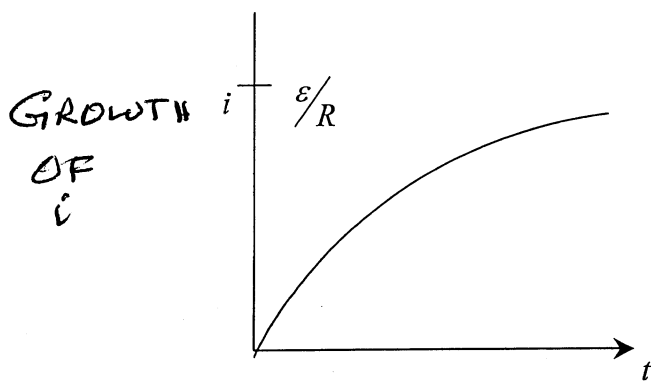


$$i = \frac{\epsilon}{R} [1 - e^{-Rt/L}]$$

$$V_R = iR = \epsilon [1 - e^{-Rt/L}]$$

$$V_L = \epsilon e^{-Rt/L}$$

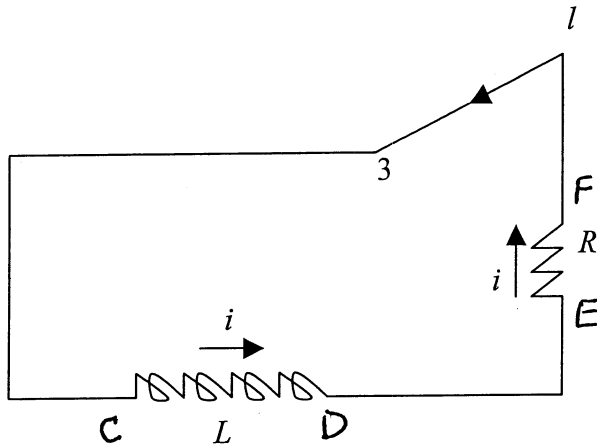After this long time $i = \frac{\varepsilon}{R}$ and a magnetic field has been established in L and stores $\frac{B^2}{2\mu_0}$ of energy per m^3 . So now if we move the switch so $1 \rightarrow 3$ the circuit becomes



No Battery in Circuit. Magnetic Energy stored in L is source of Current!


Let us start the clock again:

Step 1 $t=0$, $i = \frac{\varepsilon}{R}$ and the inductor wants to keep i going. Since $\frac{\Delta i}{\Delta t}$ is now -ive, V_L will be +ive and immediately jump to ε .

Step 2 As stored energy in L becomes smaller $\left| \frac{\Delta i}{\Delta t} \right|$ reduces with time.

Step 3 Long time later, all of the stored energy has been used up: $\frac{\Delta i}{\Delta t} \rightarrow 0$, $i \rightarrow 0$.

The time variations are

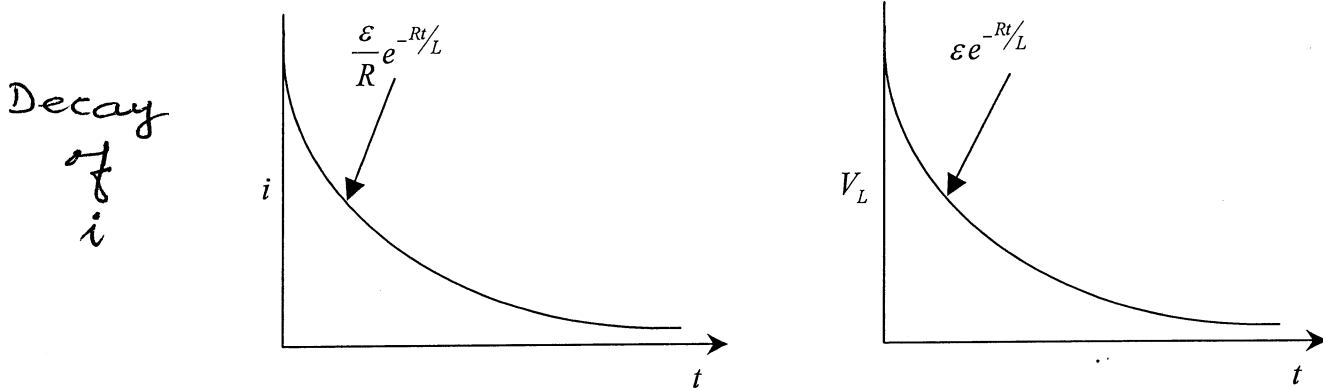

To Summarize:

- i) L keeps $i=0$ when switch first closed
- ii) $V_L \rightarrow 0$ as $t \rightarrow \infty$
- iii) in an L - R circuit potential precedes current.

QUESTION: Why does τ depend on both L and R ?

Exponential functions.

