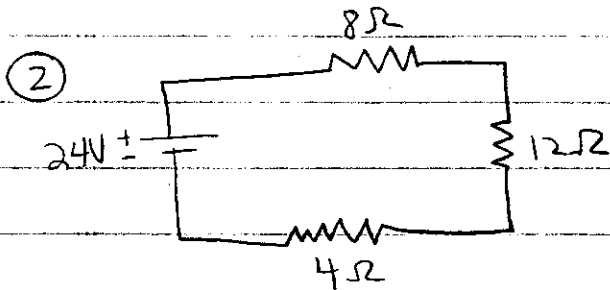


HW#4 - SOL^N - ADAM COHEN

①

Chapter 18 - DC circuits



* in series $\Rightarrow R_{eq} = R_1 + R_2 + R_3$
 $R_{eq} = 24 \Omega$

* each resistor has the same current I

$$I = \frac{DV}{R_{eq}} = \frac{24V}{24\Omega} = 1A$$

* in parallel $\Rightarrow R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \right)^{-1}$

$$= \left(\frac{1}{4} + \frac{1}{8} + \frac{1}{12} \right)^{-1} \Omega$$
$$= 2.18 \Omega$$


* each resistor has the same voltage DV

$$\Rightarrow I_4 = \frac{DV}{R_4} = \frac{24}{4} A = 6A$$

$$I_8 = \frac{24}{8} A = 3A$$

$$I_{12} = \frac{24}{12} A = 2A$$



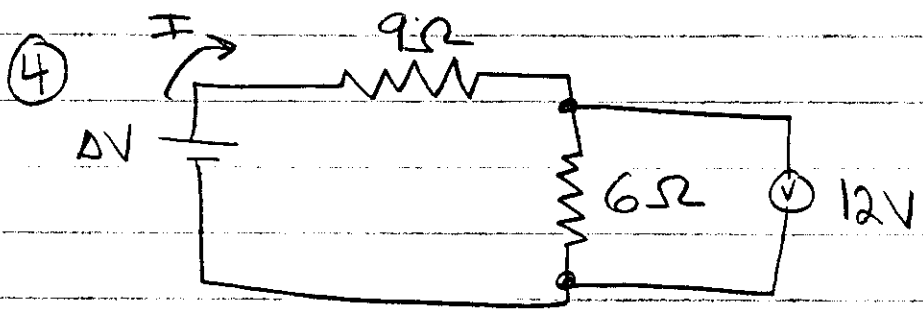

* in series each resistor has the same current.


$$\Rightarrow I_9 = I_6 = \frac{\Delta V_6}{R_6} = \frac{12}{6} A = 2A$$

$$\Rightarrow I_9 = 2A = \frac{\Delta V_9}{R_9} = \frac{\Delta V_9}{9\Omega}$$

so $\Delta V_9 = 18V$

* the loop rule says:
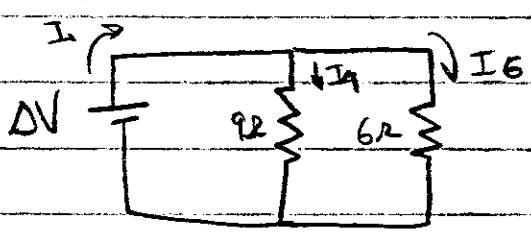
$$\begin{aligned} \Delta V_{total} &= \Delta V_6 + \Delta V_9 \\ &= 12V + 18V \\ &= \boxed{30V} \end{aligned}$$




$I_9 = 0.25A$
(measured)

* in parallel, each resistor has same potential difference

$$\Rightarrow \Delta V = I R = (0.25A)(9A) = 2.3V$$

This the the ΔV of the power supply.

3

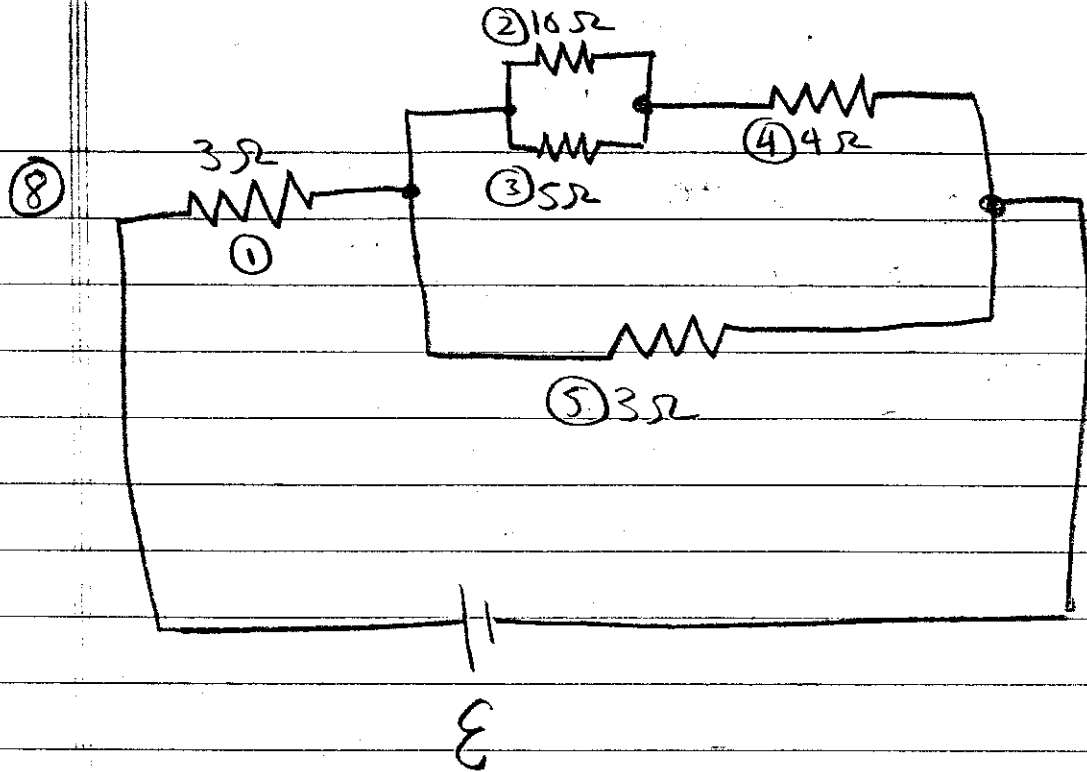

• Combine $10\ \Omega$ and $5\ \Omega$ resistor:

$$R_{23} = \left(\frac{1}{10\ \Omega} + \frac{1}{5\ \Omega} \right)^{-1} = \frac{10}{3}\ \Omega$$

• combine R_{23} and R_4 :

$$R_{234} = R_{23} + R_4 = \left(\frac{10}{3} + \frac{10}{3} \right) \Omega = \frac{20}{3}\ \Omega$$

• combine R_{234} and R_5 :

$$R_{2345} = \left(\frac{1}{R_{234}} + \frac{1}{R_5} \right)^{-1} = \left(\frac{3}{20} + \frac{1}{3} \right)^{-1} \Omega$$

$$= \left(\frac{9}{66} + \frac{22}{66} \right)^{-1} = \left(\frac{31}{66} \right)^{-1} = \frac{66}{31}\ \Omega$$

• combine R_{2345} and R_1 :

$$R_{12345} = \left(\frac{66}{31} + 3 \right) \Omega = 5.13\ \Omega$$


power can be written as:

$$P = \frac{\Delta V^2}{R} \Rightarrow \Delta V = \sqrt{PR}$$

$$= \sqrt{(4W)(5.13\Omega)}$$

$$\Delta V = 4.53V$$

16

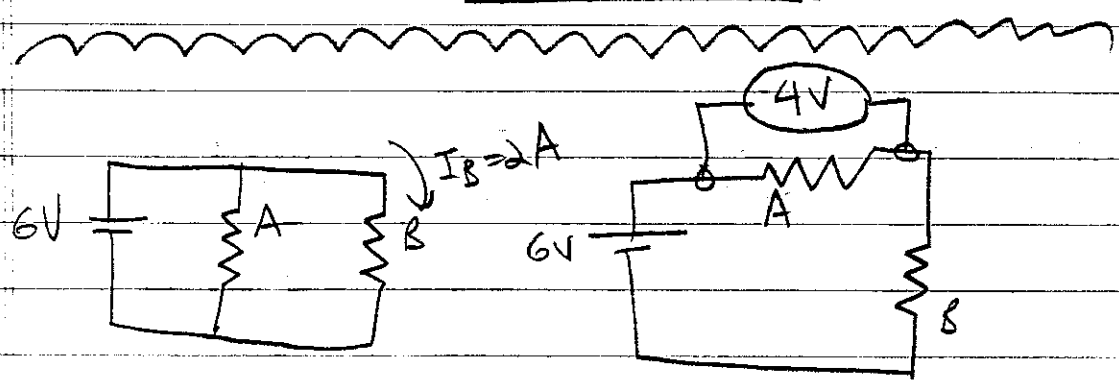

• In parallel, $\Delta V_A = \Delta V_B = 6V$

so

$$R_B = \frac{\Delta V}{I} = \frac{6V}{2A} = \boxed{3\Omega = R_B}$$

• In series:

$$\Delta V_{total} = \Delta V_A + \Delta V_B$$

$$6V = 4V + \Delta V_B$$

$$\Rightarrow \Delta V_B = 2V$$

also, $I_A = I_B \Rightarrow I_B = \frac{\Delta V_B}{R_B} = \frac{2V}{3\Omega} = \frac{2}{3}A$

so

$$I_A = \frac{2}{3}A = \frac{\Delta V_A}{R_A} = \frac{4V}{R_A}$$

$$\Rightarrow \boxed{R_A = 6\Omega}$$

30

$$\tau = RC$$

$$= [\Omega][F]$$

Ohm's Law

$$\Delta V = IR$$

$$\Rightarrow R = \frac{\Delta V}{I} = \frac{[V]}{[A]}$$

Def'n

$$C \equiv \frac{Q}{\Delta V} = \frac{[C]}{[V]}$$

so

$$\tau = \left[\frac{V}{A} \right] \left[\frac{C}{V} \right] = \left[\frac{C}{A} \right]$$


and

$$I = \frac{Q}{\Delta t} = \frac{[C]}{[s]} = [A]$$

so

$$\tau = \frac{[C]}{[C]/[s]} = [s]$$

32

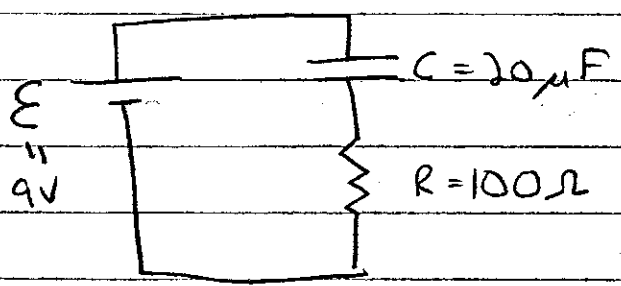

time constant

$$\tau = RC = (100 \Omega)(20 \times 10^{-6} F)$$

$$= 2 \times 10^{-3} s$$

$$\tau = 2 \text{ ms}$$

max charge

$$Q_{max} = CE \quad (\text{recall: } C \equiv \frac{Q}{\Delta V})$$

$$= (20 \mu F)(9V) = 180 \mu C$$

5

6

Charge on a capacitor:

$$q = Q_{\max} (1 - e^{-t/\tau})$$


at $t = \tau$,

$$q = [180 \mu\text{C}] (1 - e^{-1})$$

$\leftarrow \frac{1}{e} \approx 0.718 \dots$

$$q(\tau) = 114 \mu\text{C}$$

38

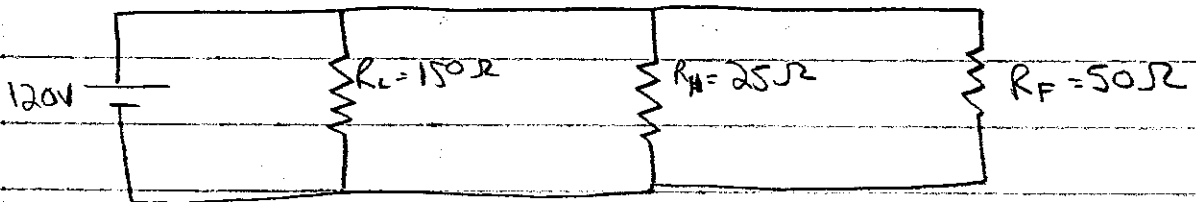

The equivalent resistance (parallel)

$$R_{eq} = \left(\frac{1}{150} + \frac{1}{25} + \frac{1}{50} \right)^{-1} = 15 \Omega$$

By Ohm's Law,

$$\Delta V = IR \Rightarrow I = \frac{\Delta V}{R} = \frac{120V}{15\Omega} = 8A$$

Since in parallel $\Delta V = \Delta V_F = \Delta V_H = \Delta V_L = 120V$

Current varies (must be split), so

$$I_L = \frac{\Delta V_L}{R_L} = \frac{120V}{150\Omega} = 0.8A$$

so, $\Delta V_H = 120V$

$$P_H = \frac{(\Delta V_H)^2}{R_H} = \frac{(120V)^2}{25\Omega} = \boxed{576W}$$

40) The maximum current to our line is:

$$P_{max} = \Delta V I_{max} = (120V)(15A) = 1800W.$$


(If we draw more than 15A, the circuit breaks.)

The power needed by the two appliances is 2400W.

$\Rightarrow P_{needed} > P_{max}$

So we can't operate both at the same time.

44

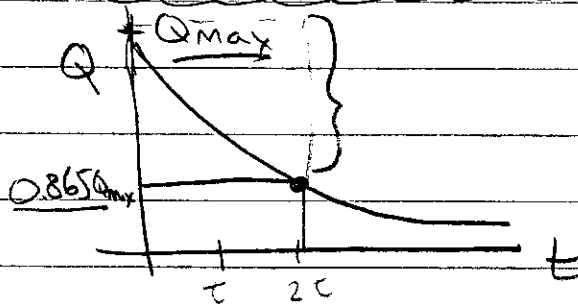

$$Q = Q_{max}(1 - e^{-t/\tau})$$


$$\text{ratio: } \frac{Q(2\tau)}{Q_{max}} = \frac{Q_{max}(1 - e^{-2\tau/\tau})}{Q_{max}}$$

$$= 1 - e^{-2} = 1 - \frac{1}{e^2} = \boxed{86.5\%}$$

(7)


(8)

46

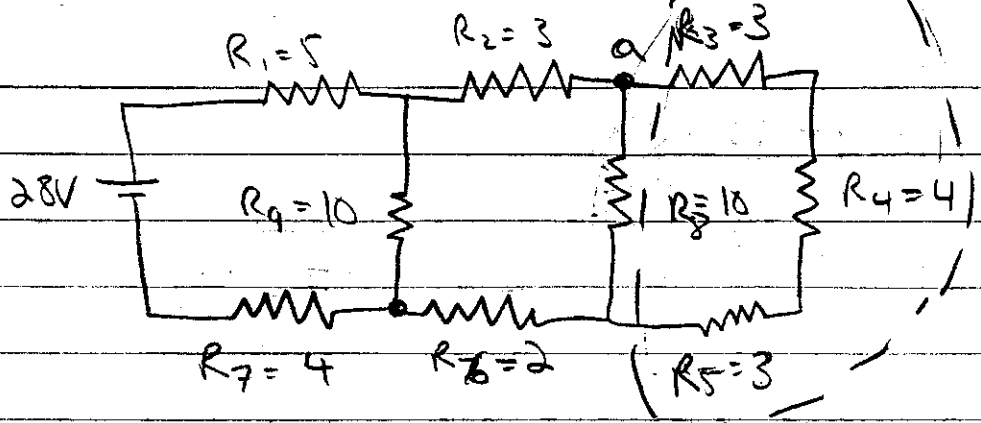


• R_3, R_4, R_5 are in series
 $\Rightarrow R_{345} = 3\Omega + 4\Omega + 3\Omega = 10\Omega$

• redraw :

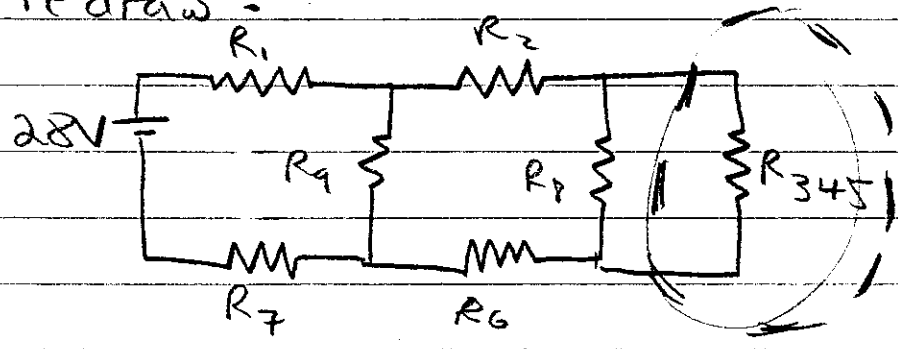

• R_8 and R_{345} are in parallel :
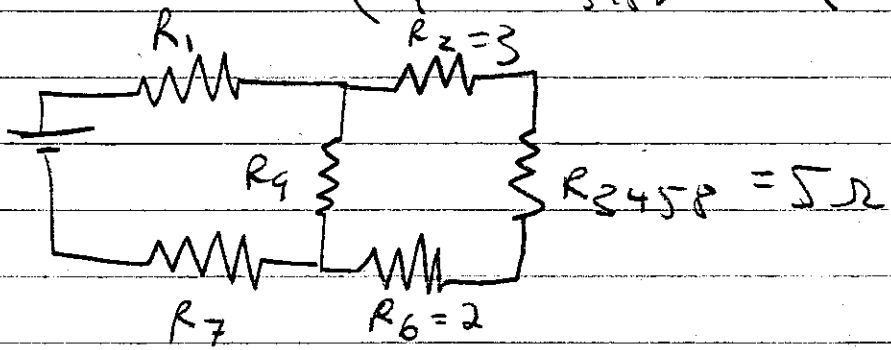
$$\Rightarrow R_{3458} = \left(\frac{1}{R_8} + \frac{1}{R_{345}} \right)^{-1} = \left(\frac{1}{10} + \frac{1}{10} \right)^{-1} = 5\Omega$$




• R_2, R_6, R_{3458} are in series, so

$$R_{234568} = 10\Omega$$


Cont →

9

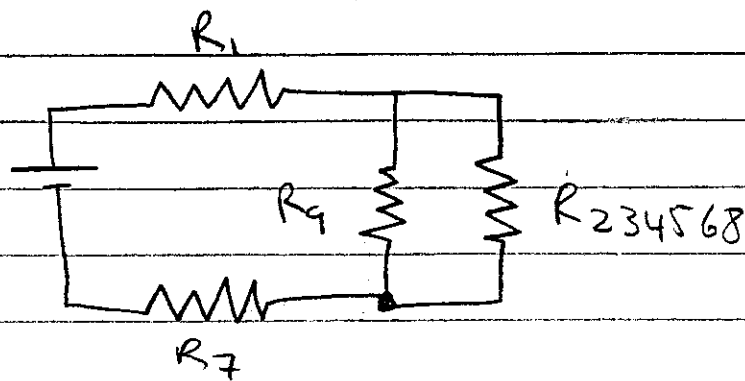

• R_9, R_{234568} are in parallel
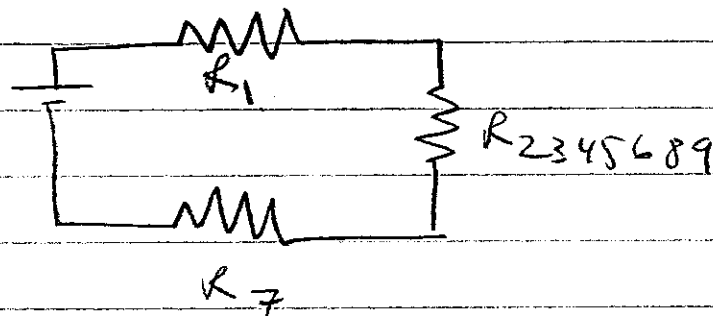
$$R_{2345689} = \left(\frac{1}{R_9} + \frac{1}{R_{234568}} \right)^{-1} = 5 \Omega$$



• the rest are in series, so

$$R_{eq} = 5 \Omega + 5 \Omega + 4 \Omega = \boxed{14 \Omega}$$

• Power = $P = \frac{\Delta V^2}{R_{eq}} = \frac{(28V)^2}{14 \Omega} = \boxed{56 W}$

• The 5Ω resistor "sees" all the current before it's split at a junction.

So $I_3 = \frac{\Delta V}{R_{eq}} = \frac{28V}{14 \Omega} = \boxed{2 A}$