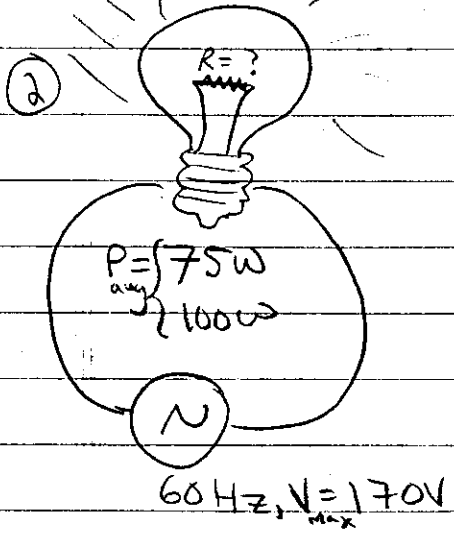


HW#7 - SOL^N - ADAM COHEN

Chapter 21 - AC Circuits & EM waves



$$P_{avg} = I_{rms}^2 R$$

$$= \left(\frac{I_{max}}{\sqrt{2}} \right)^2 R, \text{ since } I_{rms} = \frac{I_{max}}{\sqrt{2}}$$

$$= \frac{1}{2} I_{max}^2 R$$

$$= \frac{1}{2} \left(\frac{\Delta V_{max}}{R} \right)^2 R, \text{ by Ohm's Law } \Delta V = IR$$

$$P_{avg} = \frac{1}{2} \frac{\Delta V_{max}^2}{R}$$

⇒ by rearranging

$$R = \frac{\Delta V_{max}^2}{2 P_{avg}}$$

$$\text{If } P_{avg} = 75W \Rightarrow R = \frac{(170V)^2}{2(75W)} = \boxed{193\Omega}$$


$$P_{avg} = 100W \Rightarrow R = \frac{(170V)^2}{2(100W)} = \boxed{145\Omega}$$

(2)

(4)

$$\Delta V_{rms} = 120V,$$

$$f = 60Hz$$

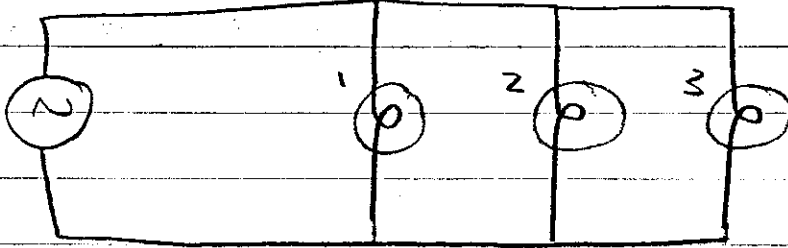

$$P_{avg} = 150W, 150W, 100W$$

- in parallel $\Rightarrow \Delta V_{rms} = \Delta V_1 = \Delta V_2 = \Delta V_3$
- by defⁿ of power, $P_{avg} = I_{rms} \Delta V_{rms}$

$$\Rightarrow I_{rms} = \frac{P_{avg}}{\Delta V_{rms}}$$

- by Ohm's Law, $\Delta V_{rms} = I_{rms} R$

$$\Rightarrow R = \frac{\Delta V_{rms}}{I_{rms}}$$

$$I_1 = \frac{150}{120} A = 1.25 A$$

$$R_1 = \frac{120}{1.25} \Omega = 96 \Omega$$

$$I_2 = \frac{150}{120} A = 1.25 A$$

$$R_2 = " " = 96 \Omega$$

$$I_3 = \frac{100}{120} A = 0.833 A$$

$$R_3 = \frac{120}{0.833} \Omega = 144 \Omega$$

3

⑦ $X_c = \frac{1}{2\pi f C}$ (don't care about prefactor $\frac{1}{2\pi}$)

$f = [Hz] = \frac{1}{[s]}$

$C = [F] = \frac{q}{\Delta V} = \frac{[C]}{[V]}$

so $X_c = \frac{1}{\left(\frac{1}{[s]} \cdot \frac{[C]}{[V]}\right)} = \frac{[V]}{[C]/[s]}$

recall: $I = \frac{q}{\Delta t} = \frac{[C]}{[s]} = [A]$

so $X_c = \frac{[V]}{[A]}$

recall, Ohm's Law: $\Delta V = IR \Rightarrow R = \frac{\Delta V}{I} = \frac{[V]}{[A]} = [\Omega]$

$\Rightarrow X_c = [\Omega] \quad \checkmark$


⑫ $\begin{cases} \omega = 120\pi \text{ rad/s} = 2\pi f \\ \Delta V_{\max} = 140 \text{ V} \\ L = 0.1 \text{ H} \end{cases} \Rightarrow I_{\text{rms}} = ?$

$\sqrt{2} \cdot \left\{ \Delta V_{\text{rms}} = I_{\text{rms}} X_L = I_{\text{rms}} (2\pi f L) \right\} \cdot \sqrt{2}$

$\Delta V_{\max} = \sqrt{2} \cdot I_{\text{rms}} (2\pi f) L = \sqrt{2} I_{\text{rms}} \omega L$

$\Rightarrow I_{\text{rms}} = \frac{\Delta V_{\max}}{\sqrt{2} \omega L} = \frac{140}{\sqrt{2} (120\pi) (0.1)} = \boxed{2.63 \text{ A}}$

(4)

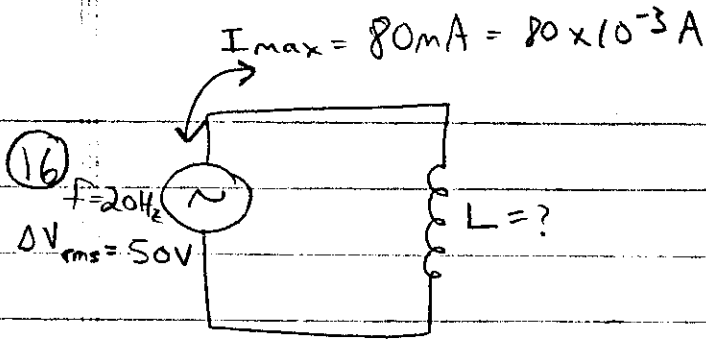

$$\bullet I_{\text{rms}} = \frac{I_{\max}}{\sqrt{2}} = \frac{80 \times 10^{-3}\text{A}}{\sqrt{2}} = 0.056\text{A}$$


$$\bullet \Delta V_{\text{rms}} = I_{\text{rms}} X_L \equiv I_{\text{rms}} 2\pi f L$$

$$\Rightarrow L = \frac{\Delta V_{\text{rms}}}{2\pi f \cdot I_{\text{rms}}} = \frac{50\text{V}}{2\pi (20\text{Hz}) (0.056\text{A})}$$

$$L = 7.03\text{H}$$

This is the minimum inductance to have
at most $80\text{mA} = I_{\max}$.

(5)

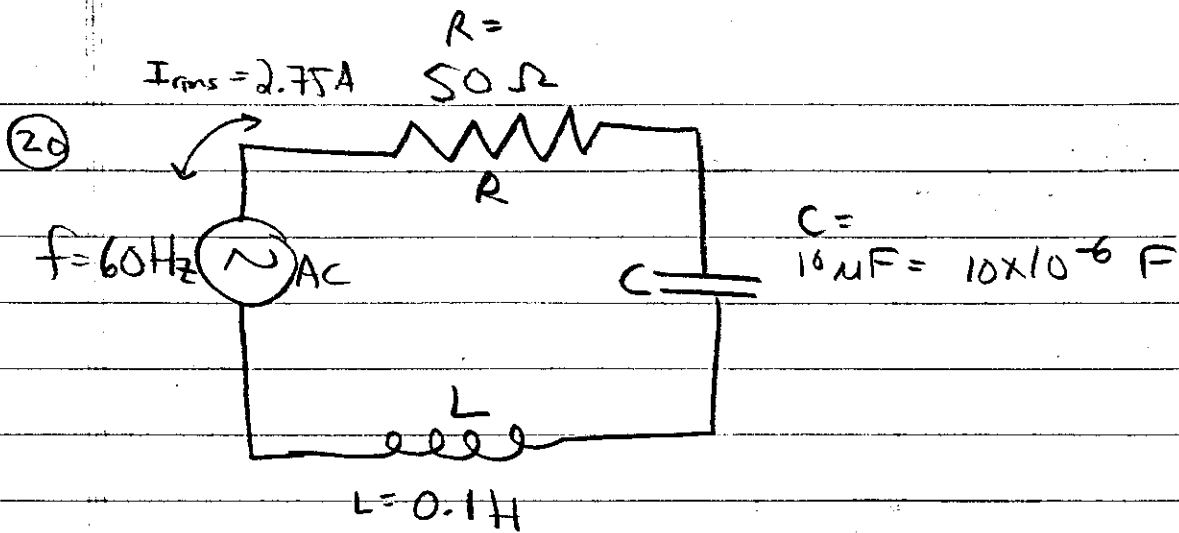

• inductive reactance $X_L = 2\pi fL$

$$= 2\pi (60)(0.1) \Omega$$

$$= 37.7 \Omega$$

• capacitive reactance $X_C = \frac{1}{2\pi fC}$

$$= \frac{1}{2\pi (60)(10 \times 10^{-6})} \Omega$$

$$= 265 \Omega$$

• impedance $Z = \sqrt{R^2 + (X_L - X_C)^2}$

$$= \sqrt{50^2 + (37.7 - 265)^2} \Omega$$

$$= 233 \Omega$$

• potential difference across R

$$\Delta V_R = I_{rms} R = \boxed{13.8 \text{ V}}$$

" " C

$$\Delta V_C = I_{rms} X_C = \boxed{72.9 \text{ V}}$$

" " L


$$\Delta V_L = I_{rms} X_L = \boxed{104 \text{ V}}$$

• potential difference across RLC :

$$\Delta V_{RLC} = I_{rms} Z = \boxed{641 \text{ V}}$$

24
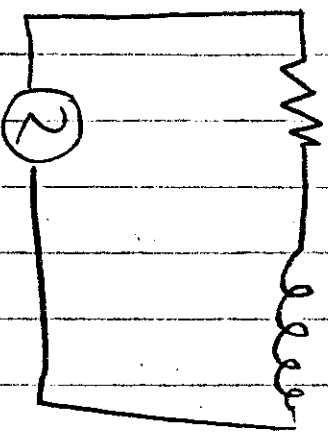
$$\begin{cases} f = 60 \text{ Hz} \\ \Delta V_{\text{max}} = 170 \text{ V} \end{cases}$$



$$R = 1.2 \text{ k}\Omega = 1.2 \times 10^3 \Omega = 1200 \Omega$$

$$L = 2.8 \text{ H}$$

$$X_L = 2\pi fL = 1056 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = 1598 \Omega$$


$$\Rightarrow I_{\text{max}} = \frac{\Delta V_{\text{max}}}{Z} = \frac{170 \text{ V}}{1.6 \times 10^3 \Omega} = \boxed{0.106 \text{ A}} \quad (a)$$

$$\Delta V_R = I_{\text{max}} R = \boxed{128 \text{ V}} \quad (b)$$

$$\Delta V_L = I_{\text{max}} X_L = \boxed{1112 \text{ V}}$$

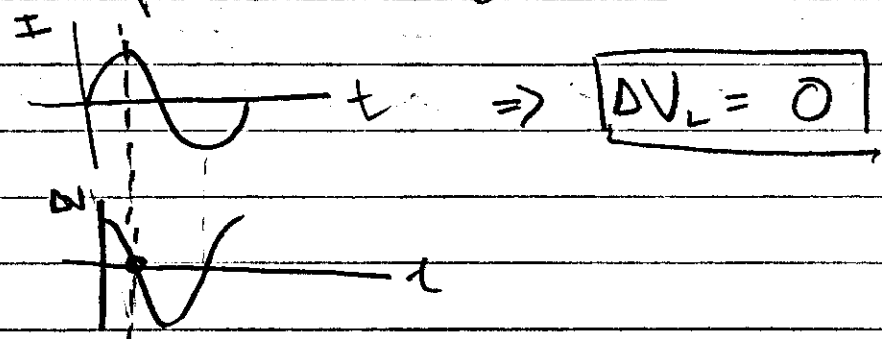c) if $I = I_{\text{max}}$ $\Rightarrow \Delta V_R = I_{\text{max}} R$
 $\Delta V_R = \boxed{128 \text{ V}}$

FACT: the instantaneous voltage across an inductor is always 90° out of phase with current:



at $I = I_{max}$, the instantaneous rate of change of I , $\frac{\Delta I}{\Delta t} = 0$, so

$$\Delta V_L = -L \frac{\Delta I}{\Delta t} = -L(0) = 0.]$$

by loop rule, $\Delta V_{closed\ path} = 0$

$$\Rightarrow \Delta V_{source} + \Delta V_R + \cancel{\Delta V_L} = 0$$

$$\Rightarrow \Delta V_{source} = -\Delta V_R$$

$$\boxed{\Delta V_{source} = -12\text{ V}}$$


d) when $I = 0$, $\Delta V_R = (0)R = \boxed{0\text{ V}}$

- depending on if the rate of change of I is positive or negative:

$$\Delta V_L = \pm 110\text{ V}$$

$$\Rightarrow \boxed{|\Delta V_L| = 112\text{ V}}$$


by loop rule $\boxed{|\Delta V_{source}| = 112\text{ V}}$

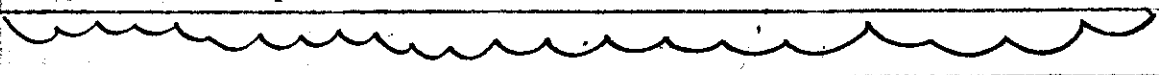

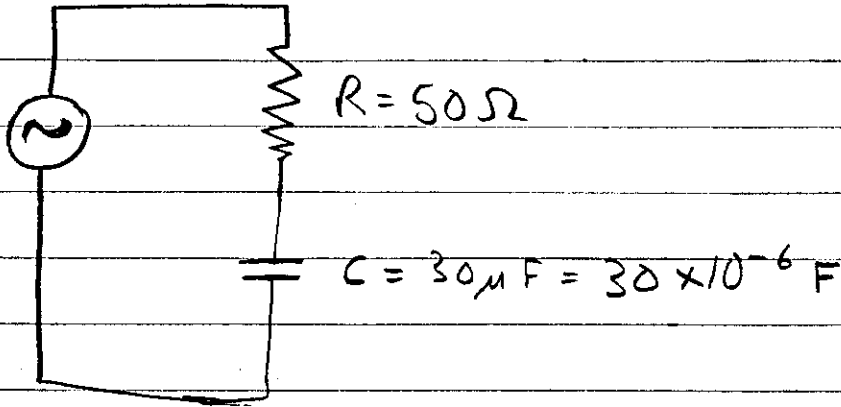(28)

$$f = 60 \text{ Hz}$$

$$\Delta V_{\text{rms}} = 100 \text{ V}$$



$$\begin{cases} R = 50 \Omega \\ X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(60)(30 \times 10^{-6})} \Omega = 88.4 \Omega \\ X_L = 0 \end{cases}$$

$$\Rightarrow \text{phase } \phi = \arctan\left(\frac{X_L - X_C}{R}\right) = \arctan\left(\frac{-88.4}{50}\right)$$

$$= -60.5^\circ$$

$$\Rightarrow \text{power factor } \cos \phi = \boxed{0.492}$$

$$\bullet \text{ impedance: } Z = \sqrt{R^2 + X_C^2} = 102 \Omega$$

$$\Rightarrow I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{Z} = 0.984 \text{ A}$$

$$\text{so } P_{\text{avg}} = I_{\text{rms}} \Delta V_{\text{rms}} \cos \phi$$

$$= (0.984 \text{ A})(100 \text{ V})(0.492)$$

$$= \boxed{48.5 \text{ W}}$$

if, instead $X_C = 0$

$$X_L \equiv 2\pi fL = 2\pi(60)(0.3) \Omega = 113 \Omega$$

$$\Rightarrow Z = \sqrt{R^2 + X_L^2} = 124 \Omega$$

$$I_{rms} = \frac{\Delta V_{rms}}{Z} = 0.809 A$$

$$\phi = \arctan\left(\frac{X_L}{R}\right) = 66.1^\circ$$

$$\text{power factor} = \cos \phi = \boxed{0.404}$$

$$\text{and } P_{avg} = I_{rms} \Delta V_{rms} \cos \phi = \boxed{32.7 W}$$

33) resonance frequency $f_0 = \frac{1}{2\pi\sqrt{LC}}$

Solve for L: $2\pi f_0 = \frac{1}{\sqrt{LC}}$

$$\frac{1}{2\pi f_0} = \sqrt{LC}$$

$$\frac{1}{4\pi^2 f_0^2} = LC$$


$$L = \frac{1}{4\pi^2 f_0^2} C$$

plug in: $f_0 = 88.9 \text{ MHz} = 88.9 \times 10^6 \text{ Hz}$

$C = 1.4 \text{ pF} = 1.4 \times 10^{-12} \text{ F}$

$$\Rightarrow L = 2.29 \times 10^{-6} \text{ H} = \boxed{2.29 \mu\text{H}}$$

38

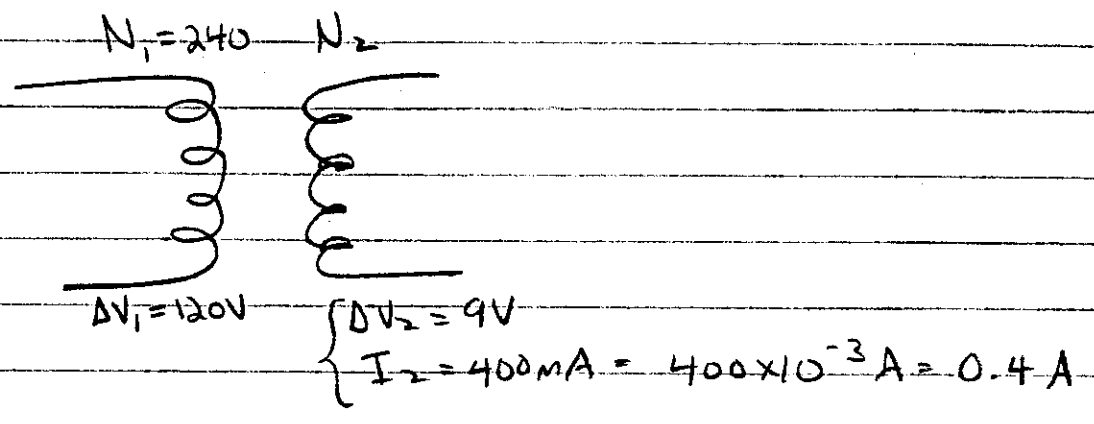

for the transformer: $\Delta V_2 = \frac{N_2}{N_1} \Delta V_1$

$$\Rightarrow N_2 = \frac{N_1 \Delta V_2}{\Delta V_1} = \frac{(240)(9V)}{(120V)} = \boxed{18 \text{ turns}}$$

for an ideal transformer

$$P_{in} = P_{out} = \Delta V_2 I_2 = (9V)(0.4A)$$

$$\text{Power} = \boxed{3.6W}$$

(45) $\left\{ \begin{aligned} \lambda_{red} &= 660 \text{ nm} = 660 \times 10^{-9} \text{ m} \\ \lambda_{IR} &= 940 \text{ nm} = 940 \times 10^{-9} \text{ m} \end{aligned} \right.$

for EM wave $c = f\lambda$ where $c = \text{speed of light} = 3 \times 10^8 \text{ m/s}$

so $f_{red} = \frac{c}{\lambda} = \frac{3 \times 10^8 \text{ m/s}}{660 \times 10^{-9} \text{ m}} = 4.55 \times 10^{14} \text{ Hz}$

$f_{IR} = \frac{c}{\lambda} = 3.19 \times 10^{14} \text{ Hz}$

$$\frac{\text{Energy out}}{\text{Energy in}} = \frac{I_{out}}{I_{in}} = \frac{\left(\frac{E_{max,out}^2}{2\mu_0 c}\right)}{\left(\frac{E_{max,in}^2}{2\mu_0 c}\right)}$$

FACT:

Intensity is related to the square of amplitude.


$$= \frac{E_{max,out}^2}{E_{max,in}^2} \quad \text{where } E_{max} \text{ is amplitude of wave}$$

$\Rightarrow \frac{E_{max,out}}{E_{max,in}} = \sqrt{\left(\frac{\text{Energy out}}{\text{Energy in}}\right)}$

$= \sqrt{\frac{0.33}{1}}$ since 33% of energy emitted.

$= \sqrt{0.33} = 0.57 = 57\% \text{ of amplitude}$

(53)

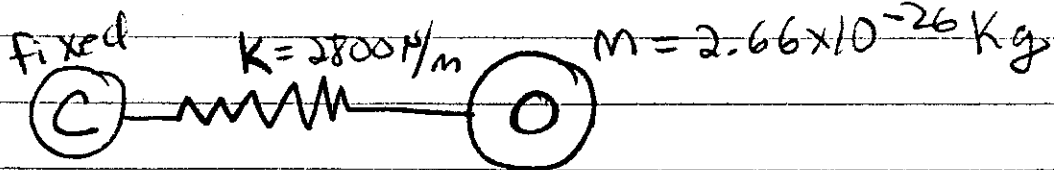

recall for a spring: $F = -Kx$

$$ma = -Kx$$

$$\Rightarrow x = A \cos\left(\sqrt{\frac{K}{m}} t\right)$$

So the resonant frequency

$$f = \frac{1}{2\pi} \sqrt{\frac{K}{m}}$$

$$f = \frac{1}{2\pi} \sqrt{\frac{2800}{2.66 \times 10^{-26}}} \text{ Hz}$$

$$f = 5.2 \times 10^{13} \text{ Hz}$$

What wavelength light corresponds to this frequency?

$$c = f\lambda \Rightarrow \lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/s}}{5.2 \times 10^{13} \text{ 1/s}}$$

$$= 5.8 \times 10^{-6} \text{ m}$$

$$= 5.8 \mu\text{m}$$

IR: $0.7 \mu\text{m} \leq \lambda \leq 1 \text{ mm}$

So $5.8 \mu\text{m}$ is IR ✓