

Name: Adam Cohen

Phys 122-401

10/31/06

QUIZ 8: Inductance

Consider the following equations:

$$\tau = \frac{L}{R} \quad L = \frac{N\Phi_B}{I} \quad (1) \quad \Delta V = IR \quad (2) \quad \vec{F}_m = q\vec{v} \times \vec{B} \quad (3)$$

$$\vec{F}_e = q\vec{E} \quad \vec{E} = -\frac{\Delta V}{\Delta x} \quad (4) \quad I \equiv \frac{\Delta Q}{\Delta t}$$

① Show that the time constant $\tau = \frac{L}{R}$ for an RL circuit has dimensions of time.

$$\tau = \frac{L}{R} = \left[\frac{\left(\frac{T \cdot m^2}{A \cdot s} \right)}{\left(\frac{V}{\Omega} \right)} \right] = \left[\frac{T \cdot m^2}{V} \right] = \left[\frac{\left(\frac{N}{A} \right) \cdot \left(\frac{s}{m} \right) \cdot m^2}{\left(\frac{N}{C} \right)} \right]$$

by (1), (2) by (3), (4)


$$= [s] \quad //$$

② In terms of R, L what is the time constant for the following circuits:



a) $\tau = L/R'$

$$\tau = \frac{L}{2R}$$

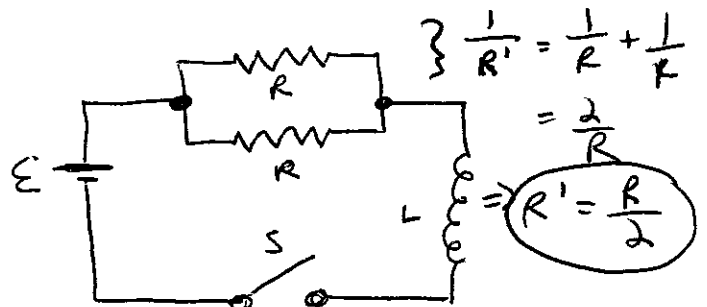

b) $\tau = L/R'$

$$= L / (R/2)$$

$$\tau = 2L/R$$

 //