

March 17, 2017

Physics 132

Prof. E. F. Redish

■ **Theme Music: Kraftwerk**  
*Ohm Sweet Ohm*

■ **Cartoon: Bill Watterson**  
*Calvin & Hobbes*



3/17/17

Physics 132

1

## Outline

- Recap: Principles of electric networks
  - Kirchoff's laws
- Examples


3/17/17

Physics 132

3
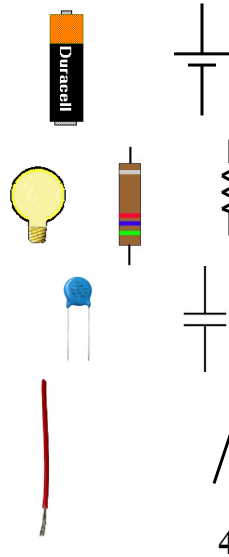
## Electric circuit elements

- **Batteries**—devices that maintain a constant electrical pressure difference across their terminals (like a water pump that raises water to a certain height).
- **Resistances**—devices that have significant drag and oppose current. Pressure will drop across them.
- **Capacitors**— devices that can maintain a separation of charge if there is a potential difference maintained across the,
- **Wires**— have very little resistance. We can ignore the drag in them (mostly – as long as there are other resistances present).



3/17/17

Physics 132

4

## Foothold ideas: Kirchhoff's principles

1. **Flow rule:** The total amount of current flowing into any volume in an electrical network equals the amount flowing out.
2. **Ohm's law:** in a resistor,  $\Delta V = IR$
3. **Loop rule:** Following around any loop in an electrical network the potential has to come back to the same value (sum of drops = sum of rises).



3/17/17

Physics 132

5

## Very useful heuristic

- The Constant Potential Corollary (CPC)  
(Kirchhoff 0)
  - Along any part of a circuit with 0 resistance, then  $\Delta V = 0$ , i.e., the voltage is constant since in any circuit element

$$\Delta V = IR$$

$$R = 0 \Rightarrow \Delta V = 0$$

(even if  $I \neq 0$ )

3/17/17

Physics 132

6

## Electric Power

- The rate at which electric energy is depleted from a battery or dissipated (into heat or light) in a resistor is

$$Power = \frac{dW}{dt} = \frac{d}{dt}(q\Delta V) = \frac{dq}{dt}\Delta V = I\Delta V$$

3/17/17

Physics 132

7

## Units

- Current ( $I$ )      **Ampere** = Coulomb/sec
- Voltage ( $V$ )      **Volt** = Joule/Coulomb
- E-Field ( $E$ )      Newton/Coulomb = Volt/meter
- Resistance ( $R$ )    **Ohm** = Volt/Ampere
- Capacitance ( $C$ ) **Farad** = Coulomb/Volt
- Power ( $P$ )        **Watt** = Joule/sec

3/17/17


Physics 132

**8**

## Series and parallel
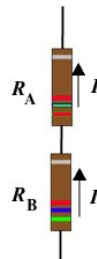
### ■ Series

- Same current flows through both devices




$$I = \frac{\Delta V_A}{R_A} = \frac{\Delta V_B}{R_B}$$

$$\frac{\Delta V_A}{\Delta V_B} = \frac{R_A}{R_B}$$

$$\Delta V = \Delta V_A + \Delta V_B = I(R_A + R_B)$$

### ■ Parallel

- Same voltage drop across both devices

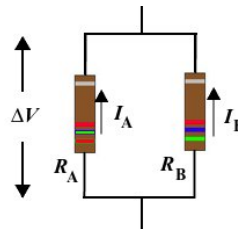

$$\Delta V = I_A R_A = I_B R_B$$

$$\frac{I_A}{I_B} = \frac{R_B}{R_A}$$

$$I = I_A + I_B = \Delta V \left( \frac{1}{R_A} + \frac{1}{R_B} \right)$$

3/17/17