

Problem 28.5

(a) first get an equivalent resistance for the 2 parallel resistors

$$\frac{1}{R_{eq}} = \frac{1}{R_3} + \frac{1}{R_4} \Rightarrow R_{eq}' = \frac{R_3 R_4}{R_3 + R_4}$$

$$R_{eq}' = \frac{(7.0\Omega)(10.0\Omega)}{17.0\Omega} = 4.12\Omega$$

now all 3 in series:

$$R_{eq} = R_1 + R_2 + R_{eq}' = 4.0\Omega + 9.0\Omega + 4.12\Omega = 17.1\Omega$$

(b) $V_{tot} = I R_{eq} \Rightarrow I = \frac{V_{tot}}{R_{eq}} = \frac{34.0V}{17.1\Omega} = 1.99A$

for the 4Ω and 9Ω resistors, this is the current:

$$I_1 = I_2 = I = 1.99A$$

for the parallel resistors:

$$V_{eq}' = I R_{eq}' = 1.99A (4.12\Omega) = 8.18V$$


$$V_{eq}' = V_3 = V_4$$

$$\Rightarrow I_3 = \frac{V_{eq}'}{R_3} = \frac{8.18V}{7.0\Omega} = 1.17A$$

$$I_4 = \frac{V_{eq}'}{R_4} = \frac{8.18V}{10.0\Omega} = 0.818A$$

Problem 28.7

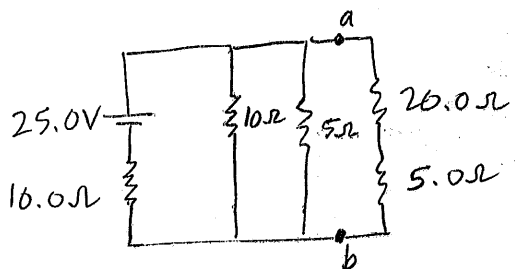(a) Redraw the circuit in a more typical fashion:



get eq resistance for parallel stuff:

$$R_{||} = \left(\frac{1}{10\Omega} + \frac{1}{5\Omega} + \frac{1}{20\Omega + 5\Omega} \right)^{-1} = 2.94\Omega$$

current through battery is

$$I = \frac{V_{\text{Tot}}}{R_{\text{eq}}} \quad \text{w/} \quad R_{\text{eq}} = R_{||} + 10\Omega + 12.94\Omega$$

$$I = \frac{25.0\text{V}}{12.94\Omega} = 1.93\text{A}$$

$$V_{||} = I R_{||} = 1.93\text{A} (2.94\Omega) = 5.68\text{V}$$

current then through 20Ω resistor (and 5Ω) is:

$$I_{20} = \frac{V_{||}}{20\Omega + 5\Omega} = \frac{5.68\text{V}}{25.0\Omega} = 0.227\text{A}$$

(b) V_{ab} is just $V_{||} = 5.68\text{V}$

Problem 28.15

get I through battery:

need R_{eq} :

$$R_{||} = \frac{(1.0\Omega)(3.0\Omega)}{4.0\Omega} = 0.75\Omega$$

$$R_{\text{eq}} = 2.0\Omega + 4.0\Omega + 0.75\Omega = 6.75\Omega$$

(Prob 28.15) cont.

$$I = \frac{V_{\text{bat}}}{R_{\text{eq}}} = \frac{18.0\text{V}}{6.75\Omega} = 2.67\text{A}$$

this is the current through the 2Ω and 4Ω resistors, so:

$$P = I^2 R \Rightarrow P_2 = (2.67\text{A})^2 (2.0\Omega) = 14.2\text{W}$$

$$P_4 = (2.67\text{A})^2 (4.0\Omega) = 28.4\text{W}$$

for parallel guys, need $V_{\parallel}$:

$$V_{\parallel} = I R_{\parallel} = 2.67\text{A} (0.75\Omega) = 2.0\text{V}$$


same for 1Ω and 3Ω :

$$P = \frac{V^2}{R} \Rightarrow P_3 = \frac{(2.0\text{V})^2}{3.0\Omega} = 1.33\text{W}$$

$$P_1 = \frac{(2.0\text{V})^2}{1.0\Omega} = 4.00\text{W}$$

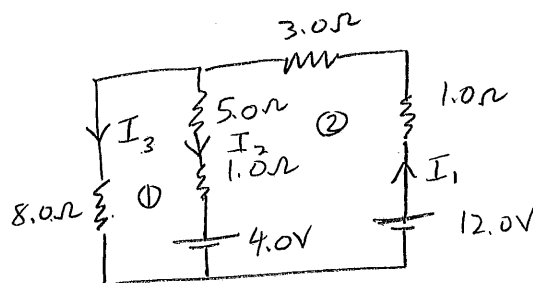Problem 28.17

use Kirchhoff's rules w/
currents labeled as shown:



$$I_1 = I_2 + I_3$$

loop ①:

$$4.0\text{V} + I_2(1.0\Omega + 5.0\Omega) - I_3(8.0\Omega) = 0 \Rightarrow 4 + 6I_2 - 8I_3 = 0$$

loop ②:

$$12.0\text{V} - I_1(1.0\Omega + 3.0\Omega) - I_2(5.0\Omega + 1.0\Omega) - 4.0\text{V} = 0$$

$$\Rightarrow 8 - 4I_1 - 6I_2 = 0$$

$$\Rightarrow I_2 = \frac{4}{3} - \frac{2}{3}I_1$$

plug in ① w/ $I_3 = I_1 - I_2$

$$4 + 6\left(\frac{4}{3} - \frac{2}{3}I_1\right) - 8\left(I_1 + \frac{2}{3}I_1 - \frac{4}{3}\right) = 0$$

(Prob 28.17) cont.

$$4 + 8 - 4I_1 - 8I_1 - \frac{16}{3}I_1 + \frac{32}{3} = 0$$


$$\Rightarrow I_1 = \frac{12 + \frac{32}{3}}{12 + \frac{16}{3}} = 1.31 \text{ A}$$

$$\Rightarrow I_2 = \frac{4}{3} - \frac{2}{3}(1.31 \text{ A}) = 0.462 \text{ A}$$

$$I_3 = I_1 - I_2 = 1.31 \text{ A} - 0.462 \text{ A} = 0.846 \text{ A}$$

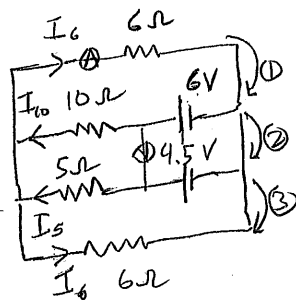Problem 28.21

loop rules (note since ΔV is the same for all branches, I is same through top and bottom):



$$\textcircled{1} \quad 6\text{V} - 10\Omega I_{10} - 6\Omega I_6 = 0$$

$$\textcircled{2} \quad 4.5\text{V} - 5\Omega I_5 + 10\Omega I_{10} - 6\text{V} = 0$$

$$\textcircled{3} \quad 4.5\text{V} - 5\Omega I_5 - 6\Omega I_6 = 0$$

$$\textcircled{4} \quad I_5 + I_{10} = 2I_6 \quad \Rightarrow \quad I_5 = 2I_6 - I_{10}$$

from $\textcircled{2}$ using $\textcircled{4}$

$$5I_{10} - 10I_6 + 10I_{10} = 1.5 \Rightarrow I_{10} = 0.1 + \frac{2}{3}I_6$$

plug in $\textcircled{1}$

$$6 - 1 - \frac{20}{3}I_6 - 6I_6 = 0 \Rightarrow \left(\frac{20}{3} + 6\right)I_6 = 5$$

$$\Rightarrow I_6 = 0.395 \text{ A} \quad \text{reading on meter } \textcircled{A}$$


do loop rule on small loop with batteries and meter only:

$$6.0\text{V} - \Delta V - 4.5\text{V} = 0$$

$$\Rightarrow \Delta V = 1.5\text{V}$$

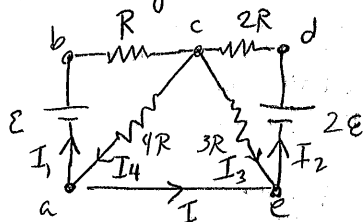Problem 28.22

let's temporarily switch circuits to eliminate variables:



$$R_{eq} = \frac{(4R)(3R)}{7R} = 1.71R$$

now use loop rule eqns:

$$\textcircled{1} \quad 250 - I_1 R - (I_1 + I_2) 1.71R = 0 \Rightarrow 2.71R I_1 + 1.71R I_2 = 250$$

$$\textcircled{2} \quad 500 - 2I_2 R - (I_1 + I_2) 1.71R = 0 \Rightarrow 1.71R I_1 + 3.71R I_2 = 500$$

$$\Rightarrow I_1 = 0.010 \text{ A}, \quad I_2 = 0.130 \text{ A}$$

now

$$\Delta V_{ca'} = \Delta V_{ca} = \Delta V_{ce} = (I_1 + I_2) 1.71R = (0.140 \text{ A})(1.71)(1000)$$

$$\Delta V_{ca} = 240 \text{ V}$$

$$I_4 = \frac{\Delta V_{eq}}{4R} = \frac{240 \text{ V}}{4(1000 \Omega)} = 0.060 \text{ A}$$

now use current sum rule at point a:

$$I_4 = I_1 + I \Rightarrow I = I_4 - I_1 = 0.060 \text{ A} - 0.010 \text{ A} = 0.050 \text{ A}$$

Problem 28.28

$$V(t) = V_0 (1 - e^{-t/RC})$$

Solve for R

$$e^{-t/RC} = 1 - \frac{V(t)}{V_0} \Rightarrow \frac{-t}{RC} = \ln\left(1 - \frac{V(t)}{V_0}\right)$$

$$\Rightarrow R = -\frac{t}{C \ln\left(1 - \frac{V(t)}{V_0}\right)} = \frac{-3.05}{1.0 \times 10^{-5} \text{ F} \ln\left(1 - \frac{4 \text{ V}}{10 \text{ V}}\right)} = 5.87 \times 10^5 \Omega$$

Problem 28.32

(a) $\tau = RC = (1.0 \times 10^5 \Omega + 5.0 \times 10^4 \Omega)(10.0 \times 10^{-6} \text{ F}) = 1.50 \text{ s}$

(b) only $100 \text{ k}\Omega$ resistor will affect capacitor charge

$$\tau = (1.0 \times 10^5 \Omega)(10.0 \times 10^{-6} \text{ F}) = 1.00 \text{ s}$$

(c) battery side current:

$$I = \frac{V_{\text{bat}}}{50 \text{ k}\Omega} = \frac{10.0 \text{ V}}{5.0 \times 10^4 \Omega} = 2.0 \times 10^{-4} \text{ A}$$

capacitor side is:

$$I = I_0 e^{-t/RC} = \left(\frac{10.0 \text{ V}}{1.0 \times 10^5 \Omega} \right) e^{-t/1.00 \text{ s}}$$

total current then is:

$$I(t) = 2.0 \times 10^{-4} \text{ A} - 1.0 \times 10^{-4} \text{ A} e^{-t/1.00 \text{ s}}$$

Problem 29.1

using $\vec{F} = q \vec{v} \times \vec{B}$ and right-hand rule:

(a) up

(b) out of page (don't forget to acct for sign)

(c) $\vec{F} = 0$, no deflection

(d) into page (mag. $q v B \sin 45^\circ$)

Problem 29.6

(a) need speed:

$$\Delta K = \Delta U = e\Delta V \Rightarrow \frac{1}{2}mv_f^2 = e\Delta V \Rightarrow v_f = \sqrt{\frac{2e\Delta V}{m}}$$

$$v_f = \sqrt{\frac{2(1.6 \times 10^{-19})(2400V)}{9.11 \times 10^{-31} \text{ kg}}} = 2.9 \times 10^7 \text{ m/s}$$

force is max when $\vec{v} \perp \vec{B}$

$$F = qvB = (1.6 \times 10^{-19} \text{ C})(2.9 \times 10^7 \text{ m/s})(1.70 \text{ T}) = 7.90 \times 10^{-17} \text{ N}$$

(b) force is zero when $\vec{v} \parallel \pm \vec{B}$

Problem 29.14

again $v = \sqrt{\frac{2qV}{m}}$

set mag-force equal to centripetal force

$$qvB = \frac{mv^2}{r} \Rightarrow r = \frac{mv}{qB} = \frac{1}{B} \sqrt{\frac{2mV}{q}}$$

$$\Rightarrow R = \frac{1}{B} \sqrt{\frac{2m\Delta V}{e}}$$

and

$$R' = 2R = \frac{1}{B} \sqrt{\frac{2m'\Delta V}{2e}}$$

$$\Rightarrow m = \frac{R^2 B^2 e}{2\Delta V} \quad ; \quad m' = \frac{4R^2 B^2 (2e)}{2\Delta V}$$

$$\Rightarrow \frac{m'}{m} = 8$$

Problem 29.17

$$\text{need } |F_e| = |F_{\text{mag}}| = qE = qvB$$

$$\text{if } E = \frac{1}{2}mv^2, \text{ then } v = \sqrt{\frac{2E}{m}}$$

$$E = B \sqrt{\frac{2E}{m}} = 1.5 \times 10^{-2} \text{ T} \sqrt{\frac{2(750 \text{ eV})}{9.11 \times 10^{-31} \text{ kg}} \left(\frac{1.6 \times 10^{-19} \text{ J}}{1 \text{ eV}} \right)}$$

$$E = 2.44 \times 10^5 \text{ N/C}$$

Problem 29.23

the trick here is in the geometry:

the deflection angle needed matches the angle the e^- is deflected by the field:

$$\theta = \tan^{-1}\left(\frac{25}{10}\right) = 68.2^\circ$$

$$R = \frac{1.0 \text{ cm}}{\sin 68.2^\circ} = 1.08 \text{ cm}$$

$$v = \sqrt{\frac{2q\Delta V}{m}} = \sqrt{\frac{2(1.6 \times 10^{-19} \text{ C})(50 \times 10^3 \text{ V})}{9.11 \times 10^{-31} \text{ kg}}} = 1.33 \times 10^8 \text{ m/s}$$

now again

$$qvB = \frac{mv^2}{R} \Rightarrow B = \frac{mv}{qR} = \frac{(9.11 \times 10^{-31} \text{ kg})(1.33 \times 10^8 \text{ m/s})}{(1.6 \times 10^{-19} \text{ C})(0.0108 \text{ m})}$$

$$B = 0.0701 \text{ T}$$

