

Problem 32.5

want to find $\frac{dI}{dt}$; use $\mathcal{E}_L = -L \frac{dI}{dt} \Rightarrow \frac{dI}{dt} = -\frac{\mathcal{E}}{L}$

$$L = \mu_0 \frac{N^2}{l} A = (4\pi \times 10^{-7}) \frac{(450)^2}{0.16 \text{ m}} (3.00 \times 10^{-4} \text{ m}^2) = 4.16 \times 10^{-4} \text{ H}$$

$$\Rightarrow \frac{dI}{dt} = \frac{-1.75 \times 10^{-4} \text{ V}}{4.16 \times 10^{-4} \text{ H}} = -0.421 \text{ A/s}$$

Problem 32.6

$$\mathcal{E}_L = -L \frac{dI}{dt} ; \frac{dI}{dt} = 2.0t - 6.0$$

$$(a) \mathcal{E}_1 = -90.0 \times 10^{-3} \text{ H} (2.0(1.0\text{s}) - 6.0) = 0.360 \text{ V}$$

$$(b) \mathcal{E}_4 = -0.0900 \text{ H} (2(4.0\text{s}) - 6.0) = -0.180 \text{ V}$$

$$(c) 0 = -0.090 [2t_0 - 6]$$

$$\Rightarrow 0.540 = 0.180t_0$$

$$\Rightarrow t_0 = 3.0 \text{ s}$$

Problem 32.7

$$(a) B = \mu_0 n I = (4\pi \times 10^{-7}) \left(\frac{450}{0.12 \text{ m}} \right) (0.040 \text{ A}) = 1.88 \times 10^{-4} \text{ T}$$

$$(b) \Phi = \vec{B} \cdot \vec{A} = BA = (1.88 \times 10^{-4} \text{ T}) \pi \left(\frac{0.015 \text{ m}}{2} \right)^2 = 3.33 \times 10^{-8} \text{ Wb}$$

$$(c) L = \frac{N\Phi}{I} = \frac{450(3.33 \times 10^{-8} \text{ Wb})}{0.040 \text{ A}} = 0.375 \text{ mH}$$

(d) the field and flux would change if the current changed, but the current actually divides out of the expression for L such that L is independent of I ; this can be seen by plugging for Φ .

Problem 32.12

if the inductor were not present, the current would be (constant):

$$I = \frac{\mathcal{E}}{R} = \frac{12\text{V}}{24\Omega} = 0.50\text{A}$$

w/ the inductor, the current will approach this value asymptotically;
looking at

$$I = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau}) = \frac{\mathcal{E}}{R} (1 - e^{-Rt/L})$$


$$(a) L \sim 0 \Rightarrow Rt/L \rightarrow \infty \Rightarrow e^{-Rt/L} \rightarrow \frac{1}{e^\infty} = \frac{1}{\infty} = 0$$

so the turn on will be almost instantaneous, with an essentially constant current of $\sim 500\text{mA}$;

(b) normal case;

$$(c) L \rightarrow \infty \Rightarrow Rt/L \sim 0 \Rightarrow e^{-Rt/L} \sim \frac{1}{e^0} = 1$$

so the turn on will be extremely slow, i.e. the current will take "forever" to reach 500mA ;

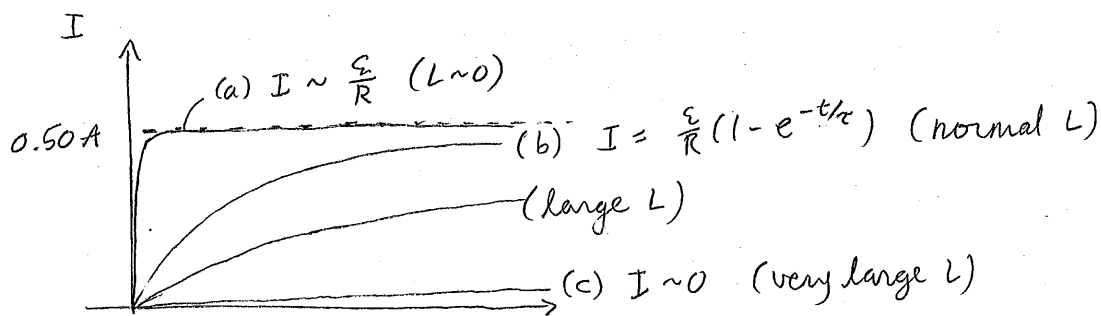

Problem 32.13

$$(a) \tau = \frac{L}{R} = \frac{8.0 \times 10^{-3} \text{H}}{4.0 \Omega} = 2.0 \times 10^{-3} \text{s} = 2.0 \text{ms}$$

$$(b) I(t) = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau})$$

$$\Rightarrow I(250\mu\text{s}) = \frac{6.0\text{V}}{4.0\Omega} \left[1 - \exp\left(-\frac{2.50 \times 10^{-4} \text{s}}{2.0 \times 10^{-3} \text{s}}\right) \right]$$

$$I(250\mu\text{s}) = 0.176\text{A}$$

(Prob 32.13) cont.

(c) value if inductor was not present:

$$I_0 = \frac{\mathcal{E}}{R} = \frac{6.0\text{V}}{4.0\Omega} = 1.50\text{A}$$

$$(d) 0.8I_0 = I_0(1 - e^{-t/\tau})$$

$$\Rightarrow 0.8 = 1 - e^{-t/2.0\text{ms}}$$

$$e^{-t/2.0\text{ms}} = 0.2$$

$$-\frac{t}{2.0\text{ms}} = \ln 0.2 = -1.609$$

$$\Rightarrow t = 3.22\text{ms}$$

Problem 32.14

$$\mathcal{E}_L = -L \frac{dI}{dt}$$

$$I(t) = \frac{\mathcal{E}}{R}(1 - e^{-t/\tau}) \Rightarrow \frac{dI}{dt} = \frac{\mathcal{E}}{R} \left(\frac{R}{L} \right) e^{-t/\tau} = \frac{\mathcal{E}}{L} e^{-t/\tau}$$

$$\Rightarrow \mathcal{E}_L = -L \left. \frac{dI}{dt} \right|_{0.200\text{s}} = 120\text{V} e^{-(9.0\Omega)(0.20\text{s})/7.0\text{H}} = 92.8\text{V}$$

Problem 32.15

(a) could get $\mathcal{E}_L$ by finding t for $I(t) = 2.0\text{A}$, then find $\left. \frac{dI}{dt} \right|_t$,
but it's much easier to just use Kirchhoff loop rule:

$$V_R = IR = 2.0\text{A}(8.0\Omega) = 16.0\text{V}$$

$$\mathcal{E} - V_R - V_L = 0 \Rightarrow V_L = \mathcal{E} - V_R = 36.0\text{V} - 16.0\text{V} = 20.0\text{V}$$

$$\Rightarrow \frac{V_R}{V_L} = \frac{16.0\text{V}}{20.0\text{V}} = 0.8$$

$$(b) V_R = (4.50\text{A})(8.0\Omega) = 36.0\text{V}$$

$$V_L = \mathcal{E} - V_R = 0\text{V}$$

Problem 32.28

(a) after a long time, current goes to ohm's law value:

$$I = \frac{\mathcal{E}}{R} = \frac{10.0\text{V}}{5.0\Omega} = 2.0\text{A}$$

total power from battery:

$$P = I\mathcal{E} = (2.0\text{A})(10.0\text{V}) = 20.0\text{W}$$

(b) to the resistor:

$$P_R = I^2 R = (2.0\text{A})^2 (5.0\Omega) = 20.0\text{W}$$

(c) resistor is using all power

$$\Rightarrow P_L = 0$$

$$(d) \quad U = \frac{1}{2} LI^2 = \frac{1}{2} (10.0\text{H})(2.0\text{A})^2 = 20.0\text{J}$$

Problem 32.33

$$(a) \quad M = \frac{N_B \Phi_{AB}}{I_A} = \frac{700(9.0 \times 10^{-5} \text{Wb})}{3.50\text{A}} = 18.0\text{mH}$$

$$(b) \quad L_A = \frac{N_A \Phi_A}{I_A} = \frac{400(3.00 \times 10^{-4} \text{Wb})}{3.50\text{A}} = 34.3\text{mH}$$

$$(c) \quad \mathcal{E}_B = -M \frac{dI_A}{dt} = -(0.0180\text{H})(0.50\text{A/s}) = -9.00\text{mV}$$

Problem 32.34

$$(a) \quad M = \frac{N_2 \Phi_{12}}{I_1} = \frac{N_2 B_1 A_2}{I_1} = \frac{\mu_0 N_2 N_1 I (\pi R_2^2)}{l I} = \frac{\mu_0 \pi N_1 N_2 R_2^2}{l}$$

$$(b) \quad M = \frac{N_1 \Phi_{21}}{I_2} = \frac{N_1 B_2 A_2}{I_2} = \frac{\mu_0 N_1 N_2 I (\pi R_2^2)}{l I} = \frac{\mu_0 \pi N_1 N_2 R_2^2}{l}$$

(c) Since the field outside the smaller coil 2 is zero, the flux through coil 1 is also dependent on A_2 ; hence the two values are the same.

Problem 34.1

(a) looking at Gauss's law in its simplest form:

$$\Phi_E = \frac{q_{enc}}{\epsilon_0}$$

$$\Rightarrow \frac{d\Phi_E}{dt} = \frac{1}{\epsilon_0} \frac{dq}{dt} = \frac{I}{\epsilon_0} = \frac{0.10 A}{8.85 \times 10^{-12}} = 11.3 \times 10^9 \text{ N/C}\cdot\text{s}$$

(b) displacement current $\bar{i}$

$$I_d = \epsilon_0 \frac{d\Phi_E}{dt} = \epsilon_0 \left(\frac{I}{\epsilon_0} \right) = I = 0.10 \text{ A}$$

Problem 34.2

(a)

$$\frac{d\Phi_E}{dt} = \frac{d}{dt} (\vec{E} \cdot \vec{A}) = \frac{I}{\epsilon_0}$$

$$\Rightarrow A \frac{dE}{dt} = \frac{I}{\epsilon_0} \Rightarrow \frac{dE}{dt} = \frac{I}{\pi R^2 \epsilon_0} = \frac{0.20 \text{ A}}{\pi (0.10 \text{ m})^2 (8.85 \times 10^{-12})}$$

$$\frac{dE}{dt} = 7.19 \times 10^{11} \text{ V}\cdot\text{m/s}$$

(b) ampere's law, displacement current version:

$$\oint \vec{B} \cdot d\vec{s} = \mu_0 \epsilon_0 \frac{d\Phi_E}{dt}$$

$$B(2\pi r) = \mu_0 \epsilon_0 A_r \frac{dE}{dt} = \mu_0 \pi r^2 \left(\frac{I}{\pi R^2} \right)$$

$$\Rightarrow B = \frac{\mu_0 I r}{2\pi R^2} = \frac{(4\pi \times 10^{-7})(0.20 \text{ A})(0.05 \text{ m})}{2\pi (0.10 \text{ m})^2}$$

$$\Rightarrow B = 2.00 \times 10^{-7} \text{ T}$$

note this expression for the field is the same as for the field inside a current-carrying wire.

