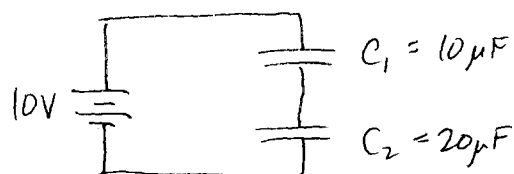


Two capacitors, $C_1 = 10 \mu\text{F}$ and $C_2 = 20 \mu\text{F}$, are connected in series to a 10V battery [Note that μ stands for 10^{-6}].

(a) [1 pts] Draw the circuit diagram.



(b) [3 pts] Find the equivalent capacitance of the combination.

Series:

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$C_{eq} = \frac{(10 \mu\text{F})(20 \mu\text{F})}{30 \mu\text{F}} = 6.67 \mu\text{F}$$

(c) [3 pts] Find the potential difference across each individual capacitor.

do part (d) first:

$$V_1 = \frac{Q_{eq}}{C_1} = \frac{6.67 \times 10^{-5} \text{ C}}{10 \times 10^{-6} \text{ F}} = 6.67 \text{ V}$$

$$V_2 = \frac{Q_{eq}}{C_2} = \frac{6.67 \times 10^{-5} \text{ C}}{20 \times 10^{-6} \text{ F}} = 3.33 \text{ V}$$

(d) [3 pts] Find the charge stored on each individual capacitor.

$$C = \frac{Q}{V} \Rightarrow Q_{eq} = C_{eq} V_{\text{battery}} = (6.67 \times 10^{-6} \text{ F})(10 \text{ V})$$

$$Q_{eq} = 6.67 \times 10^{-5} \text{ C} = 66.7 \mu\text{C}$$

Q is the same for all capacitors in series

$$Q_{eq} = Q_1 = Q_2$$

$$\Rightarrow Q_2 = Q_1 = 66.7 \mu\text{C}$$