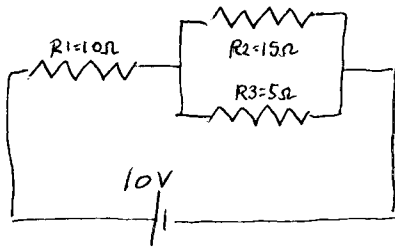


NAME:

Quiz #5:  
Phys142

Solution


[4pts] Find the resulting current through  $R_1$  in the following circuit:current through  $R_1$  is current through battery  
find  $R_{eq}$ :

$$R_{||} = \frac{R_2 R_3}{R_2 + R_3} = \frac{(15\Omega)(5\Omega)}{20\Omega} = 3.75\Omega$$

$$I_1 = I = \frac{V_{bat}}{R_{eq}} = \frac{V_{bat}}{R_1 + R_{||}} = \frac{10V}{10\Omega + 3.75\Omega} = 0.73 A$$

An electron with a kinetic energy of 750 eV is fired into a region of uniform magnetic field which is restricted to the square region shown below. The magnetic field points into the page, and the electron is initially traveling directly to the right as depicted in the diagram. A uniform electric field is applied such that the magnetic force on the electron is counteracted by the electric force. The electron continues to travel in a straight line even in the region of uniform magnetic field. (a) [1 pt] Show the required direction of the electric field on the diagram below

(b) [3 pts] What is the magnitude of the electric field required?

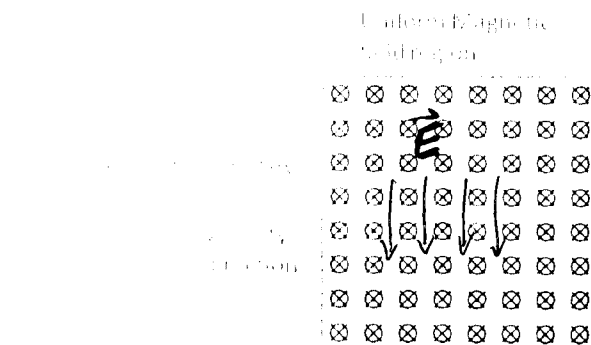Note that  $1 \text{ eV} = 1.9 \times 10^{-19} \text{ J}$ magnitudes of Electric force  
and magnetic force are equal.

$$qE = qvB$$

$$K = \frac{1}{2}mv^2$$

$$\Rightarrow v = \sqrt{\frac{2K}{m}}$$

$$\Rightarrow E = B \sqrt{\frac{2K}{m}}$$