
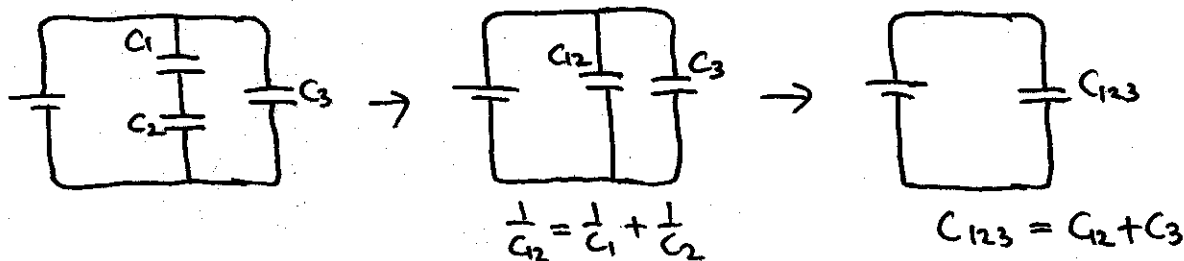


30.61

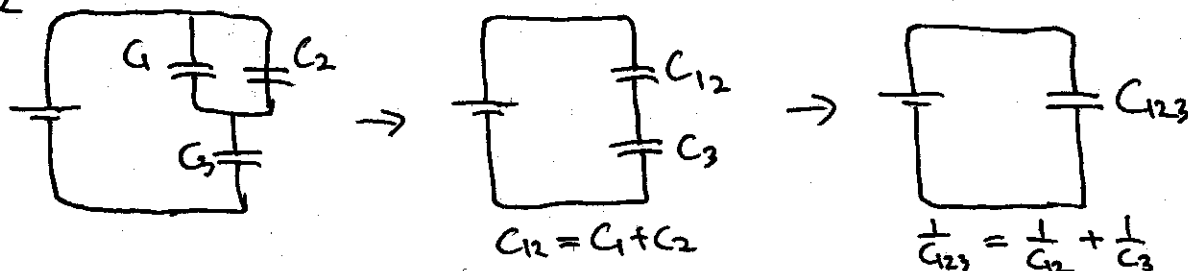

30.62



30.64 $C_{12} = C_1 + C_2$, $\frac{1}{C_{23}} = \frac{1}{C_{12}} + \frac{1}{C_3}$


$$Q_1 + Q_2 = Q_3 = (C_{123})(9V)$$

$$V_3 = Q_3 / C_3$$


$$V_1 = V_2 = (Q_1 + Q_2) / C_{12} = \frac{C_{123}(9V)}{C_1 + C_2}$$

$$Q_1 = C_1 V_1, Q_2 = C_2 V_2$$

30.68

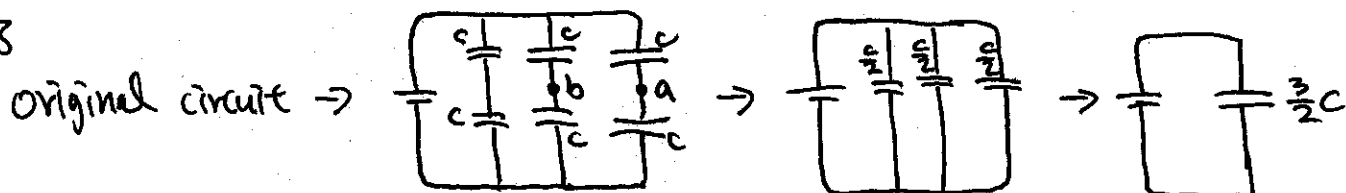

~~$V_b = V_a$~~ $V_b - V_a = 0$

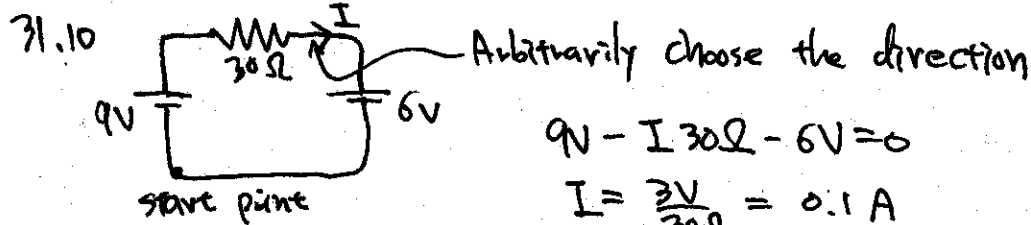

$$9V - I 30\Omega - 6V = 0$$

$$I = \frac{3V}{30\Omega} = 0.1 A$$

The current has the direction in our initial choice of direction because $\underbrace{I}_{\text{not me}}$ is positive.

31.12 $I = \frac{15V}{10\Omega + 20\Omega} = \frac{1}{2} A$

(Part A): $\Delta V = I \cdot 10\Omega = 5V$

(Part B): $\Delta V = I \cdot 20\Omega = 10V$


31.14

$$(a) I = \frac{9V}{12\Omega + 19\Omega} = \frac{9}{27} A = \frac{1}{3} A$$


$$P = I^2 R = \left(\frac{1}{9} A^2\right)(12\Omega) = \frac{12}{9} W = \frac{4}{3} W$$

$$(b) P = I^2 R = \left(\frac{1}{9} A^2\right)(15\Omega) = \frac{15}{9} W = \frac{5}{3} W$$

31.32

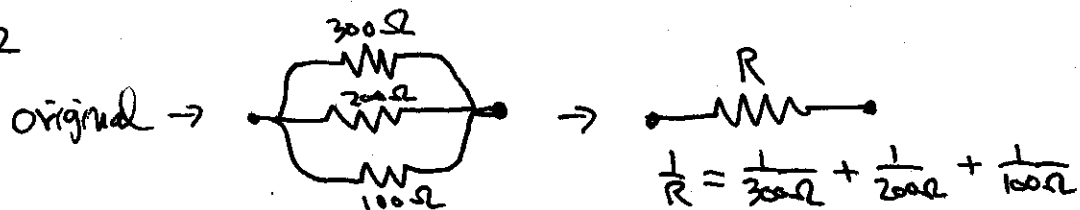

31.50

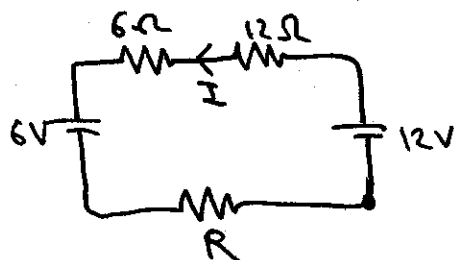


$$12V - 12\Omega I - 6\Omega I - 6V - RI = 0$$

$$\Rightarrow R = \frac{6V}{I} - 18\Omega = \frac{6V}{1/4 A} - 18\Omega = 6\Omega$$

Direction of current is counter clockwise

$$P_{\text{diss}} = I^2 R = \left(\frac{1}{4}\right)^2 6 W = \frac{6}{16} W$$

31.68

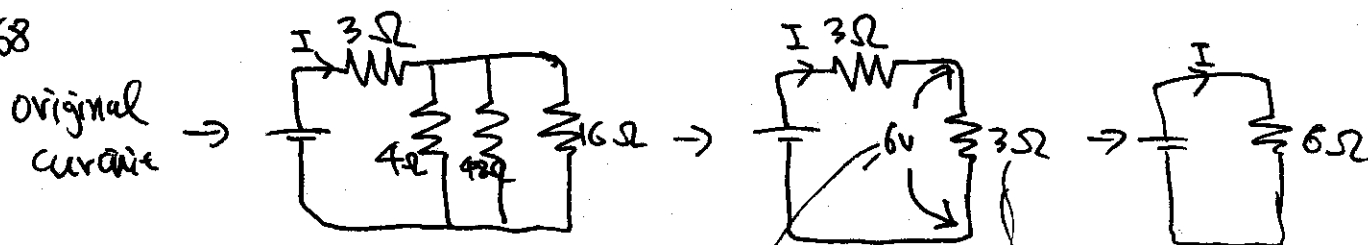

$$(a) I = \frac{12V}{6\Omega} = 2 A$$

$$(b) \Delta V = IR = (2A)(3\Omega) = 6 V$$

$$(c) \Delta V \text{ across } 4\Omega, 48\Omega, 16\Omega = I(3\Omega) = 6 V$$

$$I = 6V/4\Omega = \frac{3}{2} A$$

$$(d) 6V \leftarrow$$

$$(e) I = 6V/48\Omega = 0.125 A$$

$$(f) 6V \leftarrow$$

$$(g) I = 6V/16\Omega = 0.375 A$$

$$(h) 6V \leftarrow$$