

Q28.29 Suppose $\mathcal{E} = 12 \text{ V}$ and each lamp has $R = 2 \Omega$. Before the switch is closed the current is $\frac{12 \text{ V}}{6 \Omega} = 2 \text{ A}$. The potential difference across each lamp is $(2 \text{ A})(2 \Omega) = 4 \text{ V}$. The power of each lamp is $(2 \text{ A})(4 \text{ V}) = 8 \text{ W}$, totaling 24 W for the circuit. Closing the switch makes the switch and the wires connected to it a zero-resistance branch. All of the current through A and B will go through the switch and (b) lamp C goes out, with zero voltage across it. With less total resistance, the (c) current in the battery $\frac{12 \text{ V}}{4 \Omega} = 3 \text{ A}$ becomes larger than before and (a) lamps A and B get brighter. (d) The voltage across each of A and B is $(3 \text{ A})(2 \Omega) = 6 \text{ V}$, larger than before. Each converts power $(3 \text{ A})(6 \text{ V}) = 18 \text{ W}$, totaling 36 W , which is (e) an increase.

P28.6

$$(a) \quad R_p = \frac{1}{(1/7.00 \, \Omega) + (1/10.0 \, \Omega)} = 4.12 \, \Omega$$

$$R_s = R_1 + R_2 + R_3 = 4.00 + 4.12 + 9.00 = \boxed{17.1 \, \Omega}$$

$$(b) \quad \Delta V = IR$$

$$34.0 \, \text{V} = I(17.1 \, \Omega)$$

$$I = \boxed{1.99 \, \text{A}} \text{ for } 4.00 \, \Omega, 9.00 \, \Omega \text{ resistors.}$$


$$\text{Applying } \Delta V = IR, \quad (1.99 \, \text{A})(4.12 \, \Omega) = 8.18 \, \text{V}$$

$$8.18 \, \text{V} = I(7.00 \, \Omega)$$

$$\text{so } I = \boxed{1.17 \, \text{A}} \text{ for } 7.00 \, \Omega \text{ resistor}$$

$$8.18 \, \text{V} = I(10.0 \, \Omega)$$

$$\text{so } I = \boxed{0.818 \, \text{A}} \text{ for } 10.0 \, \Omega \text{ resistor.}$$

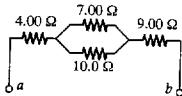**FIG. P28.6**

P28.24 We name the currents I_1 , I_2 , and I_3 as shown.

$$[1] \quad 70.0 - 60.0 - I_2(3.00 \text{ k}\Omega) - I_1(2.00 \text{ k}\Omega) = 0$$

$$[2] \quad 80.0 - I_3(4.00 \text{ k}\Omega) - 60.0 - I_2(3.00 \text{ k}\Omega) = 0$$

$$[3] \quad I_2 = I_1 + I_3$$

- (a) Substituting for I_2 and solving the resulting simultaneous equations yields

$$I_1 = \boxed{0.385 \text{ mA}} \quad (\text{through } R_1)$$

$$I_3 = \boxed{2.69 \text{ mA}} \quad (\text{through } R_3)$$

$$I_2 = \boxed{3.08 \text{ mA}} \quad (\text{through } R_2)$$

(b) $\Delta V_{cf} = -60.0 \text{ V} - (3.08 \text{ mA})(3.00 \text{ k}\Omega) = \boxed{-69.2 \text{ V}}$

Point c is at higher potential.

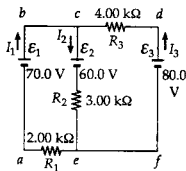


FIG. P28.24

P28.36

(a) $\tau = RC = (1.50 \times 10^5 \, \Omega)(10.0 \times 10^{-6} \, \text{F}) = \boxed{1.50 \, \text{s}}$

(b) $\tau = (1.00 \times 10^5 \, \Omega)(10.0 \times 10^{-6} \, \text{F}) = \boxed{1.00 \, \text{s}}$

(c) The battery carries current

$$\frac{10.0 \, \text{V}}{50.0 \times 10^3 \, \Omega} = 200 \, \mu\text{A}.$$

The $100 \, \text{k}\Omega$ carries current of magnitude

$$I = I_0 e^{-t/RC} = \left(\frac{10.0 \, \text{V}}{100 \times 10^3 \, \Omega} \right) e^{-t/1.00 \, \text{s}}.$$

So the switch carries downward current

$$\boxed{200 \, \mu\text{A} + (100 \, \mu\text{A})e^{-t/1.00 \, \text{s}}}.$$

P28.71 (a) After steady-state conditions have been reached, there is no DC current through the capacitor.

Thus, for R_3 : $I_{R_3} = 0$ (steady-state).

For the other two resistors, the steady-state current is simply determined by the 9.00-V emf across the 12-k Ω and 15-k Ω resistors in series:

For R_1 and R_2 : $I_{(R_1+R_2)} = \frac{\mathcal{E}}{R_1 + R_2} = \frac{9.00 \text{ V}}{(12.0 \text{ k}\Omega + 15.0 \text{ k}\Omega)} = 333 \mu\text{A}$ (steady-state).

(b) After the transient currents have ceased, the potential difference across C is the same as the potential difference across $R_2 (= IR_2)$ because there is no voltage drop across R_3 . Therefore, the charge Q on C is

$$Q = C(\Delta V)_{R_2} = C(IR_2) = (10.0 \mu\text{F})(333 \mu\text{A})(15.0 \text{ k}\Omega) = 50.0 \mu\text{C}.$$

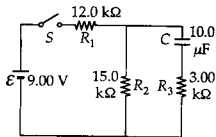


FIG. P28.71(b)