



Electrical Oscillators

Mechanical Oscillator: energy is converted between kinetic and elastic potential

$$KE = \frac{1}{2}mv^2 = \frac{1}{2}m\dot{x}^2$$

$$U = \frac{1}{2}kx^2$$


AMPAD

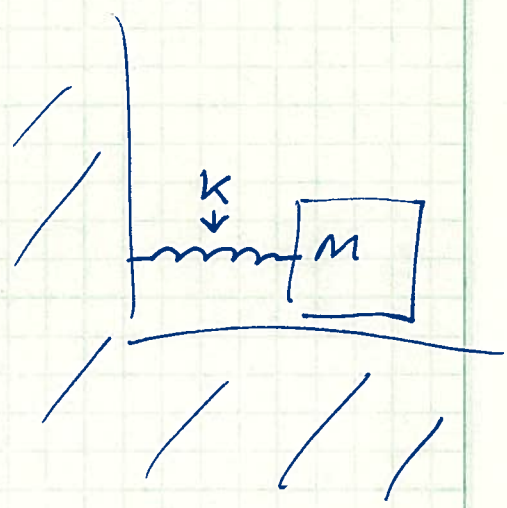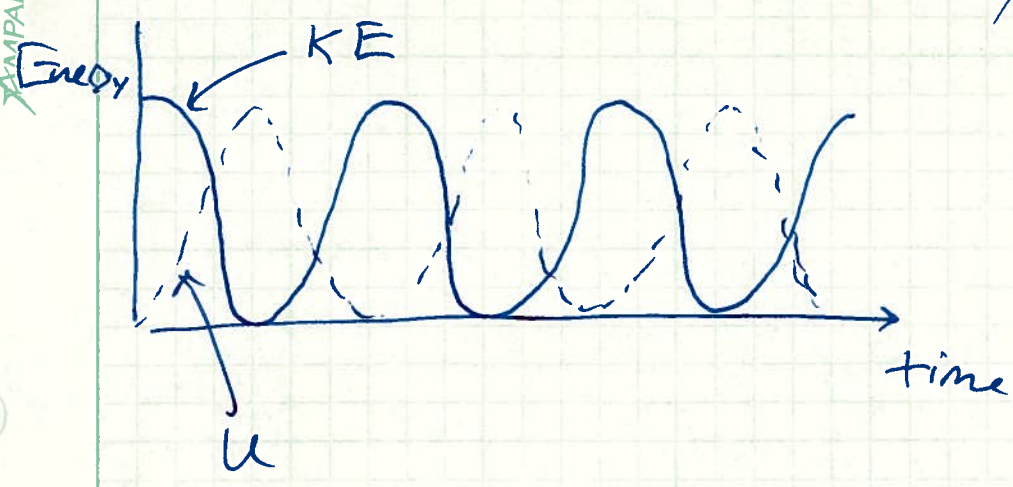

Electrical Oscillator: Energy is converted between electric (\vec{E} field) and magnetic (\vec{B} field).

① Capacitor: Device for storing energy in an electric field

Ex: Parallel Plate Capacitor

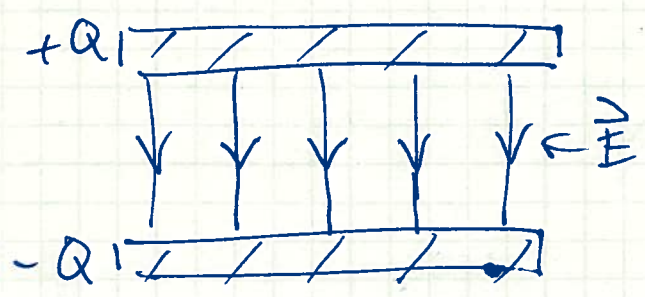

Each small volume of space (dV) with an electric field \vec{E} stores a small amount of electric energy (dU_E):

$$dU_E = \underbrace{\frac{1}{2} \epsilon_0 |\vec{E}|^2}_{u_E} dV, \quad u_E = \frac{1}{2} \epsilon_0 |\vec{E}|^2$$

Energy, big U \nearrow

u_E
↑
energy density, little u

= "electric energy density of free space"
= $\frac{\text{Joules}}{\text{meter}^3}$

The total energy stored is

"big U " $\rightarrow U_E = \int_{\text{all space}} \frac{1}{2} \epsilon_0 |\vec{E}|^2 dV$

If the electric field is created by a capacitor with charges $+Q$ and $-Q$ and voltage difference V , then the total energy can be written

$$U_E = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{Q^2}{2C}$$


where $C = \text{capacitance} = \frac{Q}{V}$

Capacitance is a constant that only depends on the shape and material of the capacitor.

" $Q = CV$ " says "charge on the capacitor is proportional to the voltage across it. C is the proportionality constant."

② Inductor: Device for storing energy in a magnetic field.

A simple solenoid:

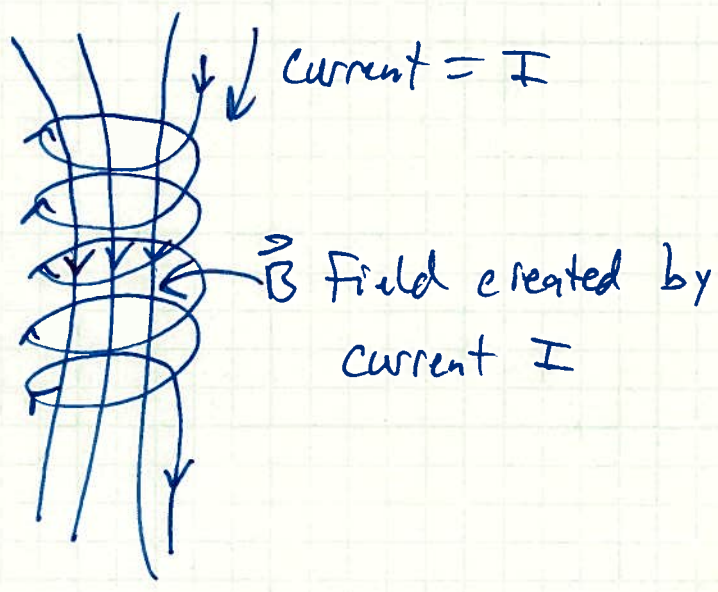

The energy density of a magnetic field is

$$dU_B = \frac{1}{2\mu_0} |\vec{B}|^2 dV, \quad u_B = \frac{1}{2\mu_0} |\vec{B}|^2$$

The total magnetic energy is

$$\Rightarrow U_B = \int_{\text{all space}} \frac{1}{2\mu_0} |\vec{B}|^2 dV$$

"little u" = "magnetic energy density of free space"

"big u"

For an inductor, the total energy can be written as

$$= \frac{\text{Joules}}{\text{meter}^3}$$

$$U_B = \frac{1}{2} LI^2, \quad \text{where } L = \text{"self-inductance"}$$

L is determined by the shape and material of the inductor. It is the proportionality constant between magnetic flux and current:

Φ_B = magnetic flux through the inductor = LI
 ↑ ↓ current
 proportionality constant.

Similarities between C & L

Device	Circuit Symbol	MKS unit	Stores energy in:	Proportionality Constant:	Determined by
C		Farad	\vec{E}	$Q = CV$	Shape and material
L		Henry	\vec{B}	$\Phi_B = LI$	

If you know the shape & material of your capacitor/inductor, then you can calculate $\left\{ \begin{matrix} C \\ L \end{matrix} \right\}$.

Neither C nor L depends on $\left\{ \begin{matrix} Q \\ V \\ I \end{matrix} \right\}$ These things depend on time, but C & L are constant.

Voltage Rules:

Capacitor: $|V_C| = \left| \frac{1}{C} Q \right|$ or $V_C = \frac{1}{C} Q$ (ignoring any sign)

Inductor: $|V_L| = \left| - \frac{d\Phi_B}{dt} \right| = \left| - \frac{d(LI)}{dt} \right| = \left| L \frac{dI}{dt} \right|$


$\therefore V_L = L \frac{dI}{dt}$ (ignoring any sign)

LC oscillator

Simplest electrical oscillator.

Energy exchanges between electric & magnetic.

q = charge on plate

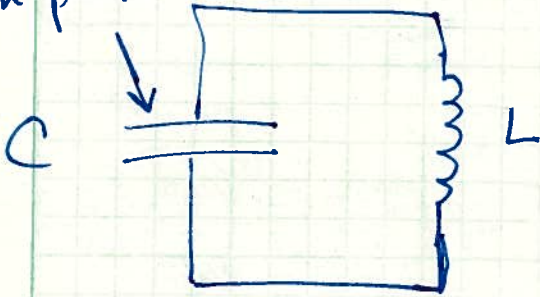

Voltage Loop rule:

$$V_C + V_L = \emptyset$$

$$\left(\frac{1}{C} q\right) \left(L \frac{dI}{dt}\right) = L \frac{dq}{dt^2}$$

since $I = \frac{dq}{dt}$

$$\therefore \frac{1}{C} q + L \frac{d^2 q}{dt^2} = \emptyset$$

$$\boxed{\ddot{q} + \frac{1}{LC} q = \emptyset}$$

Simple harmonic oscillator equation

Solution: $q(t) = q_0 e^{i(\omega_0 t + \delta)}$, where $\omega_0 = \frac{1}{\sqrt{LC}}$

q_0 & δ are determined by the initial conditions

= "natural freq."

$$\dot{q}(t) = I(t) = (i\omega_0)(q_0 e^{i(\omega_0 t + \delta)}) = i\omega_0 q(t)$$

current has a phase shift of 90° compared to charge

Energy: $U_E = \text{electric energy}$

$$= \frac{1}{2C} q^2 = \frac{1}{2C} [q_0 \cos(\omega_0 t + \delta)]^2$$

$$= \frac{q_0^2}{2C} \cos^2(\omega_0 t + \delta)$$

$U_B = \text{magnetic energy}$

$$= \frac{1}{2} L I^2$$

$$= \frac{1}{2} L \left[\frac{q_0}{C} \operatorname{Re}(i \omega_0 e^{i(\omega_0 t + \delta)}) \right]^2$$


$$= \frac{1}{2} q_0^2 \omega_0^2 L \sin^2(\omega_0 t + \delta)$$

$$\omega_0^2 = \frac{1}{LC} \quad \text{so} \quad \omega_0^2 L = \frac{1}{C}$$

$$= \frac{q_0^2}{2C} \sin^2(\omega_0 t + \delta)$$


Total energy = $U_E + U_B = \frac{q_0^2}{2C} \left[\cos^2(\omega_0 t + \delta) + \sin^2(\omega_0 t + \delta) \right]$

$$= \frac{q_0^2}{2C} = \text{constant}$$

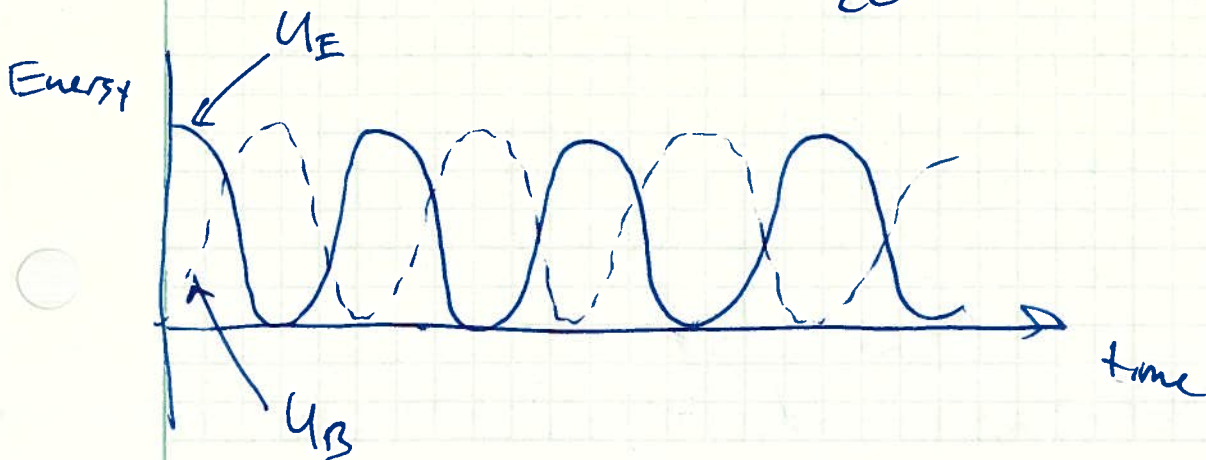

LC oscillator with damping - RLC circuit

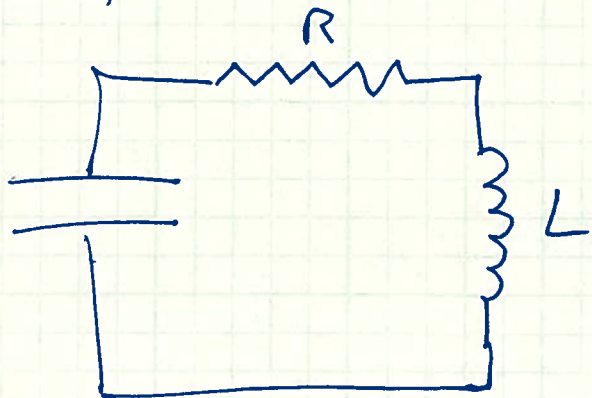Add a resistor to the circuit: Electrical energy will be converted to heat in the resistor



Voltage Rule:

$$V_C + V_R + V_L = 0$$

$$\downarrow \quad \downarrow \quad \downarrow$$

$$\frac{q}{C} \quad IR \quad L \frac{dI}{dt} = L \frac{dq}{dt}$$

$$= -\dot{q}R \quad = L\ddot{q}$$

$$\therefore \frac{q}{C} + R\dot{q} + L\ddot{q} = 0$$

$$\ddot{q} + \frac{R}{L}\dot{q} + \frac{1}{LC}q = 0$$


Simple Harmonic Oscillator with damping

Solution (light damping):

$$q(t) = q_0 e^{-\gamma/2 t} e^{i(\omega t + \delta)}$$

where $\gamma = \frac{R}{L}$

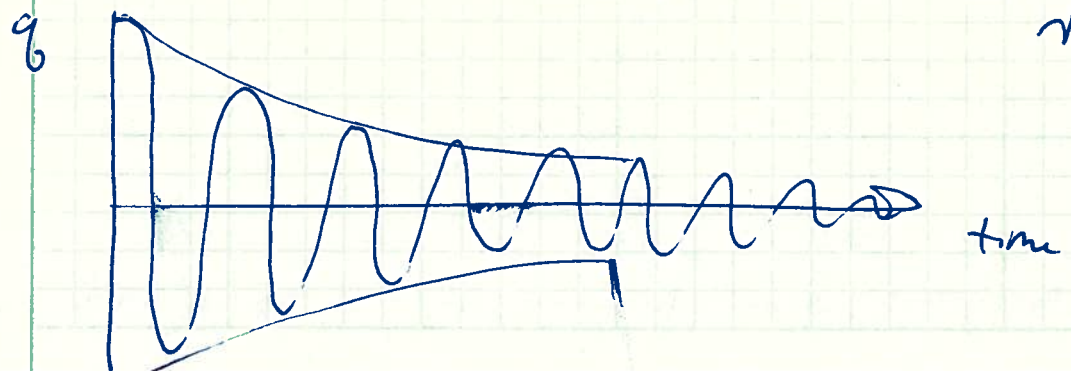and $\omega = \sqrt{\omega_0^2 - \frac{\gamma^2}{4}}$



Driven RLC circuit - Series


Suppose we have an oscillating circuit with a voltage source that varies in time as a cosine:

$$V_{source}(t) = V_0 \cos(\omega t) = V_0 e^{i\omega t}$$

↑
driving frequency

We choose δ (phase shift) = ϕ by choosing $t = \phi$ correctly.

Then the RLC series circuit looks like:

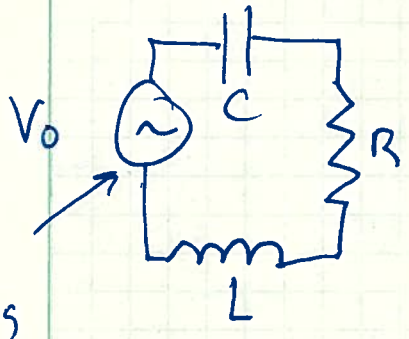

time varying voltage source

Voltage Loop Rule:

$$V_S = V_C + V_R + V_L$$

\downarrow \downarrow \downarrow \downarrow
 $(V_0 e^{i\omega t})$ $(\frac{1}{C} q)$ $(R \dot{q})$ $(L \ddot{q})$

$$\ddot{q} + \left(\frac{R}{L}\right) \dot{q} + \left(\frac{1}{LC}\right) q = \left(\frac{V_0}{L}\right) e^{i\omega t}$$

Driven Harmonic Oscillator.

Steady State

Solution: $q(t) = q_0 e^{i(\omega t + \delta)}$ or $A e^{i(\omega t + \delta)}$

where

$$q_0(\omega) = \frac{V_0/L}{\sqrt{(\omega_0^2 - \omega^2)^2 + (\omega r)^2}}$$

ω = driving frequency

$$\omega_0 = \frac{1}{\sqrt{LC}}$$



$$r = (R/L)$$

and $\delta(\omega) = -\tan^{-1} \left[\frac{\omega R}{\omega_0^2 - \omega^2} \right]$

Just like the forced mechanical oscillators, we have a resonance when $\omega \approx \omega_0$.

When $\omega \approx \omega_0$, the following things become very large:

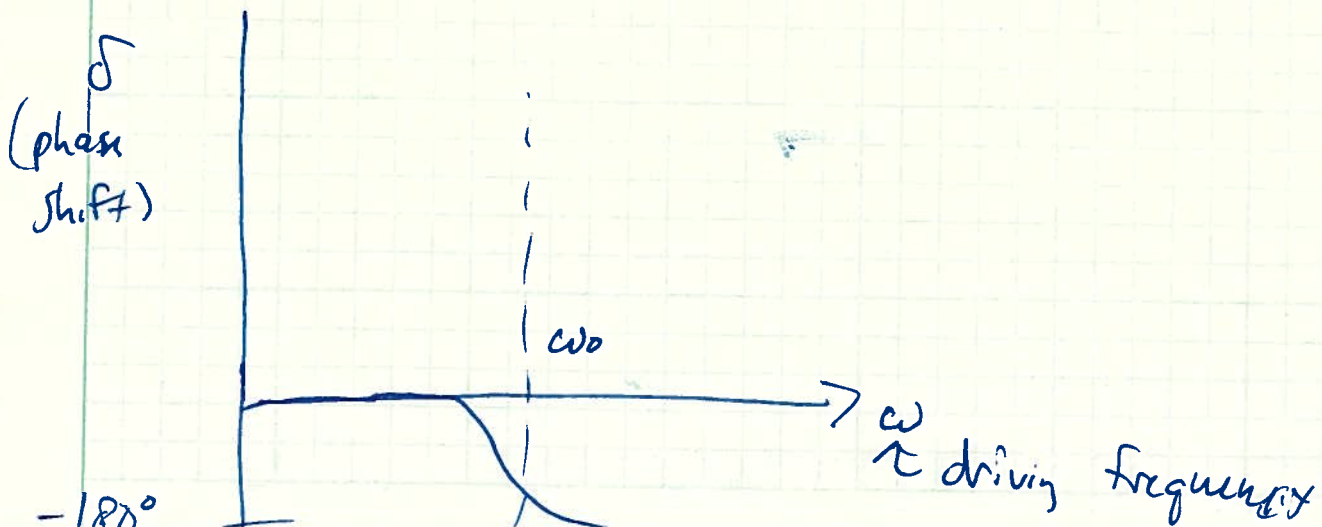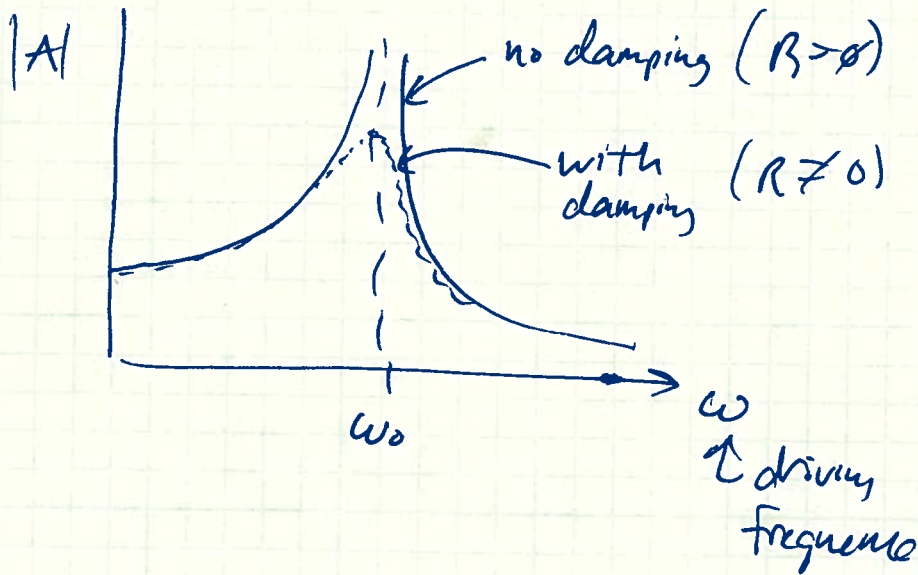- 1) the peak charge on the capacitor
- 2) the peak current in the circuit
- 3) the ^{total} energy stored in the C & L.



AMPAD