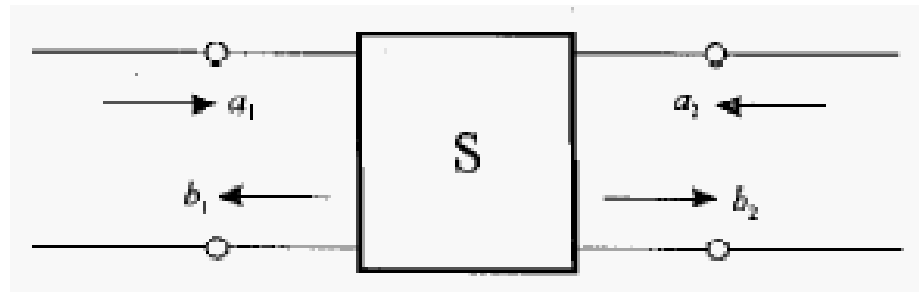


Network Analysis



$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

Assumes linearity!

If port 2 is terminated by a perfect match of impedance Z_{02} , i.e. all of the incident energy is absorbed in the termination, we have the following properties

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad \text{and} \quad S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0}$$

The S-parameter representation equally applies to multi-port devices. For an n -port device, the S-parameter matrix is given by


$$\begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_n \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \cdots & S_{1n} \\ S_{21} & S_{22} & \cdots & S_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ S_{n1} & S_{n2} & \cdots & S_{nn} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ \vdots \\ a_n \end{bmatrix}$$

$$S_{ij} = \left. \frac{b_i}{a_j} \right|_{a_k=0 \text{ for } k \neq j}$$

N-Port Description of an Arbitrary Enclosure

N Ports

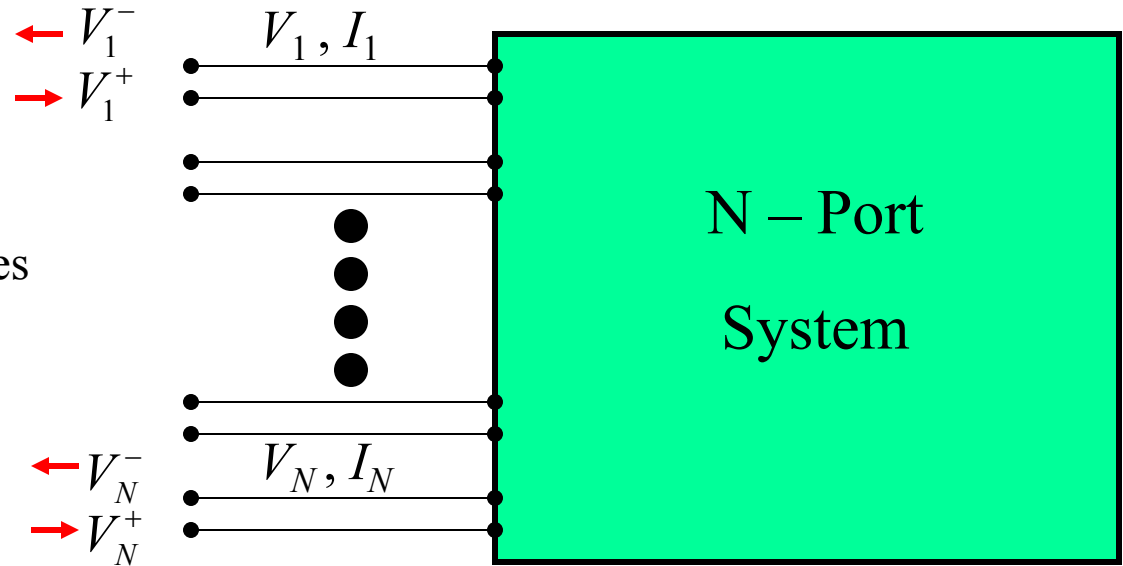- ← Voltages and Currents,
- ← Incoming and Outgoing Waves



S matrix

$$\begin{bmatrix} V_1^- \\ V_2^- \\ \bullet \\ \bullet \\ \bullet \\ V_N^- \end{bmatrix} = [S] \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \\ \bullet \\ \bullet \\ \bullet \\ V_N^+ \end{bmatrix}$$

Z matrix

$$\begin{bmatrix} V_1 \\ V_2 \\ \bullet \\ \bullet \\ \bullet \\ V_N \end{bmatrix} = [Z] \cdot \begin{bmatrix} I_1 \\ I_2 \\ \bullet \\ \bullet \\ \bullet \\ I_N \end{bmatrix}$$


$$S = (Z + Z_0)^{-1} (Z - Z_0)$$

$$Z(\omega), S(\omega)$$

← Complicated
Functions of
frequency

← Detail Specific
(Non-Universal)

Network Analysis

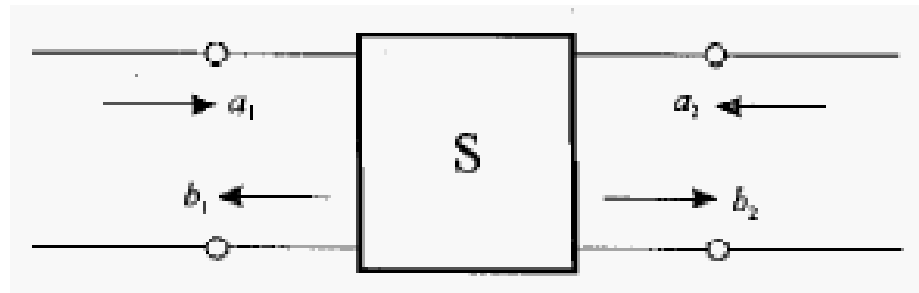




2-port system

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

Assumes linearity!

If port 2 is terminated by a perfect match of impedance Z_{02} , i.e. all of the incident energy is absorbed in the termination, we have the following properties

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad \text{and} \quad S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0}$$

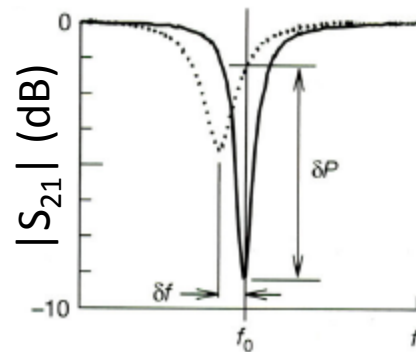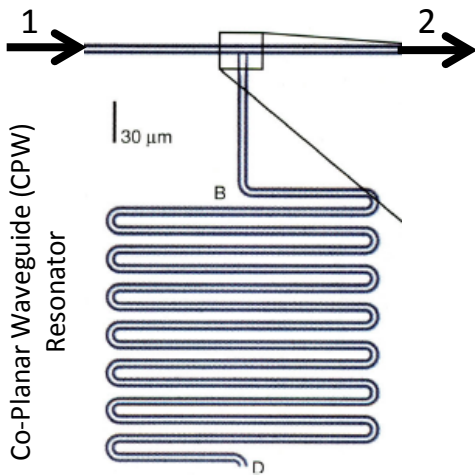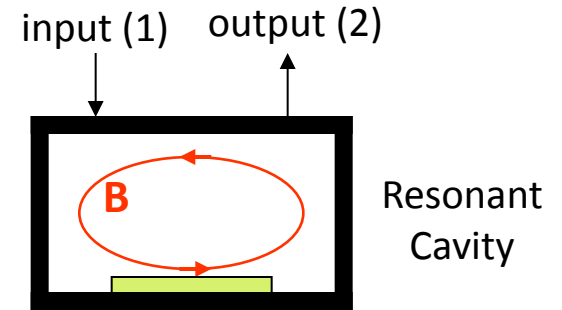

P. K. Day, Nature, 2003

