

Q28.29 Suppose $\mathcal{E} = 12 \text{ V}$ and each lamp has $R = 2 \Omega$. Before the switch is closed the current is $\frac{12 \text{ V}}{6 \Omega} = 2 \text{ A}$. The potential difference across each lamp is $(2 \text{ A})(2 \Omega) = 4 \text{ V}$. The power of each lamp is $(2 \text{ A})(4 \text{ V}) = 8 \text{ W}$, totaling 24 W for the circuit. Closing the switch makes the switch and the wires connected to it a zero-resistance branch. All of the current through A and B will go through the switch and (b) lamp C goes out, with zero voltage across it. With less total resistance, the (c) current in the battery $\frac{12 \text{ V}}{4 \Omega} = 3 \text{ A}$ becomes larger than before and (a) lamps A and B get brighter. (d) The voltage across each of A and B is $(3 \text{ A})(2 \Omega) = 6 \text{ V}$, larger than before. Each converts power $(3 \text{ A})(6 \text{ V}) = 18 \text{ W}$, totaling 36 W , which is (e) an increase.

P28.1 (a) $\mathcal{P} = \frac{(\Delta V)^2}{R}$

becomes $20.0 \text{ W} = \frac{(11.6 \text{ V})^2}{R}$

so $R = \boxed{6.73 \, \Omega}$.

(b) $\Delta V = IR$

so $11.6 \text{ V} = I(6.73 \, \Omega)$

and $I = 1.72 \text{ A}$

$$\mathcal{E} = IR + Ir$$

so $15.0 \text{ V} = 11.6 \text{ V} + (1.72 \text{ A})r$

$r = \boxed{1.97 \, \Omega}$.

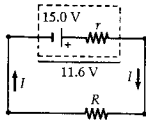


FIG. P28.1

P28.4

(a) Here $\mathcal{E} = I(R + r)$, so $I = \frac{\mathcal{E}}{R + r} = \frac{12.6 \text{ V}}{(5.00 \, \Omega + 0.0800 \, \Omega)} = 2.48 \text{ A}.$

Then, $\Delta V = IR = (2.48 \text{ A})(5.00 \, \Omega) = \boxed{12.4 \text{ V}}.$

(b) Let I_1 and I_2 be the currents flowing through the battery and the headlights, respectively.

Then, $I_1 = I_2 + 35.0 \text{ A}$, and $\mathcal{E} - I_1 r - I_2 r = 0$

so $\mathcal{E} = (I_2 + 35.0 \text{ A})(0.0800 \, \Omega) + I_2(5.00 \, \Omega) = 12.6 \text{ V}$

giving $I_2 = 1.93 \text{ A}.$

Thus, $\Delta V_2 = (1.93 \text{ A})(5.00 \, \Omega) = \boxed{9.65 \text{ V}}.$

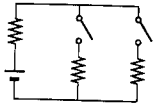


FIG. P28.4

P28.6

$$(a) \quad R_p = \frac{1}{(1/7.00 \, \Omega) + (1/10.0 \, \Omega)} = 4.12 \, \Omega$$

$$R_s = R_1 + R_2 + R_3 = 4.00 + 4.12 + 9.00 = \boxed{17.1 \, \Omega}$$

$$(b) \quad \Delta V = IR$$

$$34.0 \, \text{V} = I(17.1 \, \Omega)$$

$$I = \boxed{1.99 \, \text{A}} \text{ for } 4.00 \, \Omega, 9.00 \, \Omega \text{ resistors.}$$


$$\text{Applying } \Delta V = IR, \quad (1.99 \, \text{A})(4.12 \, \Omega) = 8.18 \, \text{V}$$

$$8.18 \, \text{V} = I(7.00 \, \Omega)$$

$$\text{so } I = \boxed{1.17 \, \text{A}} \text{ for } 7.00 \, \Omega \text{ resistor}$$

$$8.18 \, \text{V} = I(10.0 \, \Omega)$$

$$\text{so } I = \boxed{0.818 \, \text{A}} \text{ for } 10.0 \, \Omega \text{ resistor.}$$

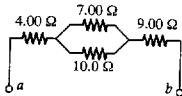**FIG. P28.6**

P28.11 (a) Since all the current in the circuit must pass through the series $100\ \Omega$ resistor, $\mathcal{P} = I^2 R$

$$\mathcal{P}_{\max} = R I_{\max}^2$$

$$\text{so } I_{\max} = \sqrt{\frac{\mathcal{P}}{R}} = \sqrt{\frac{25.0\ \text{W}}{100\ \Omega}} = 0.500\ \text{A}$$

$$R_{\text{eq}} = 100\ \Omega + \left(\frac{1}{100} + \frac{1}{100} \right)^{-1} \Omega = 150\ \Omega$$

$$\Delta V_{\max} = R_{\text{eq}} I_{\max} = \boxed{75.0\ \text{V}}$$

(b) $\mathcal{P} = I \Delta V = (0.500\ \text{A})(75.0\ \text{V}) = \boxed{37.5\ \text{W}}$ total power

$$\mathcal{P}_1 = \boxed{25.0\ \text{W}}$$

$$\mathcal{P}_2 = \mathcal{P}_3 = R I^2 (100\ \Omega)(0.250\ \text{A})^2 = \boxed{6.25\ \text{W}}$$

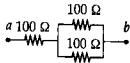


FIG. P28.11

P28.15

$$R_p = \left(\frac{1}{3.00} + \frac{1}{1.00} \right)^{-1} = 0.750 \, \Omega$$

$$R_s = (2.00 + 0.750 + 4.00) \, \Omega = 6.75 \, \Omega$$

$$I_{\text{battery}} = \frac{\Delta V}{R_s} = \frac{18.0 \, \text{V}}{6.75 \, \Omega} = 2.67 \, \text{A}$$

$$\mathcal{P} = I^2 R: \quad \mathcal{P}_2 = (2.67 \, \text{A})^2 (2.00 \, \Omega)$$

$$\mathcal{P}_2 = \boxed{14.2 \, \text{W}} \text{ in } 2.00 \, \Omega$$

$$\mathcal{P}_4 = (2.67 \, \text{A})^2 (4.00 \, \Omega) = \boxed{28.4 \, \text{W}} \text{ in } 4.00 \, \Omega$$

$$\Delta V_2 = (2.67 \, \text{A})(2.00 \, \Omega) = 5.33 \, \text{V},$$

$$\Delta V_4 = (2.67 \, \text{A})(4.00 \, \Omega) = 10.67 \, \text{V}$$

$$\Delta V_p = 18.0 \, \text{V} - \Delta V_2 - \Delta V_4 = 2.00 \, \text{V} (= \Delta V_3 = \Delta V_1)$$

$$\mathcal{P}_3 = \frac{(\Delta V_3)^2}{R_3} = \frac{(2.00 \, \text{V})^2}{3.00 \, \Omega} = \boxed{1.33 \, \text{W}} \text{ in } 3.00 \, \Omega$$

$$\mathcal{P}_1 = \frac{(\Delta V_1)^2}{R_1} = \frac{(2.00 \, \text{V})^2}{1.00 \, \Omega} = \boxed{4.00 \, \text{W}} \text{ in } 1.00 \, \Omega$$


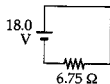
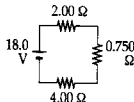


FIG. P28.15

P28.18 (a) $\Delta V = IR$: $33.0 \text{ V} = I_1(11.0 \, \Omega)$ $33.0 \text{ V} = I_2(22.0 \, \Omega)$
 $I_3 = 3.00 \text{ A}$ $I_2 = 1.50 \text{ A}$

$\mathcal{P} = I^2 R$: $\mathcal{P}_1 = (3.00 \text{ A})^2(11.0 \, \Omega)$ $\mathcal{P}_2 = (1.50 \text{ A})^2(22.0 \, \Omega)$
 $\mathcal{P}_1 = 99.0 \text{ W}$ $\mathcal{P}_2 = 49.5 \text{ W}$

The 11.0- Ω resistor uses more power.

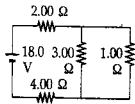

FIG. P28.18(a)

(b) $\mathcal{P}_1 + \mathcal{P}_2 = \boxed{148 \text{ W}}$ $\mathcal{P} = I(\Delta V) = (4.50)(33.0) = \boxed{148 \text{ W}}$

(c) $R_s = R_1 + R_2 = 11.0 \, \Omega + 22.0 \, \Omega = 33.0 \, \Omega$

$\Delta V = IR$: $33.0 \text{ V} = I(33.0 \, \Omega)$, so $I = 1.00 \text{ A}$

$\mathcal{P} = I^2 R$: $\mathcal{P}_1 = (1.00 \text{ A})^2(11.0 \, \Omega)$ $\mathcal{P}_2 = (1.00 \text{ A})^2(22.0 \, \Omega)$
 $\mathcal{P}_1 = 11.0 \text{ W}$ $\mathcal{P}_2 = 22.0 \text{ W}$

The 22.0- Ω resistor uses more power.

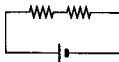


FIG. P28.18(c)

(d) $\mathcal{P}_1 + \mathcal{P}_2 = I^2(R_1 + R_2) = (1.00 \text{ A})^2(33.0 \, \Omega) = \boxed{33.0 \text{ W}}$

$\mathcal{P} = I(\Delta V) = (1.00 \text{ A})(33.0 \text{ V}) = \boxed{33.0 \text{ W}}$

(e) The parallel configuration uses more power.

P28.21 We name currents I_1 , I_2 , and I_3 as shown.

From Kirchhoff's current rule, $I_3 = I_1 + I_2$.

Applying Kirchhoff's voltage rule to the loop containing I_2 and I_3 ,

$$12.0 \text{ V} - (4.00)I_3 - (6.00)I_2 - 4.00 \text{ V} = 0$$

$$8.00 = (4.00)I_3 + (6.00)I_2$$

Applying Kirchhoff's voltage rule to the loop containing I_1 and I_2 ,

$$-(6.00)I_2 - 4.00 \text{ V} + (8.00)I_1 = 0 \quad (8.00)I_1 = 4.00 + (6.00)I_2.$$

Solving the above linear system, we proceed to the pair of simultaneous equations:

$$\begin{cases} 8 = 4I_1 + 4I_2 + 6I_2 \\ 8I_1 = 4 + 6I_2 \end{cases} \quad \text{or} \quad \begin{cases} 8 = 4I_1 + 10I_2 \\ I_2 = 1.33I_1 - 0.667 \end{cases}$$

and to the single equation $8 = 4I_1 + 13.3I_1 - 6.67$

$$I_1 = \frac{14.7 \text{ V}}{17.3 \Omega} = 0.846 \text{ A.} \quad \text{Then} \quad I_2 = 1.33(0.846 \text{ A}) - 0.667$$

and $I_3 = I_1 + I_2$ give $I_1 = 846 \text{ mA}, I_2 = 462 \text{ mA}, I_3 = 1.31 \text{ A}$.

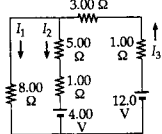


FIG. P28.21

All currents are in the directions indicated by the arrows in the circuit diagram.

P28.27 Using Kirchhoff's rules,

$$12.0 - (0.0100)I_1 - (0.0600)I_3 = 0$$

$$10.0 + (1.00)I_2 - (0.0600)I_3 = 0$$

and $I_1 = I_2 + I_3$

$$12.0 - (0.0100)I_2 - (0.0700)I_3 = 0$$

$$10.0 + (1.00)I_2 - (0.0600)I_3 = 0$$

Solving simultaneously,

$$I_2 = \boxed{0.283 \text{ A downward}} \text{ in the dead battery}$$

and $I_3 = \boxed{171 \text{ A downward}}$ in the starter.

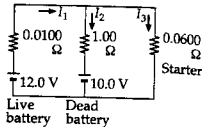


FIG. P28.27

#10-13 Answers in the textbook.